



Putting the New 8-bit PIC[®] MCU Peripherals to Work in the Real World

1610 CLC

Objectives

At the end of this class you will be able to describe the function of and implement designs using the PIC16F1509

- **Configurable Logic Cell (CLC)**
- **Numerically Controlled Oscillator (NCO)**
- **Complimentary Waveform Generator (CWG)**

Agenda

- **Overview of the new Peripherals**
 - **CLC**
 - **CLC Design Tool**
 - Lab 1 Manchester Encoder
 - **NCO**
 - Lab 2 Manchester Decoder
 - **CWG**
 - Lab 3 Driving a motor using the PIC Communicator
 - Lab 4 Combining all three modules to send motor speed



Configurable Logic Cell (CLC)

Configurable Logic Cell



What does it do?

Performs one of eight single output logic functions on a selection of 4 of 16 inputs. Operates outside the speed limitations of software execution.

Benefits:


- **Increases on chip interconnection**
- **Replaces External Components**
- **Saves Code Space - function as a programmable logic device**

Configurable Logic = Consolidation

  

Code-free implementation with many PIC® MCUs


Configurable Logic Cell

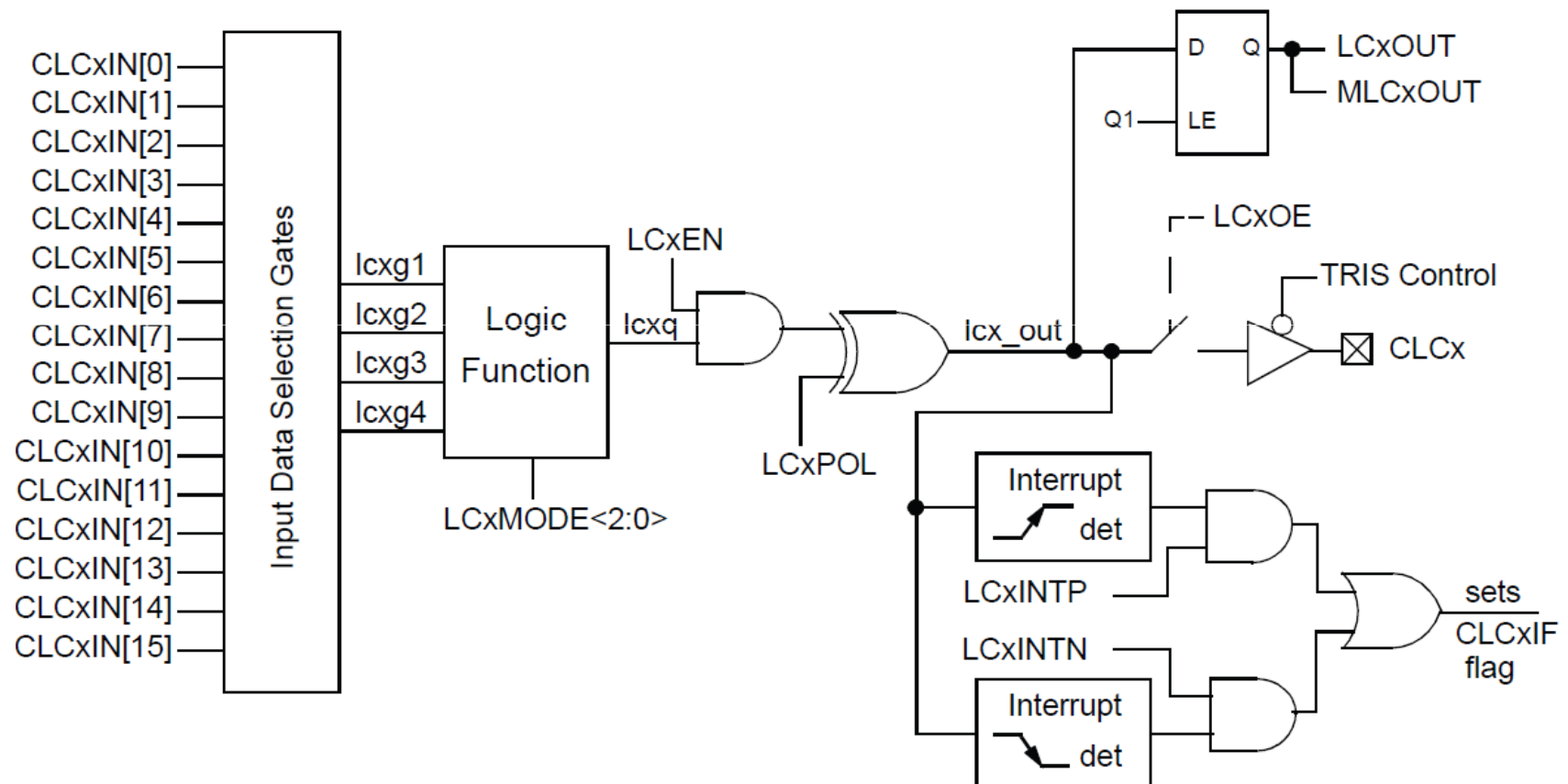




CLC Designer


CLC Designer

 

Configurable Logic Cell Peripheral Setup

 


Configurable Logic Cell Peripheral Setup

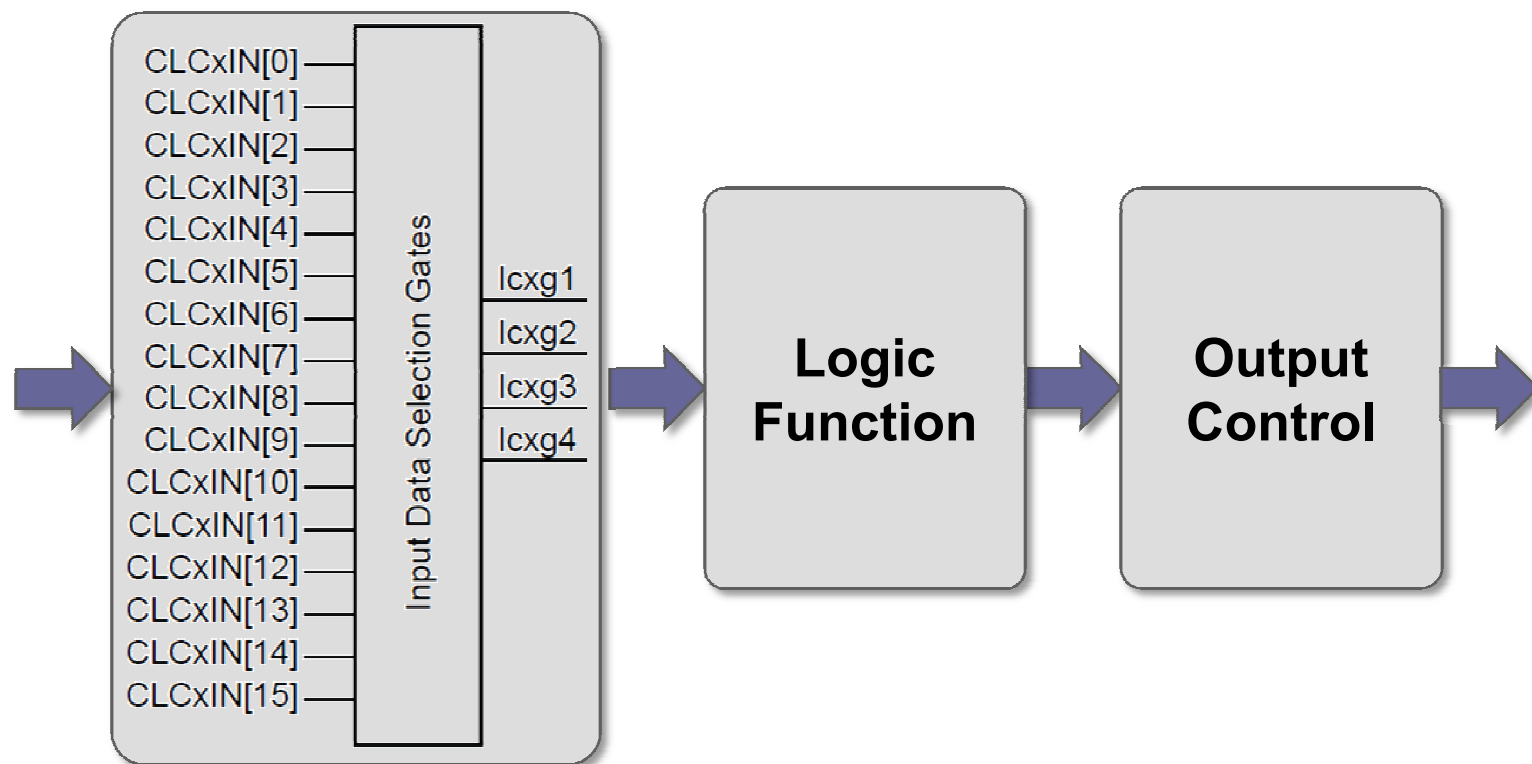


**Input Data
Selection and
Data Gating**

CLC Design Tool

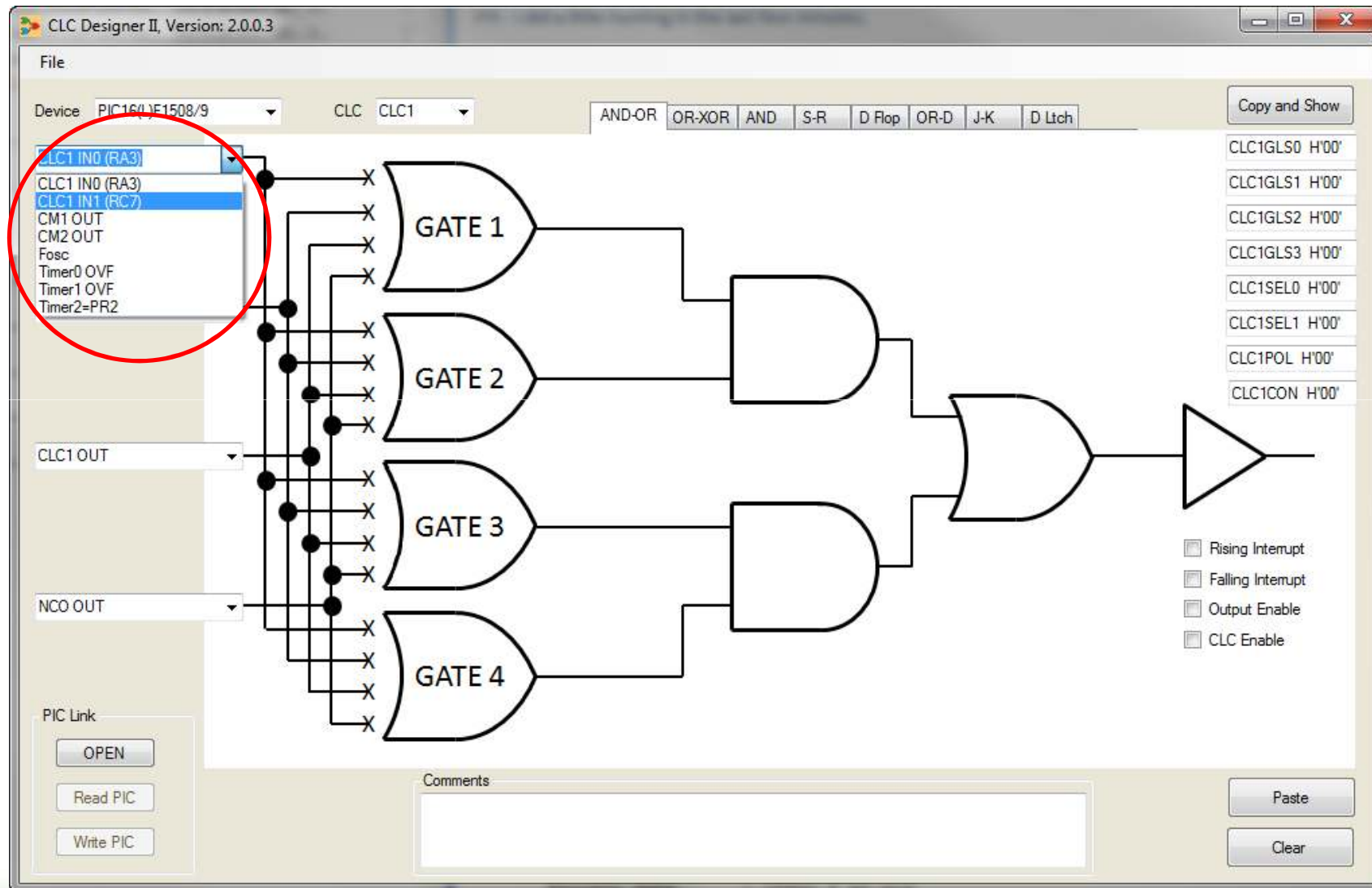


Configurable Logic Cell

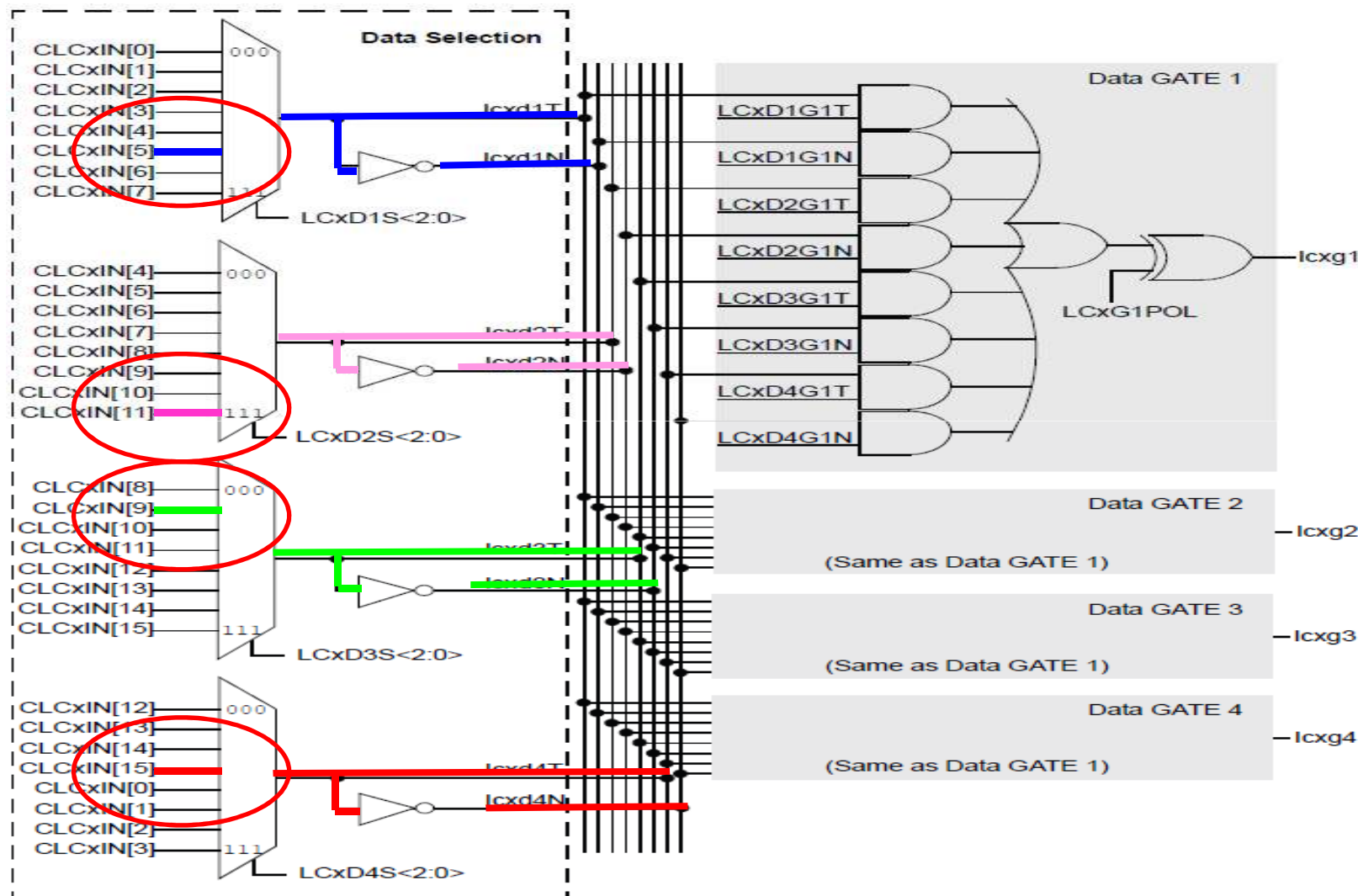


Note: All controls are undefined at power-up.

Configurable Logic Cell


Data Input	lcxd1 D1S	lcxd2 D2S	lcxd3 D3S	lcxd4 D4S	CLC 1	CLC 2	CLC 3	CLC 4
CLCxIN[0]	000	—	—	100	CLC1IN0	CLC2IN0	CLC3IN0	CLC4IN0
CLCxIN[1]	001	—	—	101	CLC1IN1	CLC2IN1	CLC3IN1	CLC4IN1
CLCxIN[2]	010	—	—	110	SYNCC1OUT	SYNCC1OUT	SYNCC1OUT	SYNCC1OUT
CLCxIN[3]	011	—	—	111	SYNCC2OUT	SYNCC2OUT	SYNCC2OUT	SYNCC2OUT
CLCxIN[4]	100	000	—	—	Fosc	Fosc	Fosc	Fosc
CLCxIN[5]	101	001	—	—	TMR0IF	TMR0IF	TMR0IF	TMR0IF
CLCxIN[6]	110	010	—	—	TMR1IF	TMR1IF	TMR1IF	TMR1IF
CLCxIN[7]	111	011	—	—	TMR2 = PR2	TMR2 = PR2	TMR2 = PR2	TMR2 = PR2
CLCxIN[8]	—	100	000	—	lc1_out	lc1_out	lc1_out	lc1_out
CLCxIN[9]	—	101	001	—	lc2_out	lc2_out	lc2_out	lc2_out
CLCxIN[10]	—	110	010	—	lc3_out	lc3_out	lc3_out	lc3_out
CLCxIN[11]	—	111	011	—	lc4_out	lc4_out	lc4_out	lc4_out
CLCxIN[12]	—	—	100	000	NCO1OUT	LFINTOSC	TX (EUSART)	SCK (MSSP)
CLCxIN[13]	—	—	101	001	HFINTOSC	ADFRC	LFINTOSC	SDO (MSSP)
CLCxIN[14]	—	—	110	010	PWM3OUT	PWM1OUT	PWM2OUT	PWM1OUT
CLCxIN[15]	—	—	111	011	PWM4OUT	PWM2OUT	PWM3OUT	PWM4OUT

 


CLC Design Tool

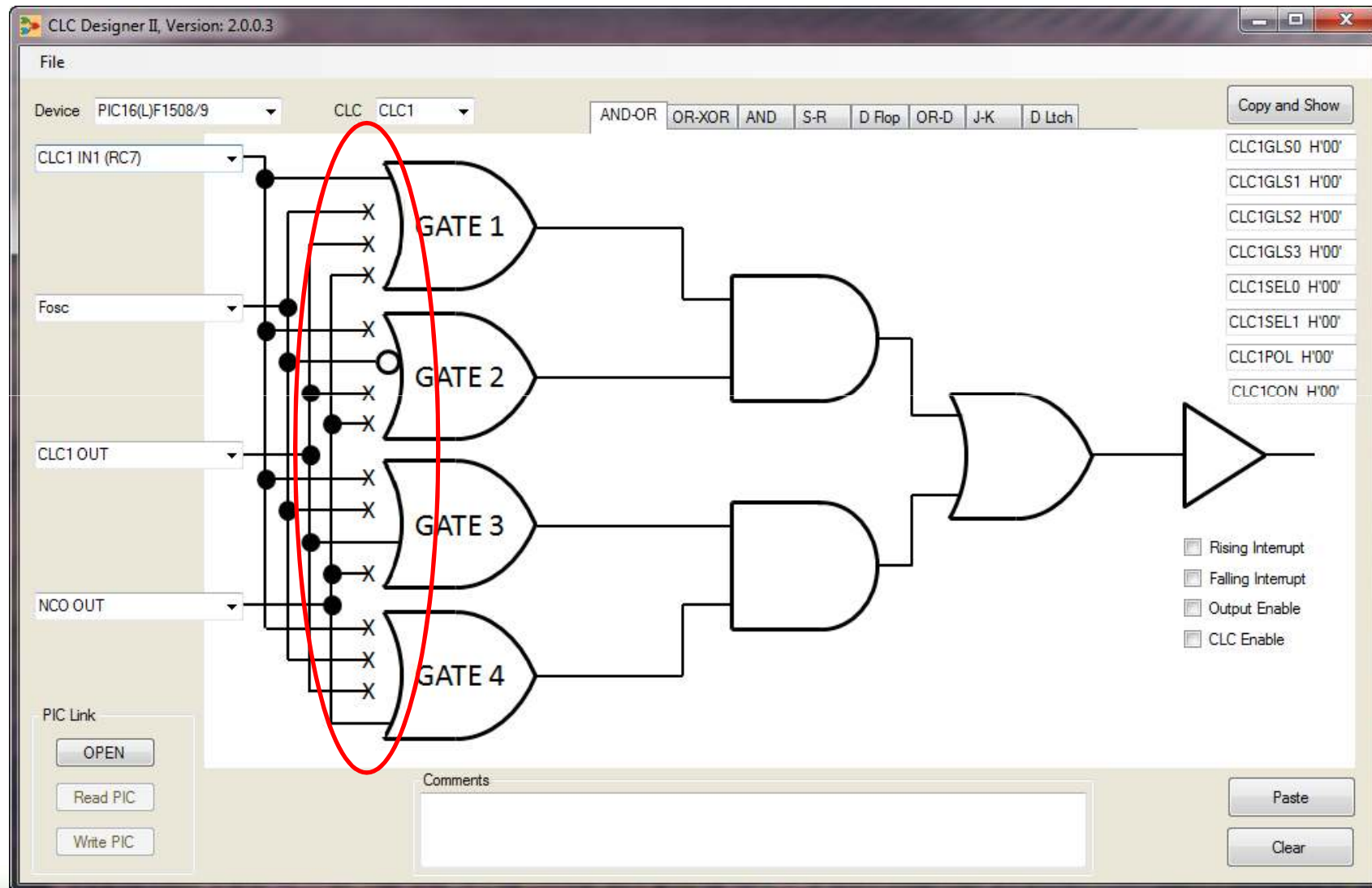

Configurable Logic Cell

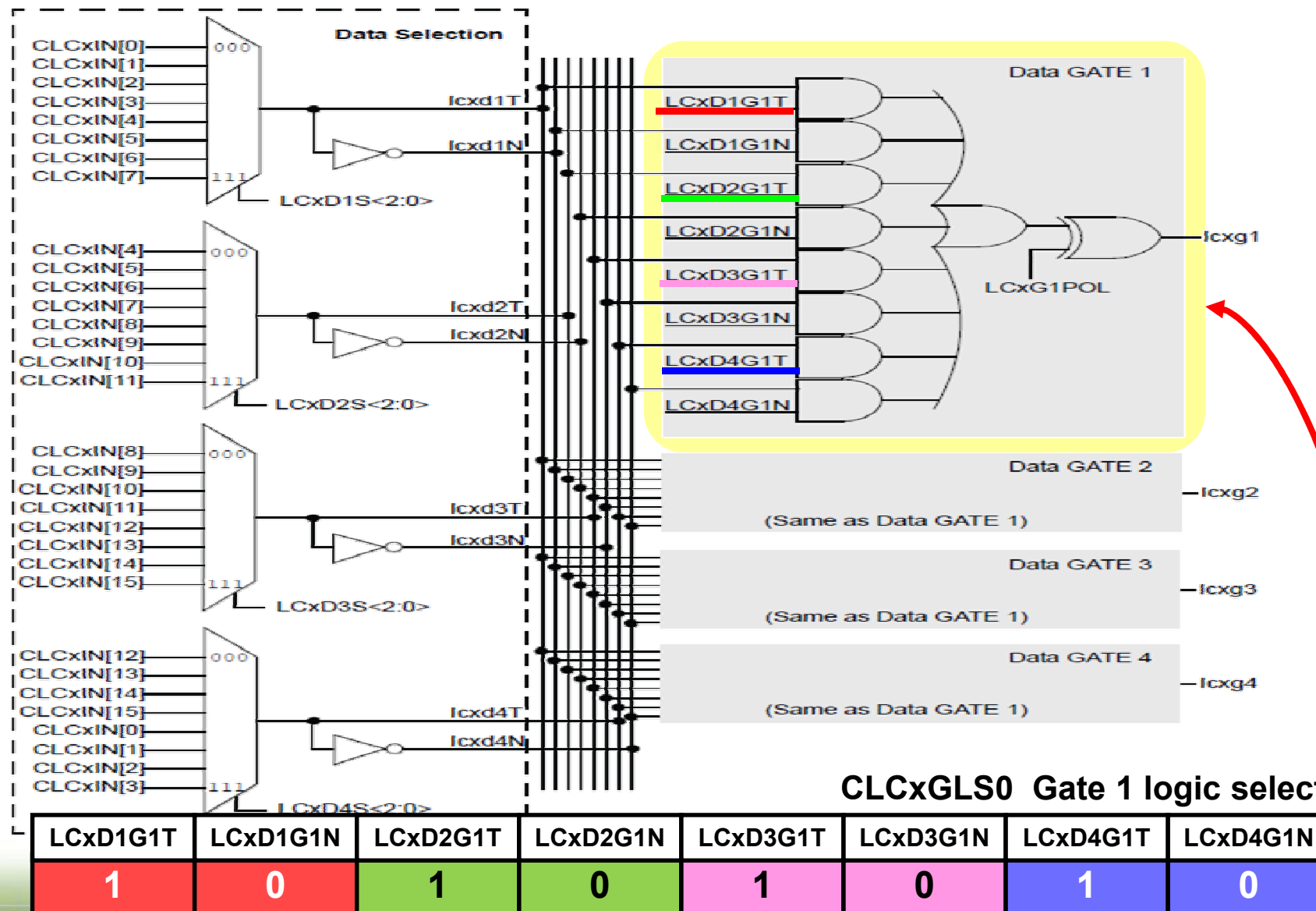

Configurable Logic Cell

 

CLCxGLS0	LCxGyPOL	Gate Logic
0x55	1	AND
0x55	0	NAND
0xAA	1	NOR
0xAA	0	OR
0x00	0	Logic 0
0x00	1	Logic 1

CLCxPOL


LCxPOL	—	—	—	LCxG4POL	LCxG3POL	LCxG2POL	LCxG1POL 0
--------	---	---	---	----------	----------	----------	---------------

CLCxGLS0 Gate 1 logic select


LCxG1D4T 1	LCxG1D4N 0	LCxG1D3T 1	LCxG1D3N 0	LCxG1D2T 1	LCxG1D2N 0	LCxG1D1T 1	LCxG1D1N 0
---------------	---------------	---------------	---------------	---------------	---------------	---------------	---------------

Non-Inverted Inputs (T) Selected

Configurable Logic Cell Peripheral Setup

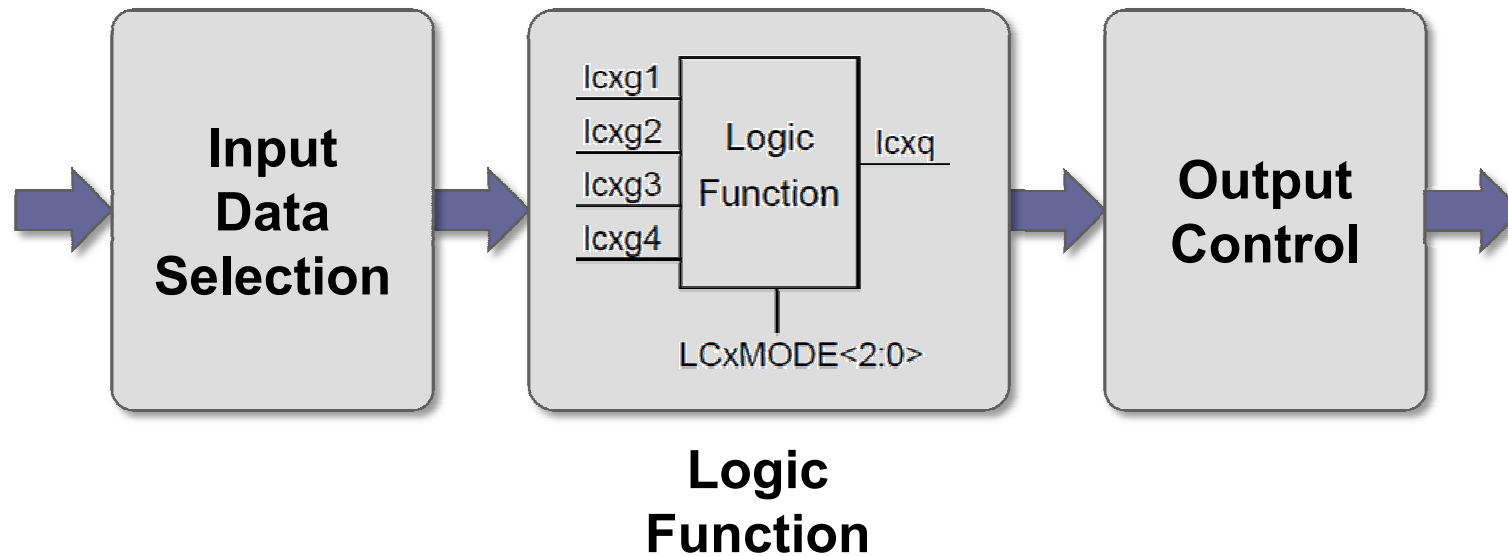

CLC Design Tool

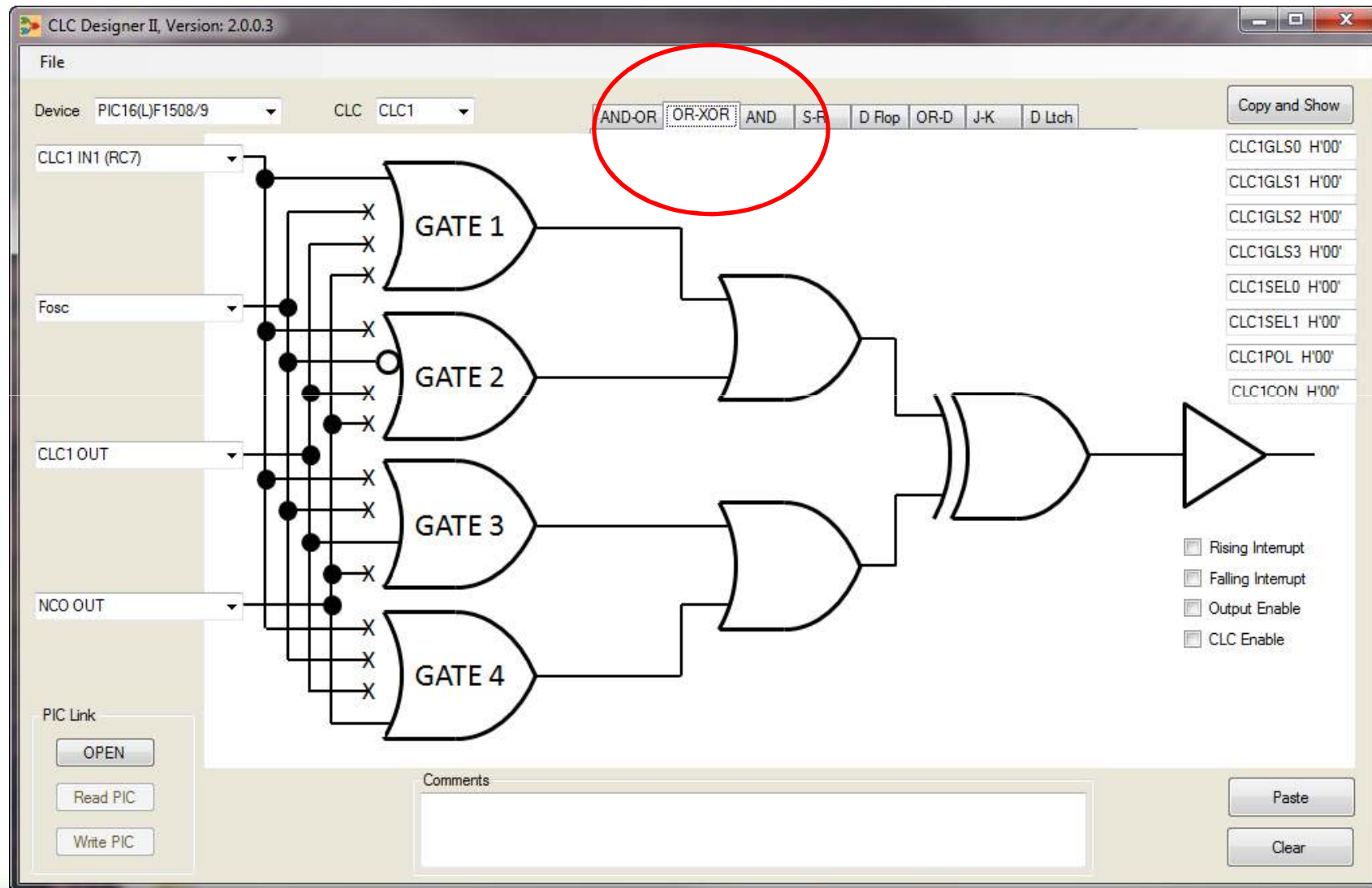


Configurable Logic Cell


Logic Function Selection

Select the desired logic function using the **LCxMODE<2:0>** bits of the **CLCxCON** register.


000 = AND – OR

 


001 = OR – XOR

 

010 = 4-Input AND

 

011 = S-R Latch

 


Configurable Logic Cell


Logic Function Selection

Select the desired logic function using the **LCxMODE<2:0>** bits of the **CLCxCON** register.


100 = 1-Input D Flip-Flop with S and R

 


101 = 2-Input D Flip-Flop with R

 


110 = J-K Flip-Flop with R

 

 
111 = 1-Input Transparent Latch with S and R




Configurable Logic Cell Peripheral Setup

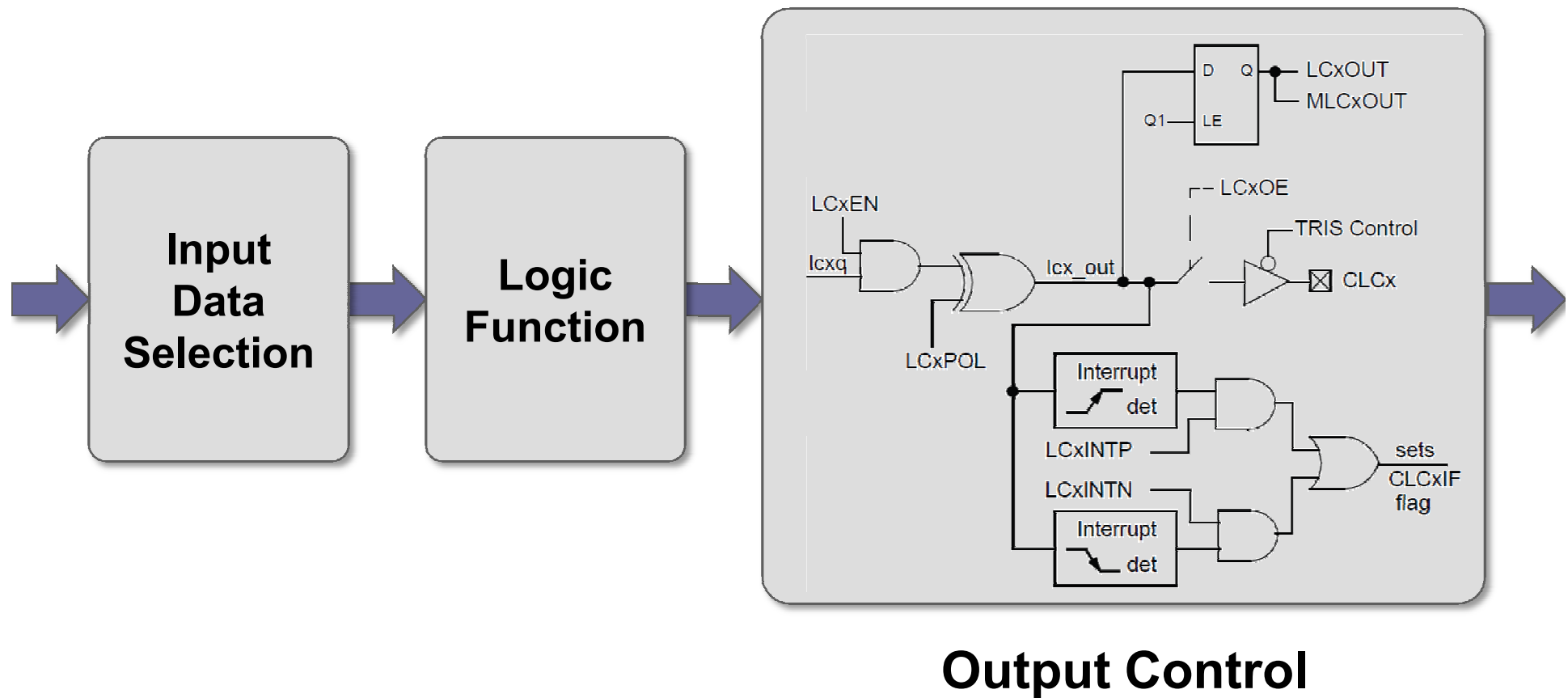

CLC Design Tool

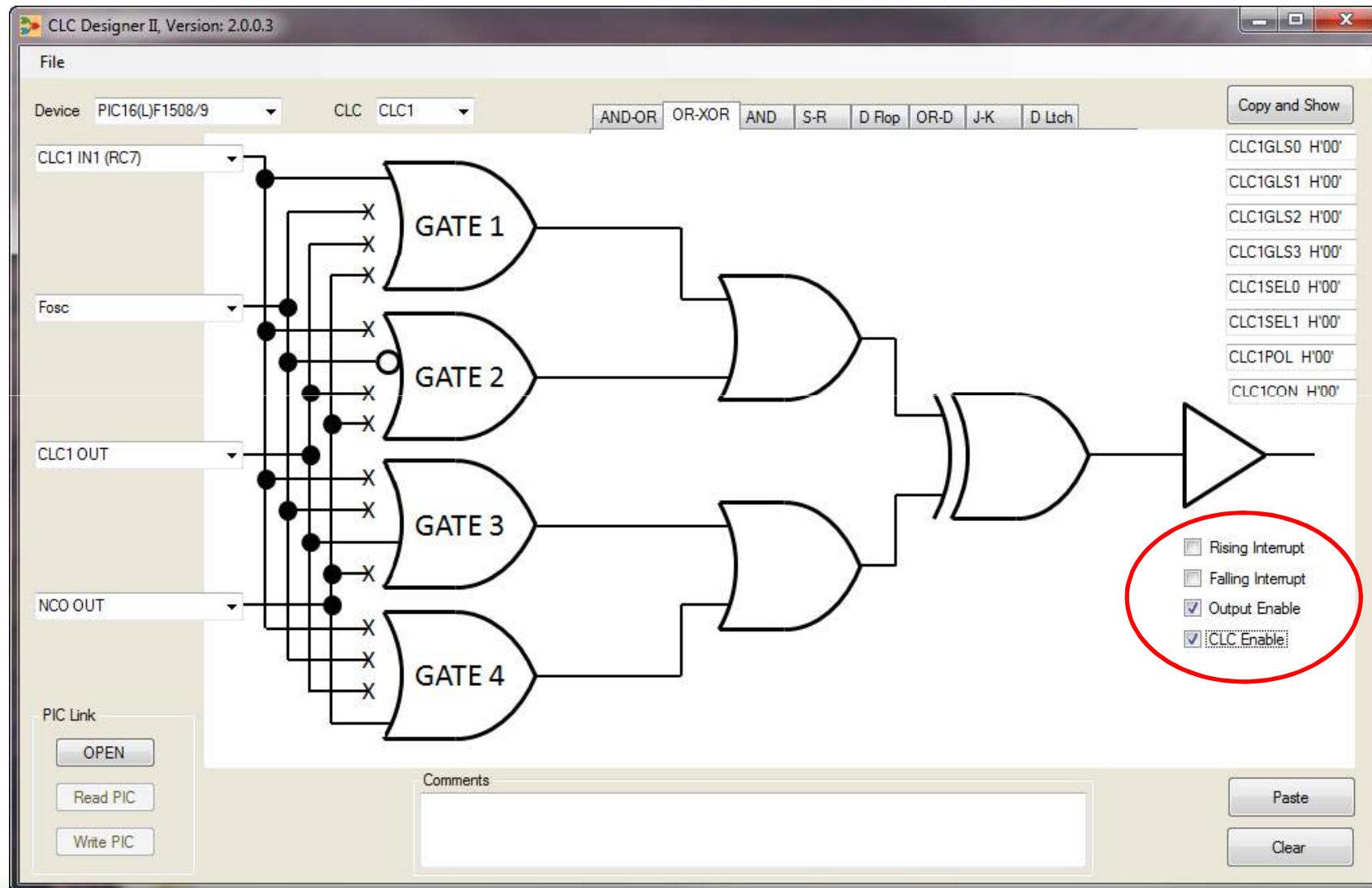

Configurable Logic Cell Output Control

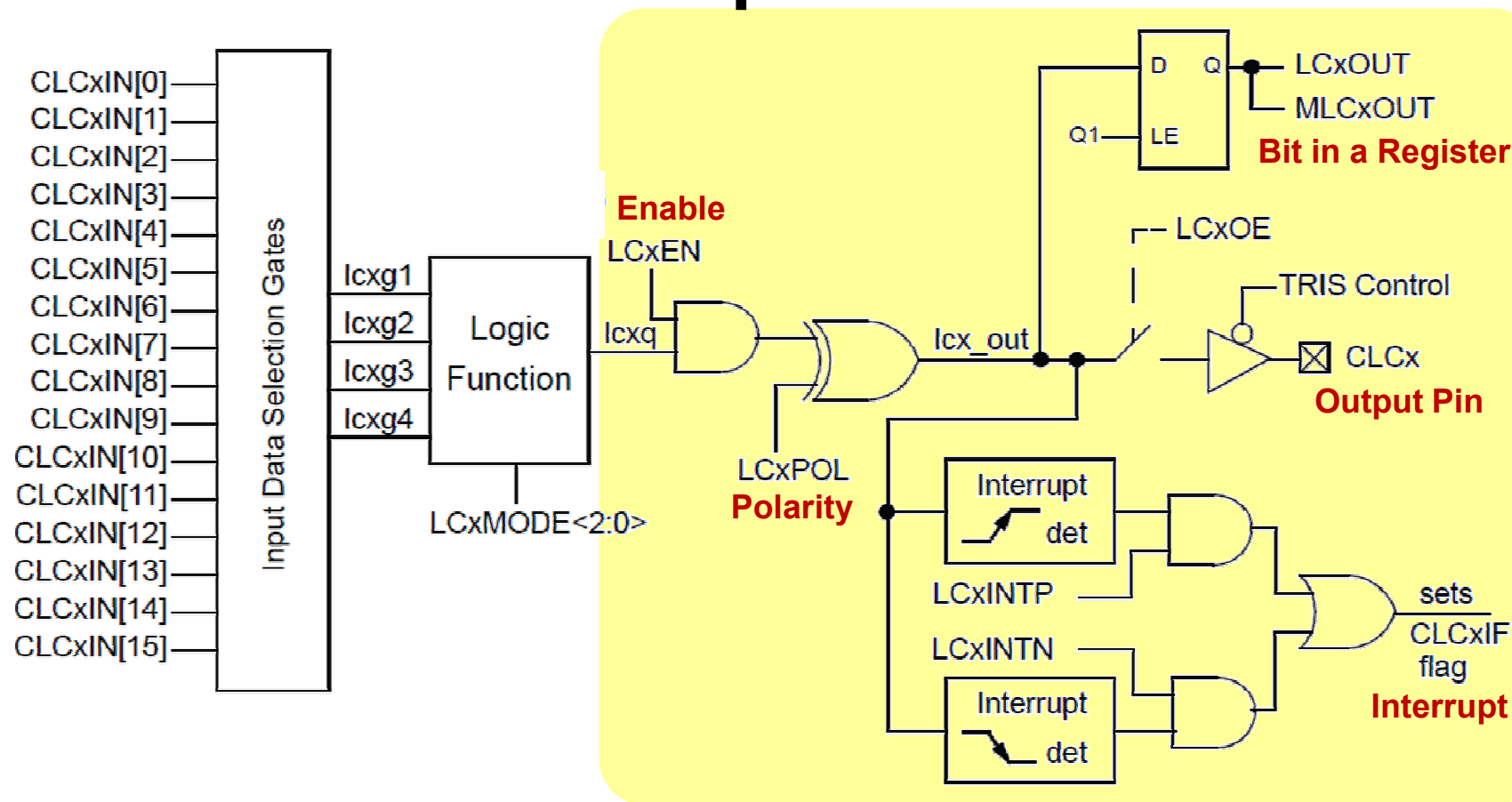

REGISTER 24-1: CLCxCON: CONFIGURABLE LOGIC CELL CONTROL REGISTER


R/W-0/0	R/W-0/0	R-0/0	R/W-0/0	R/W-0/0	R/W-0/0	R/W-0/0	R/W-0/0
LCxEN	LCxOE	LCxOUT	LCxINTP	LCxINTN	LCxMODE<2:0>		
bit 7							bit 0

Application Example: Output Pin Re-Routing


- Route signals without adding additional layers
- Cost effective solution
- Crucial in small form factor applications

Example:

- **RB7 = EUSART transmit pin**
 - Re-route using CLC
 - Signal can be routed to:
RC4, RC0, RA4 & RA2

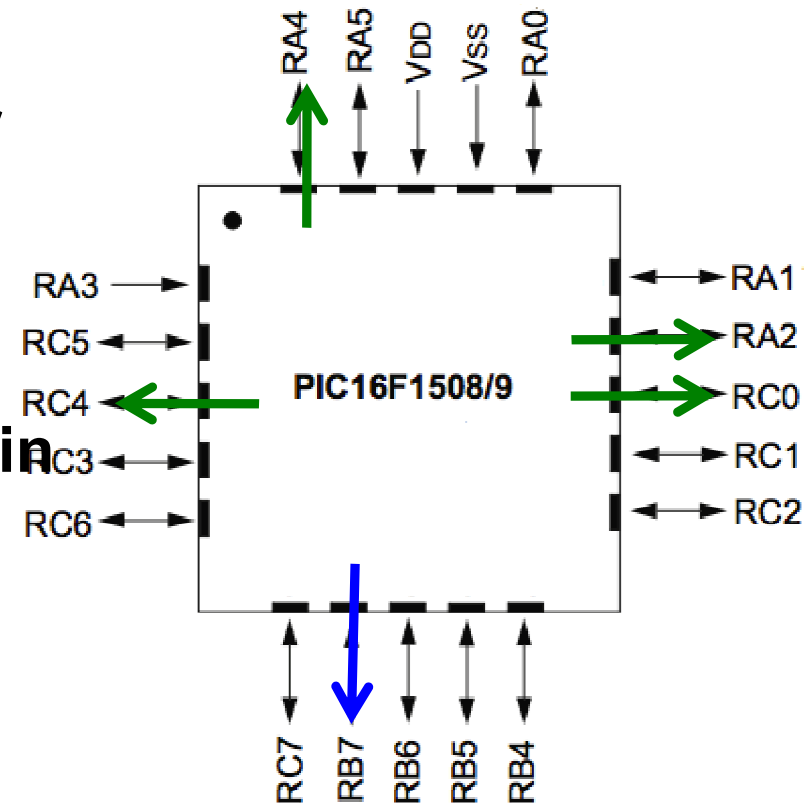

CLC1 -> CLC4 : AND-OR

 


↓
Pulse

↓
CLC1 Out

↓
CLC4 Out

DeltaX = CLC1 Out - Pulse
DeltaX ~ 40nS

CLC1 -> CLC4 : AND-OR

 

Pulse

CLC1 Out

CLC4 Out

$\Delta X = \text{CLC4 Out} - \text{CLC1 Out}$

$\Delta X \approx 16\text{ns}$

$\text{CLC Prop Delay} = 16\text{ns} / 4 = 4\text{ns}$




Lab 1

Manchester Encoder

Lab 1 - Manchester Encoder

What is Manchester Encoding?

Manchester encoding is a method of encoding data by combining the clock and data lines using an exclusive OR into a single signal.

 

Lab 1 - Manchester Encoder


Setup

Use the CLC design tool to build and implement this circuit.

Inputs: SPI Clock, SPI Data

Output: CLC 4 Out (RC4)

CLC 4

 


Note:

- Make sure POT 2 is turned all the way clockwise!
- “S3” sends your message, not “S2”
- Open main.c and edit line 167 to send a custom Message!

Lab 1 - Manchester Encoder

Use CLC4

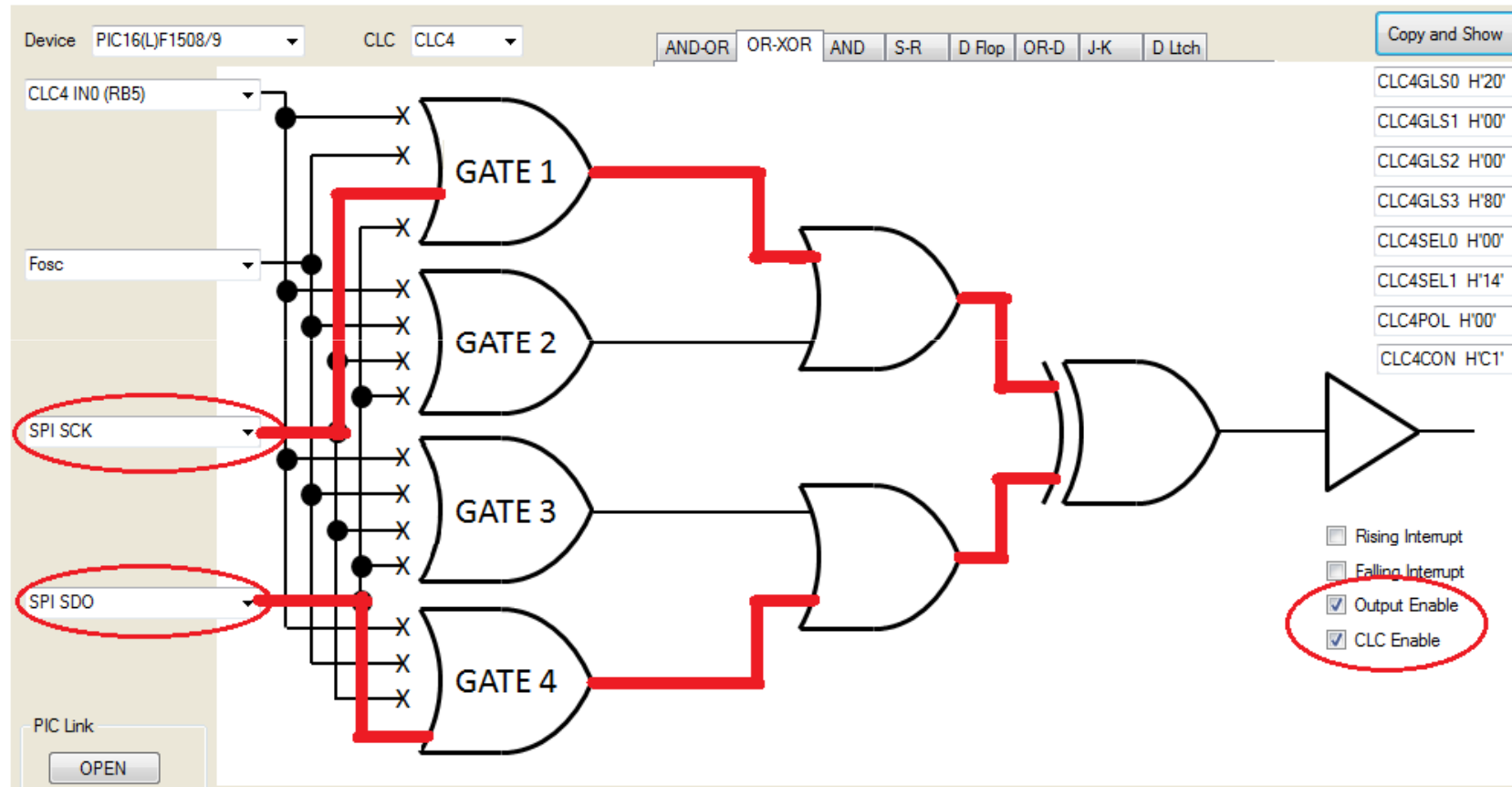

- Make sure POT 1 is turned all the way clockwise!
- “S3” sends your message, not “S2”
- Save as “lab1.inc” in: C:\MASTERS\1610\Manchester Encoder.X\src



Numerically Controlled Oscillator (NCO)

Numerically Controlled Oscillator

What does it do?

Provides an adjustable output frequency pulse based on an input clock and increment value that with true linear frequency control and increased frequency resolution over standard PWM.

NCO Features

- **Two modes of operation**
 - Fixed 50% duty cycle (FDC)
 - **500 KHz max output**
 - Pulse Frequency Modulation (PFM)
 - **1MHz max output**

Numerically Controlled Oscillator

Pulse Frequency Mode

f_{max} = 1MHz

$$f_{NCO} = \left(\frac{f_{CLK}}{\text{Accumulator}} \right) \left(\text{Increment value} \right)$$

(Constant)

Fixed Duty Cycle Mode


f_{max} = 500KHz

$$f_{NCO} = \left(\frac{f_{CLK}}{2 * \text{Accumulator}} \right) \left(\text{Increment value} \right)$$

(Constant)

Accumulator = 20-bit
Increment value = 16-bit

Numerically Controlled Oscillator

 


Increment value = $2^{16} = 0 \rightarrow 65,535$

$$F_{NCO} = \left(\frac{F_{osc}}{\text{Accumulator}} \right) \left(\text{Increment value} \right)$$

Increment value \uparrow , $F_{NCO} \uparrow$

Linear change in NCO Frequency.

 


PR2 = $2^8 = 0 \rightarrow 255$

$$F_{PWM} = \left(\frac{F_{osc}}{4 (PR2 + 1)} \right)$$


PR2 \uparrow , $F_{osc} \downarrow$

Nonlinear change in PWM Frequency.


Numerically Controlled Oscillator

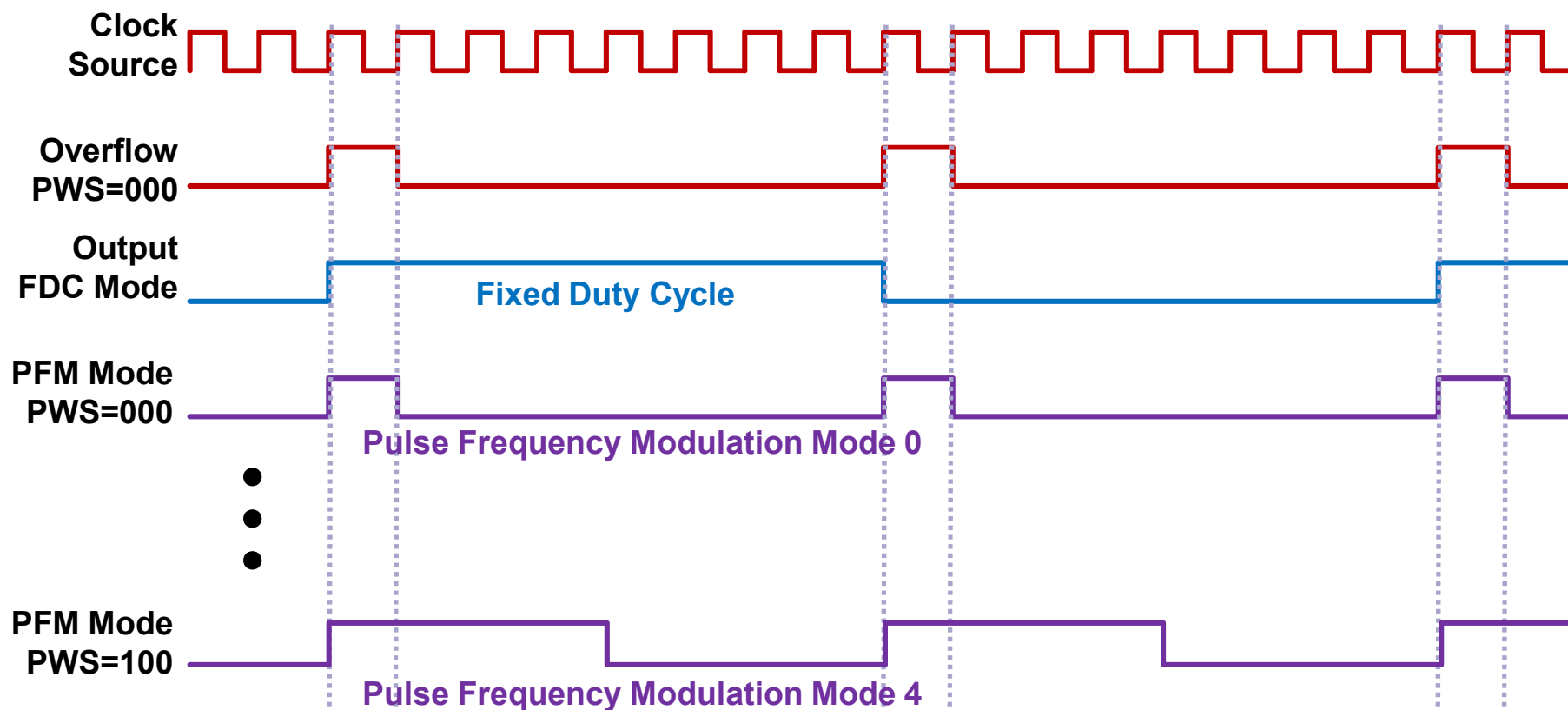


Numerically Controlled Oscillator

 

Numerically Controlled Oscillator

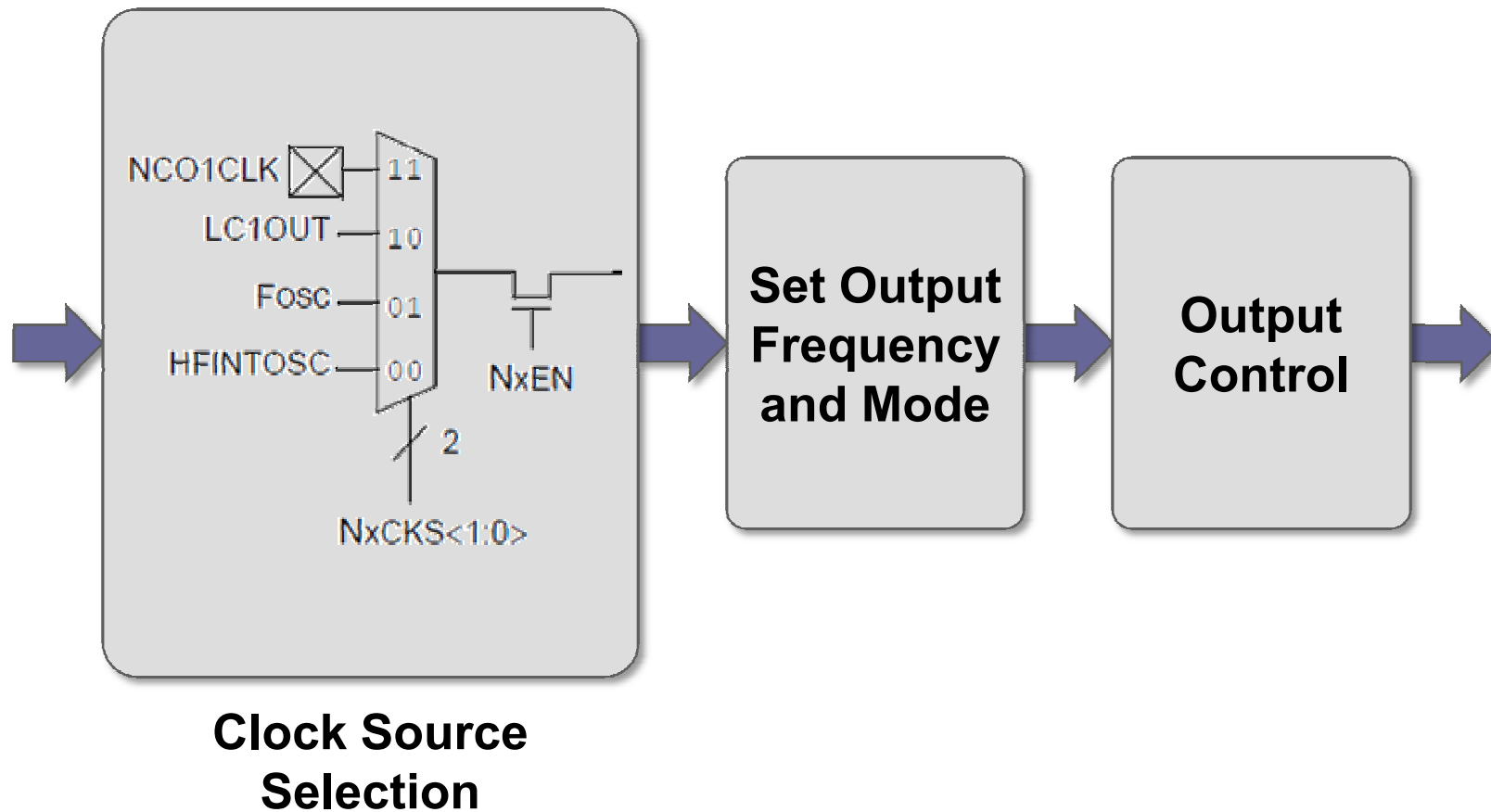


Clock Source Selection

 

NCOxCLK Register


NxPWS<2:0>	-	-	-	NxCKS<1:0>
------------	---	---	---	------------

Numerically Controlled Oscillator

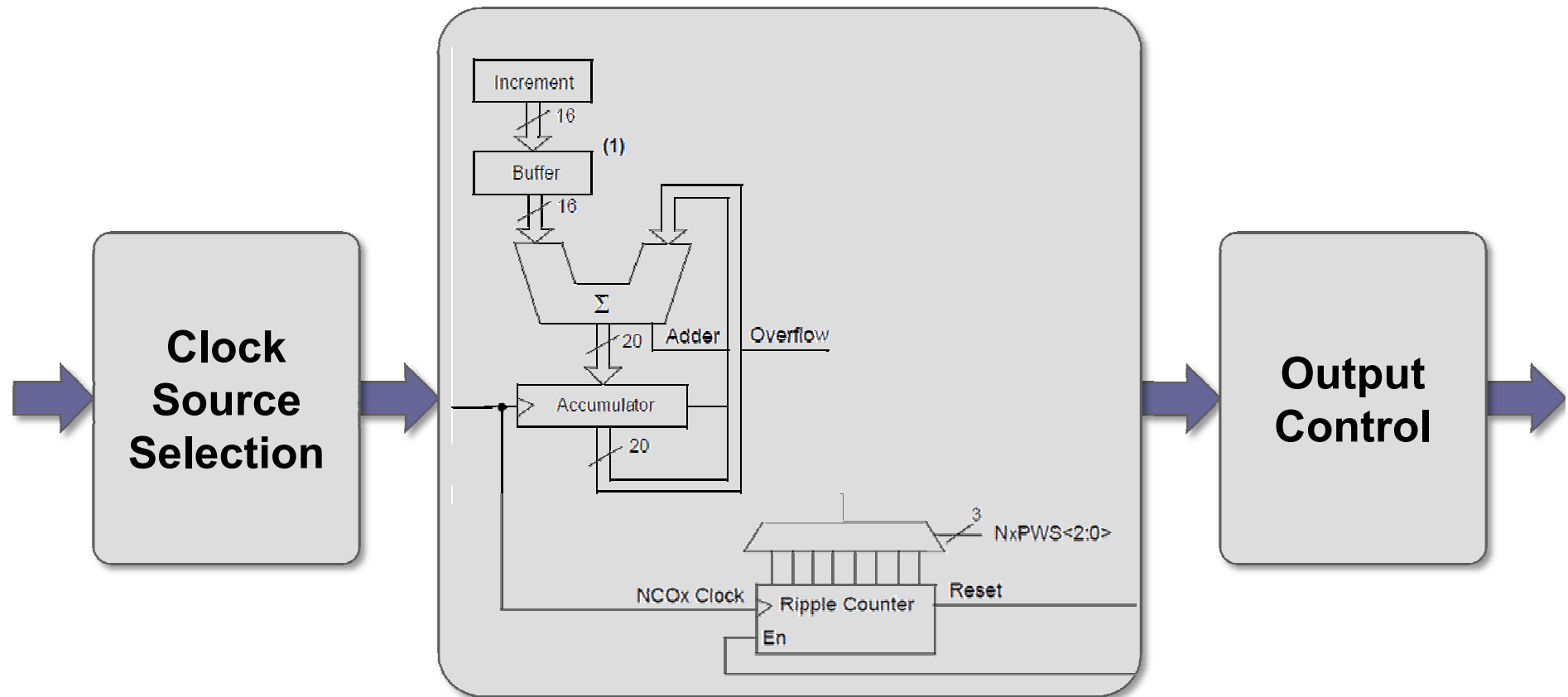

Set Output Frequency and Mode

Mode & Frequency

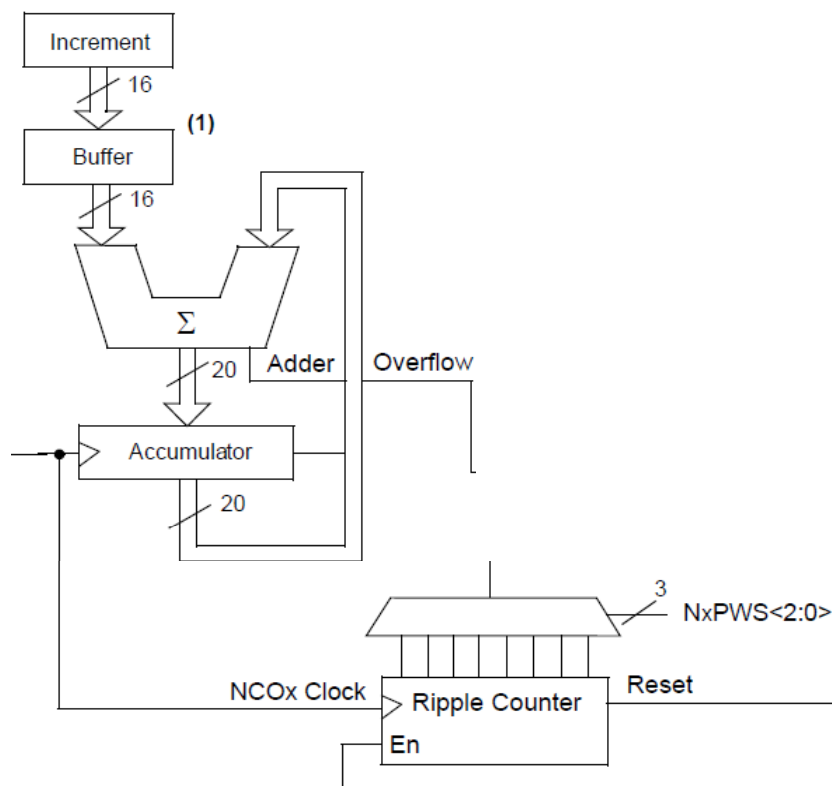

NCOxCLK Register

NxPWS<2:0>	-	-	-	NxCKS<1:0>
------------	---	---	---	------------


NCOxINCH Register

Increment <15:8>


NCOxINCL Register

Increment <7:0>

Numerically Controlled Oscillator

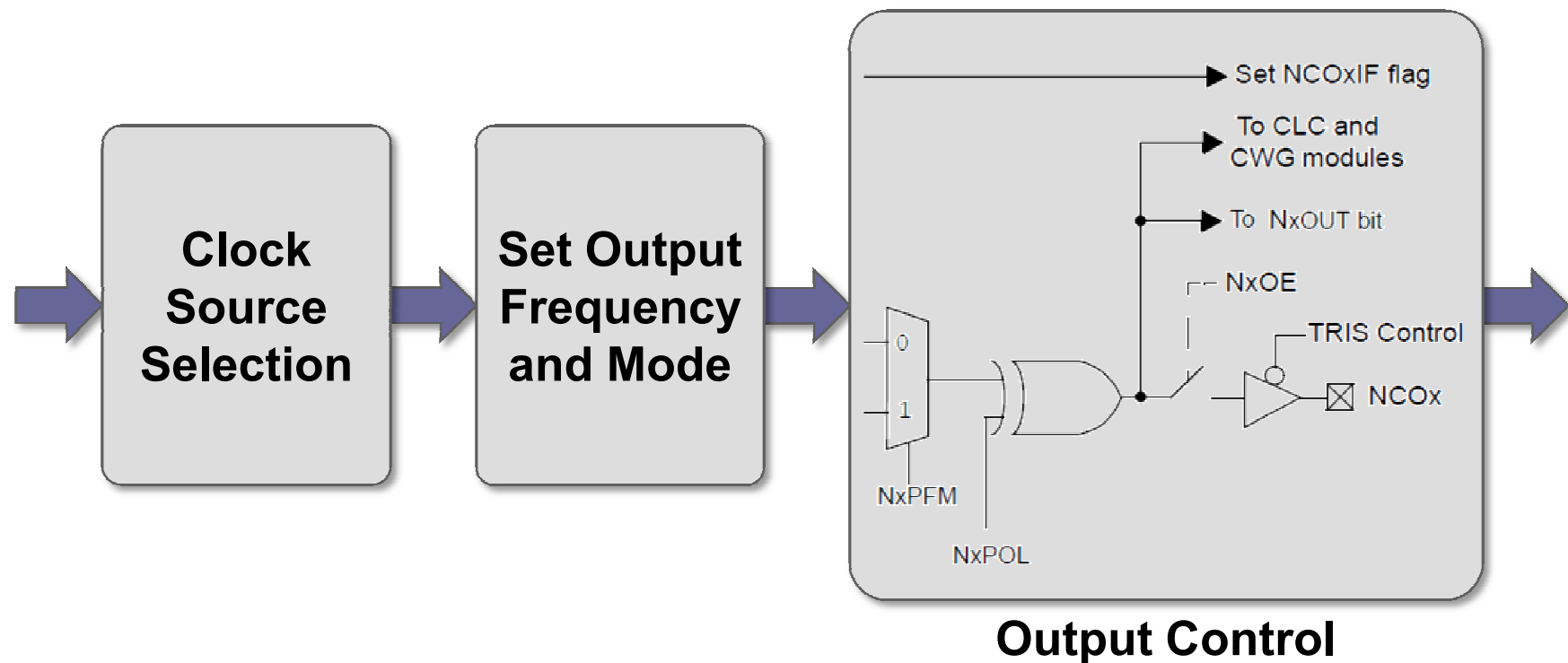

Output Control

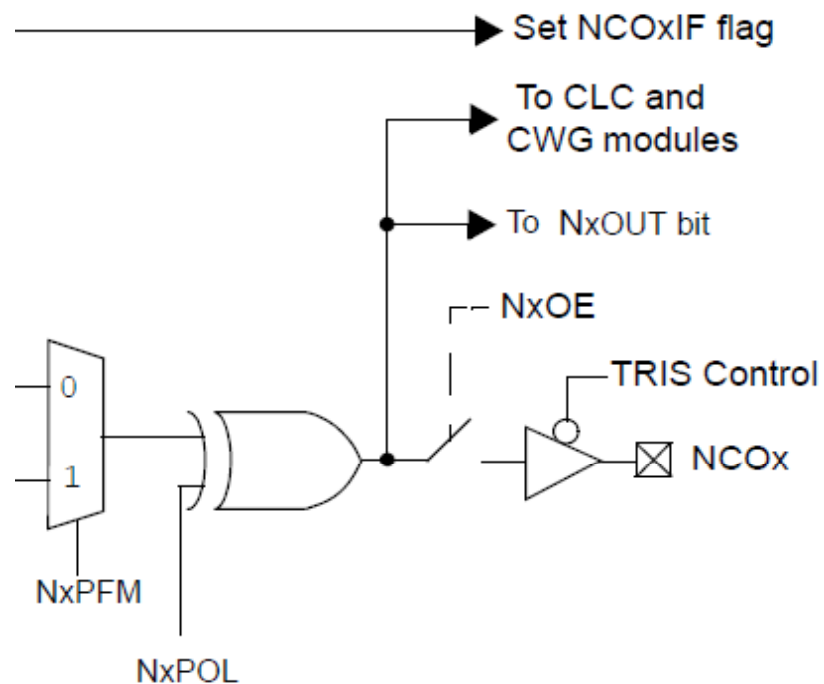

NCOxCON Register

NxEN	NxOE	NxOUT	NxPOL	-	-	-	NxPFM
------	------	-------	-------	---	---	---	-------

NCO Controlled PWM

How does it work?


- The NCO can produce some pulses that are 1 clock period smaller than the regular pulse.
- By this averaging (dithering/spreading), the NCO period increments achievable are much smaller than one CPU clock.
- If we pulse 3 clocks wide, but every second pulse is one system clock shorter the average pulse width would be exactly $2\frac{1}{2} T_{SYS}$, an increment of less than 1 clock period
- By using this period for timing the PWM pulse width we can adjust it by increments effectively much smaller than the CPU clock (on Average)



Lab 2

Manchester Decoder

Lab 2 - Manchester Decoder

 

Lab 2 - Manchester Decoder


NCO Timing

If we synchronize our signal on the middle transition then we must use NCO in pulse frequency mode to generate an overflow at $\frac{3}{4}$ bit time to best capture the correct data.

$$F_{\text{overflow}} = \frac{\text{NCO Clock Frequency} * \text{Increment Value}}{2^n}$$

n = accumulator width in bits

Manchester Signal

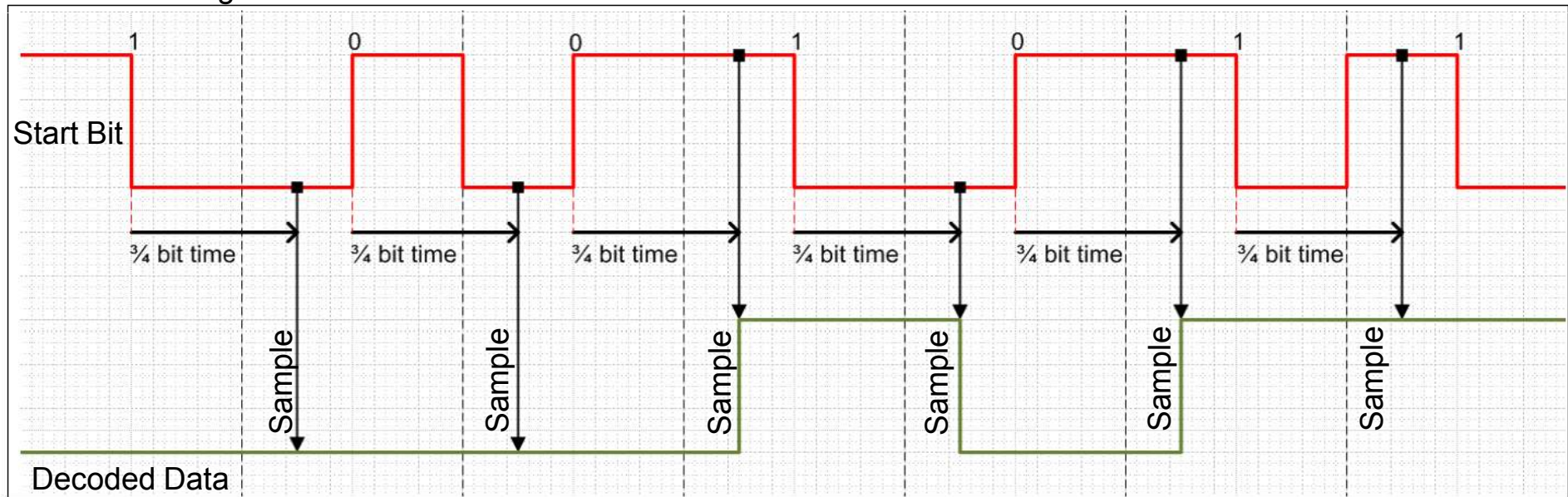

Lab 2 - Manchester Decoder

NCO Timing

The Manchester signal is running at 25 kHz, which gives us a 40 us cycle time

$\frac{3}{4}$ of that is 30 us, which is 33.33 kHz.

Plugging it in to our equation gives us:


$$F_{\text{overflow}} = \frac{\text{NCO Clock Frequency} * \text{Increment Value}}{2^n} = \frac{16 \text{ MHz}(\text{Internal Clock } F_{\text{osc}}) * \text{Increment Value}}{2^{20}}$$

n = accumulator width in bits


$$30\text{us pulse} = 33.33 \text{ kHz} = \frac{16 \text{ MHz} * \text{Increment Value}}{2^{20}} \Rightarrow \text{Increment Value} = 2184 = 0x0888$$

NCO Increment = 0x0888


Lab 2 - Manchester Decoder

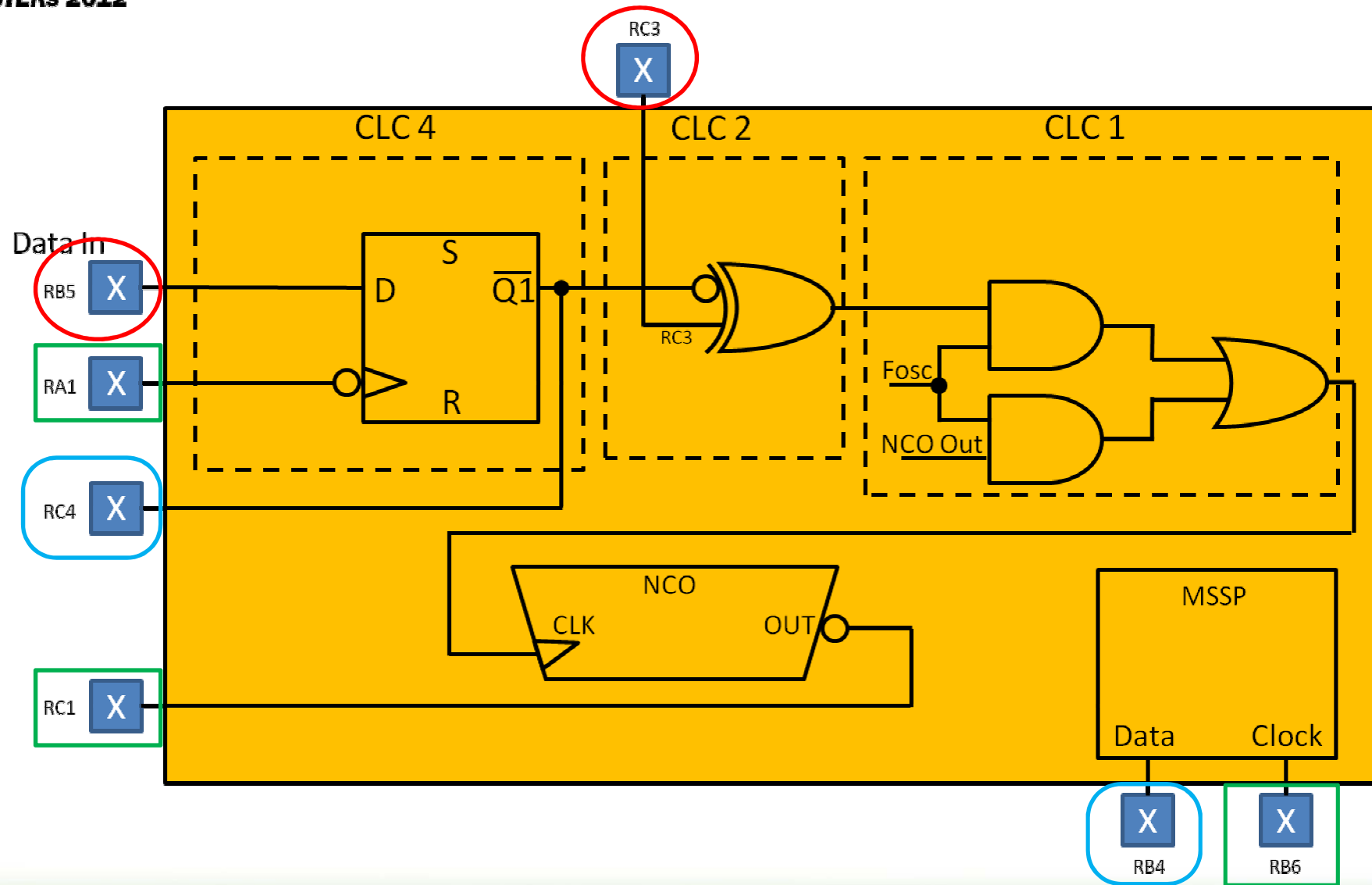


Lab 2 - Manchester Decoder

 


This stage captures the incoming encoded data and samples it every $\frac{3}{4}$ bit time to produce the decoded data

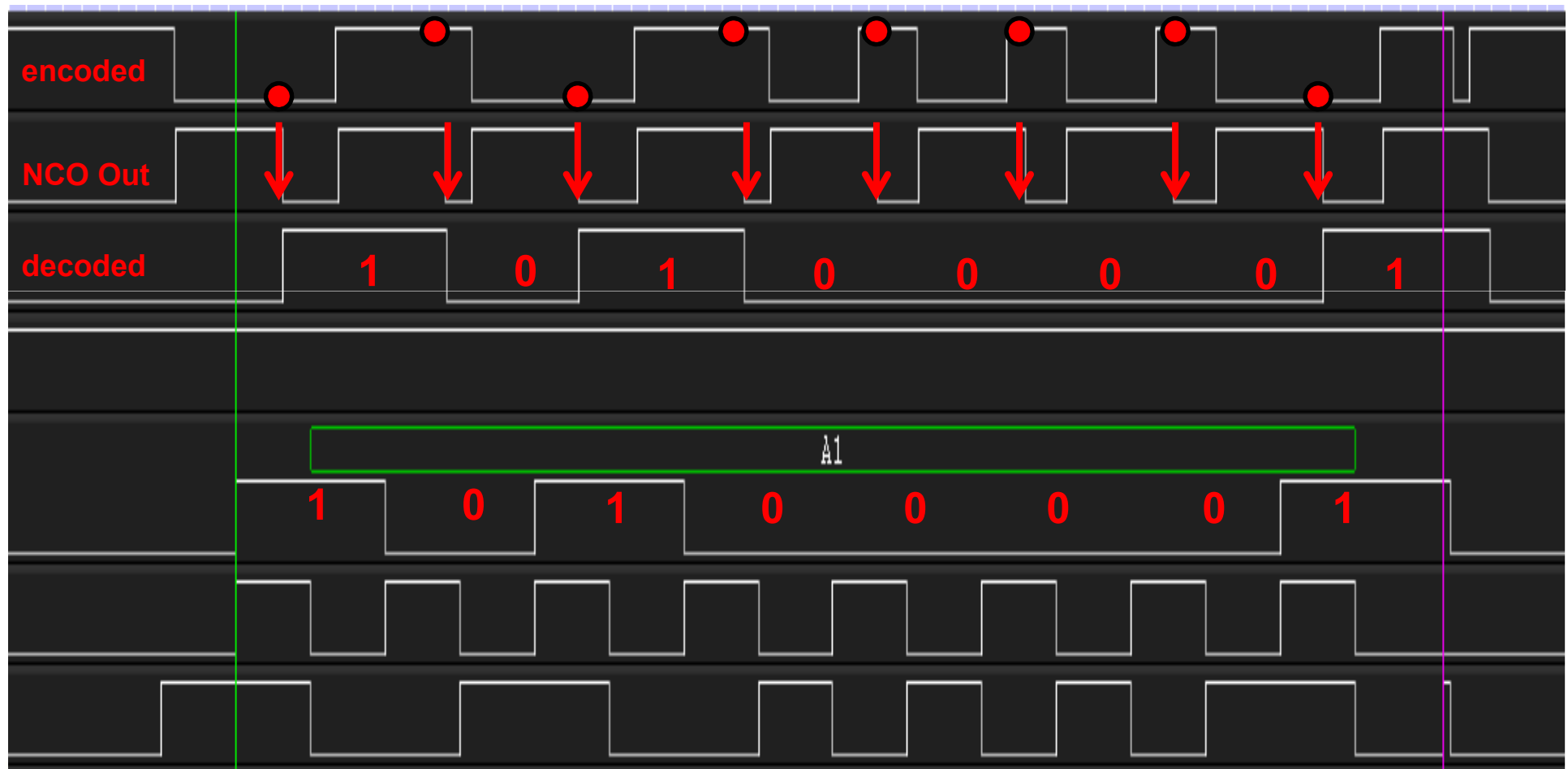


Lab 2 - Manchester Decoder

 


This stage ensures that every encoded mid-bit transition produces a rising edge for the next stage (Synchronization)

 

Lab 2 - Manchester Decoder

 

This stage takes the previous rising edge and starts clocking the NCO. It also ensures that the NCO continues clocking until it overflows if the input to this stage goes to zero

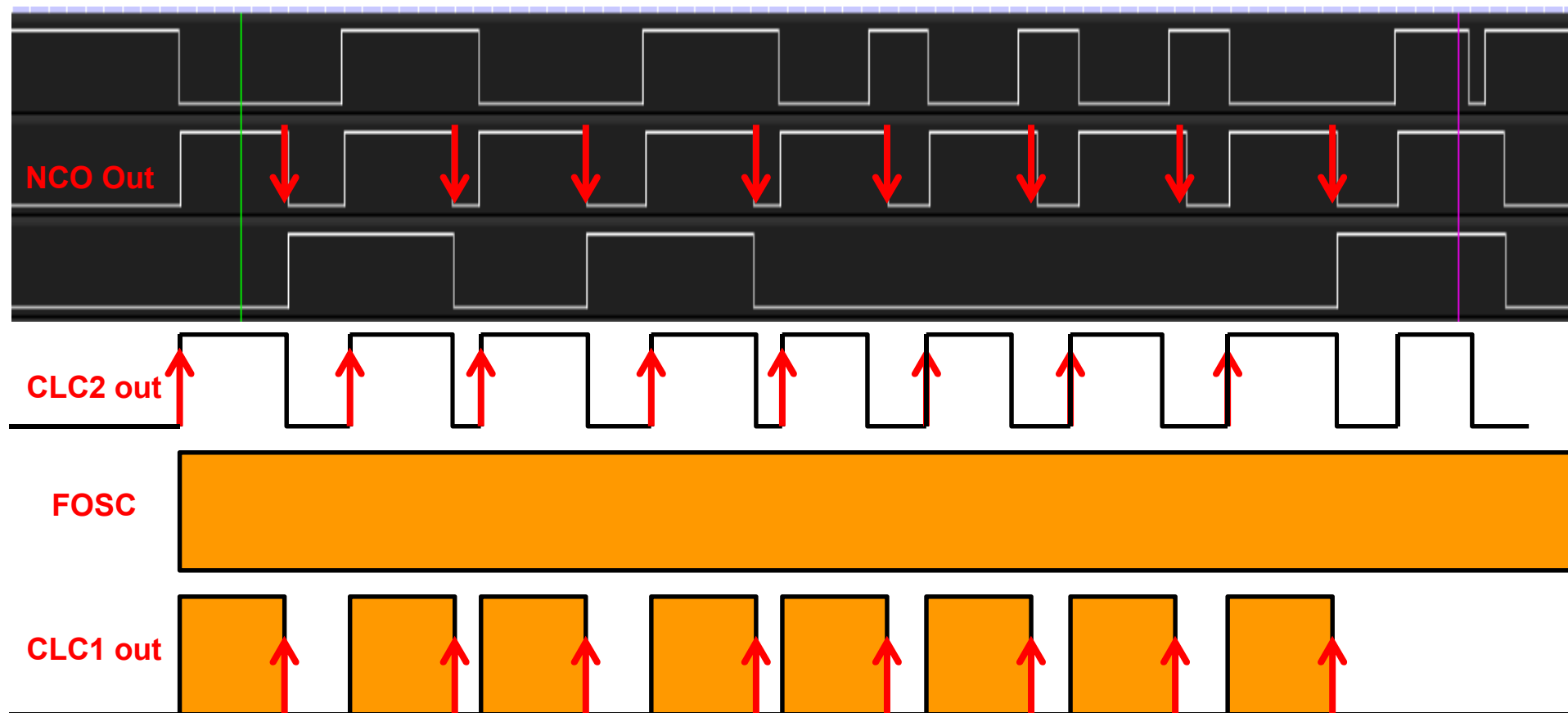


Lab 2 - Manchester Decoder



This stage generates the $\frac{3}{4}$ bit time to create the clock. Combined with the previous stage, it also keeps the input clock present until the output goes low (overflow)

Lab 2 - Manchester Decoder

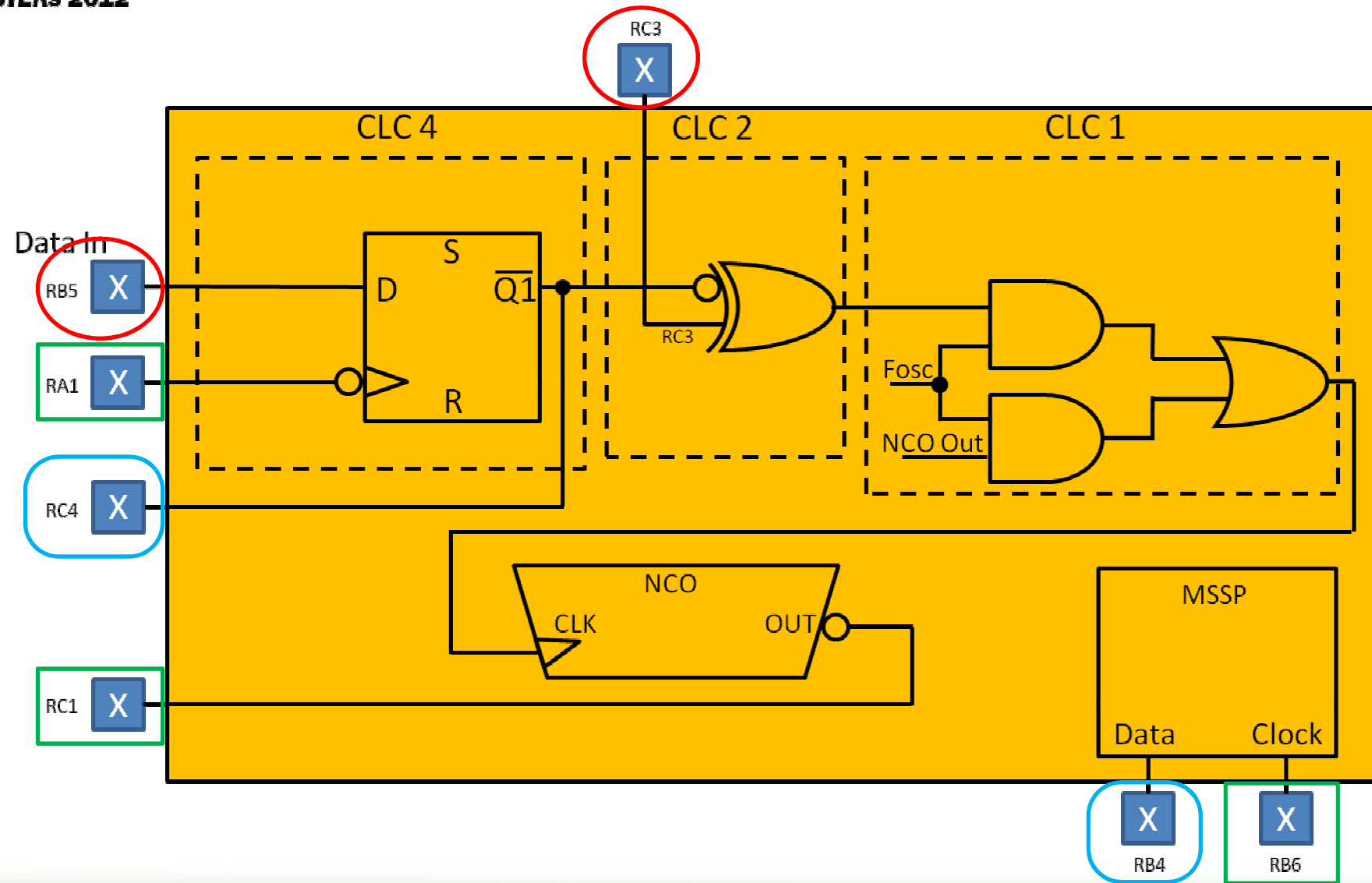




Complementary Waveform Generator (CWG)


Complementary Waveform Generator

What does it do?

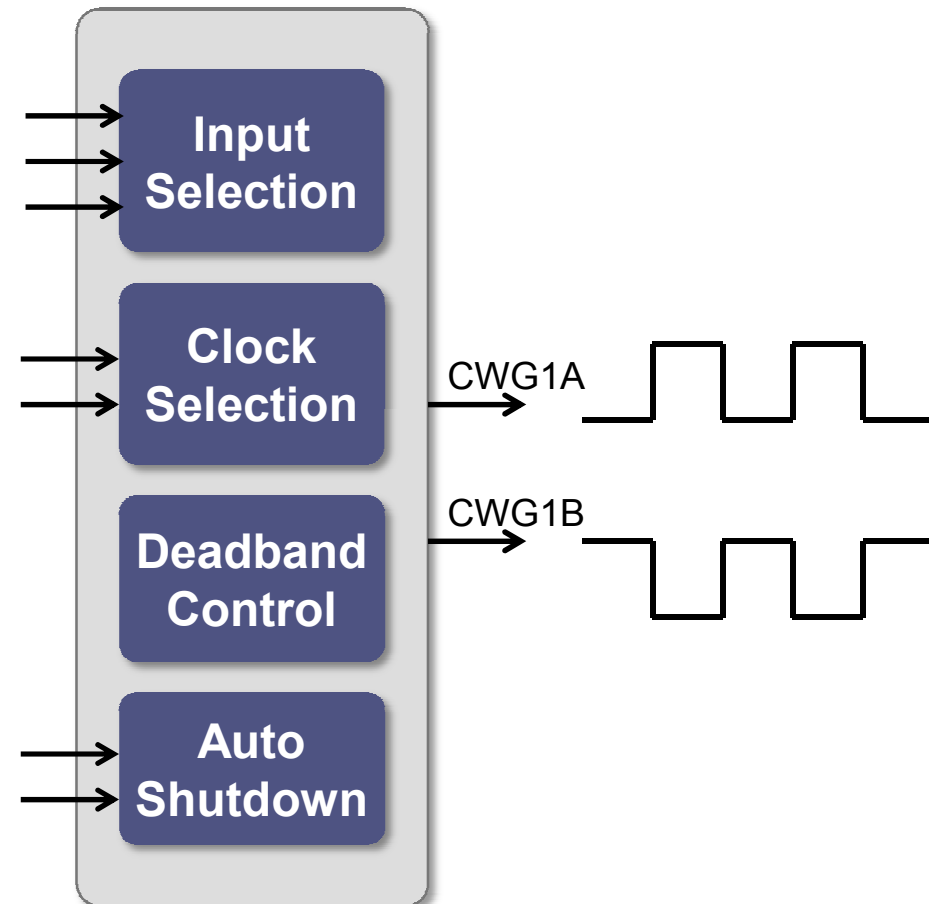generates a complementary waveform with dead-band delay and auto-shutdown capabilities from a selection of input sources.





Input Selection

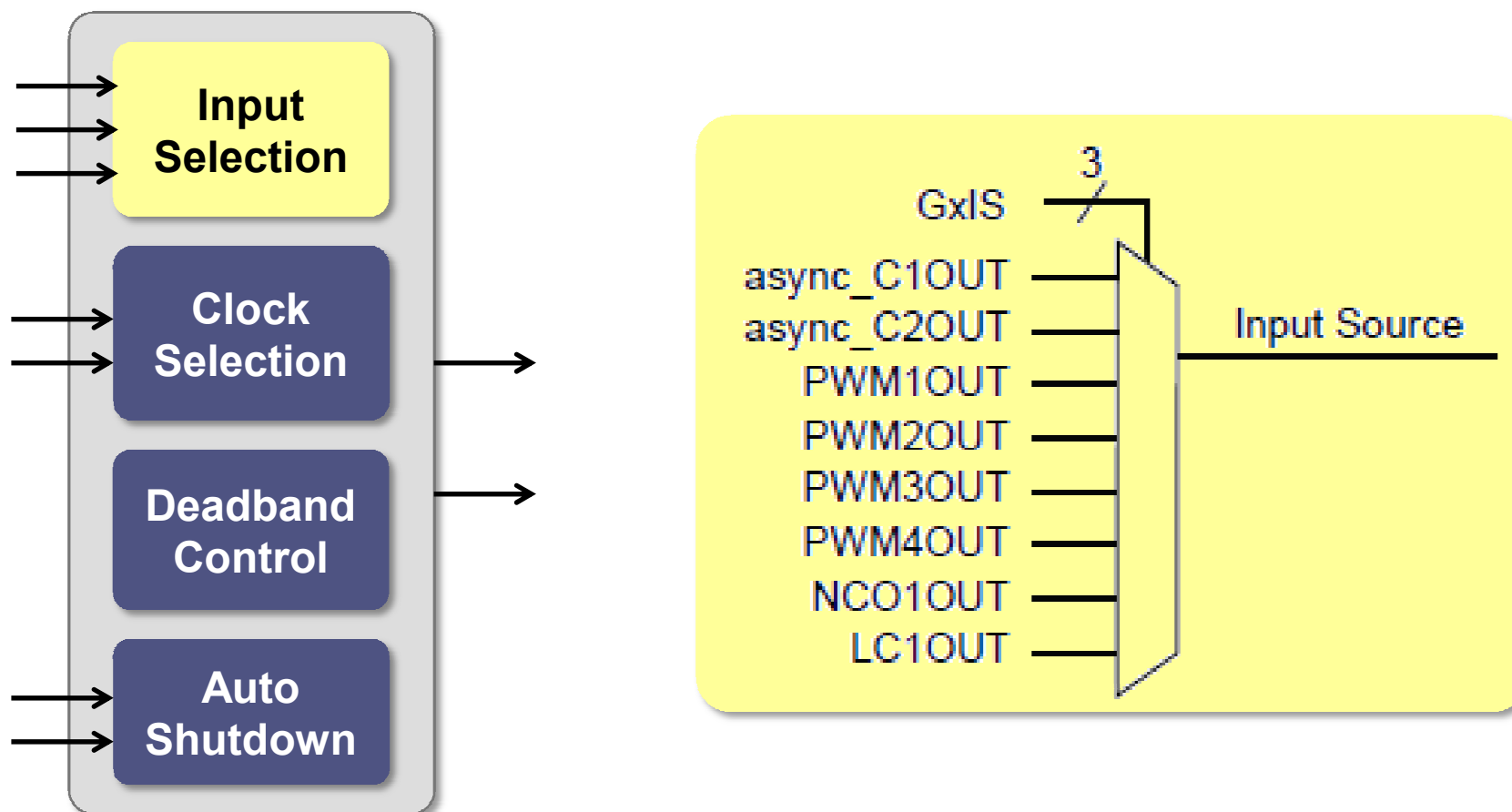

CWGxCON1 Register

GxASDLB<1:0>	GxADSLA<1:0>	-	GxIS2	GxIS1	GxIS0
--------------	--------------	---	-------	-------	-------


Clock Selection

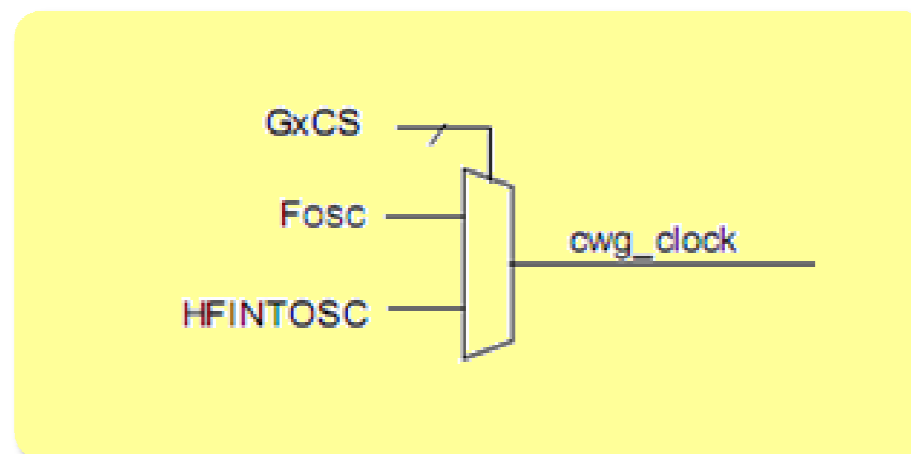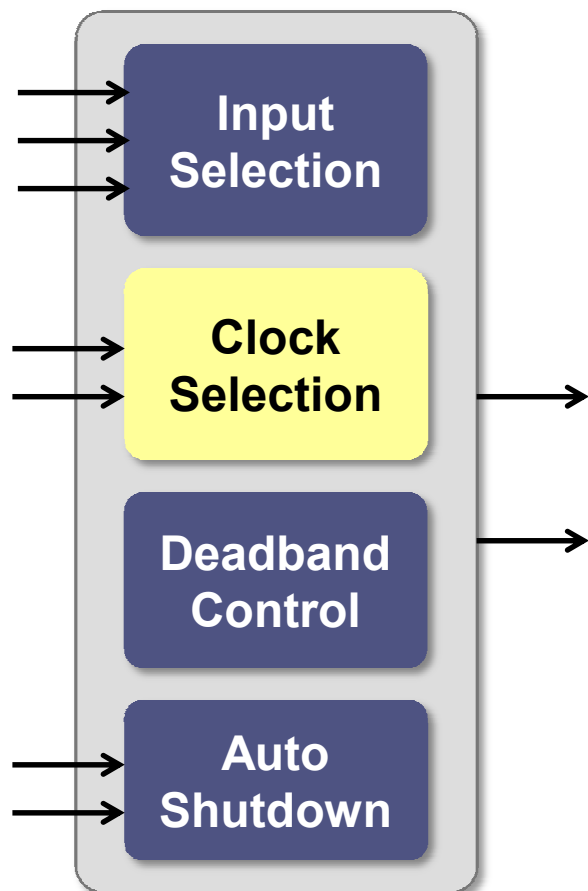

CWGxCON0 Register

GxEN	GxOEB	GxOEA	GxPOLB	GxPOLA	-	-	GxCS
------	-------	-------	--------	--------	---	---	------

Clock Selection

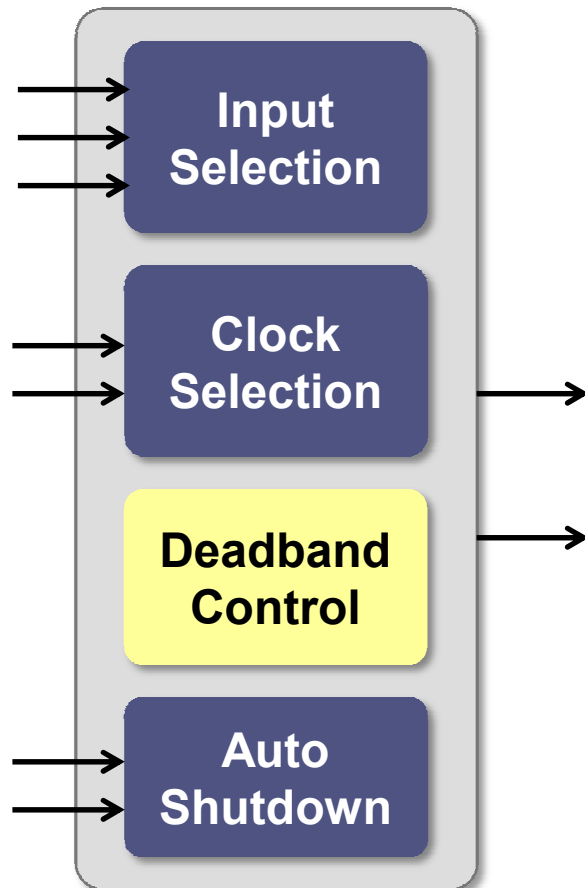

What does Dead-Band Control do?


It provides for non-overlapping output signals to prevent shoot-through current in power switches.

- Two 6-bit counters (64 counts of delay)
- Configurable for rising or falling edge of input source


CWGxDBR and CWGxDBF Registers

-	-	CWGxDBR<5:0> or CWGxDBF<5:0>
---	---	------------------------------

Complementary Waveform Generator

 

Auto Shutdown

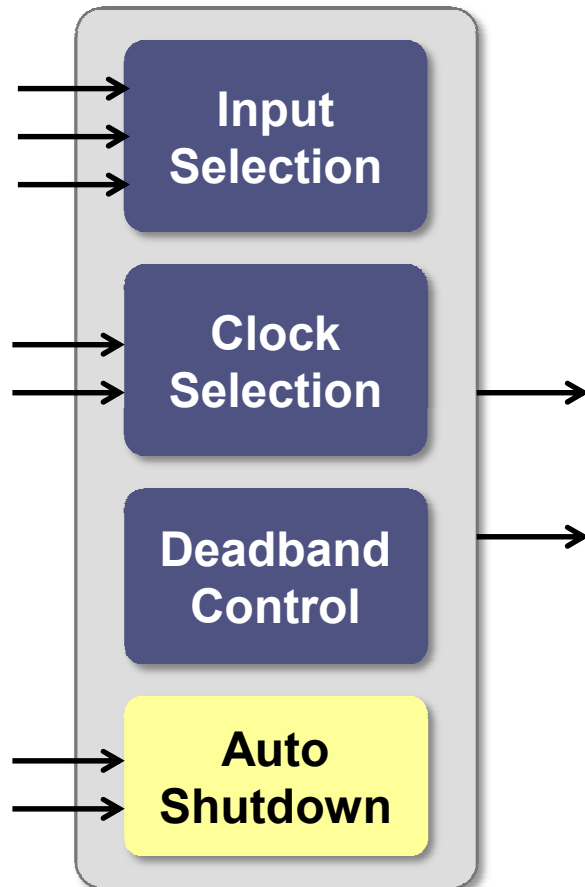

What does Auto-Shutdown Control do?

Forces an immediate override of the CWG outputs allowing a safe shutdown of external circuitry.

Complementary Waveform Generator

Selectable shutdown conditions:

- Software generated
- External input pin (CWG1FLT ► **GxASDFLT**)
- Output of CLC (LC1OUT ► **GxASDCLC2**)

The shutdown state can be cleared automatically or held until cleared by software.


- **GxARSEN** Enables automatic hardware restart
- **GxASE** indicates if shutdown has occurred

CWGxCON2 Register

GxASE	GxARSEN	-	-	-	-	GxASDFLT	GxASDCLC2
--------------	----------------	---	---	---	---	-----------------	------------------


Complementary Waveform Generator

Auto-Shutdown using Auto-Restart

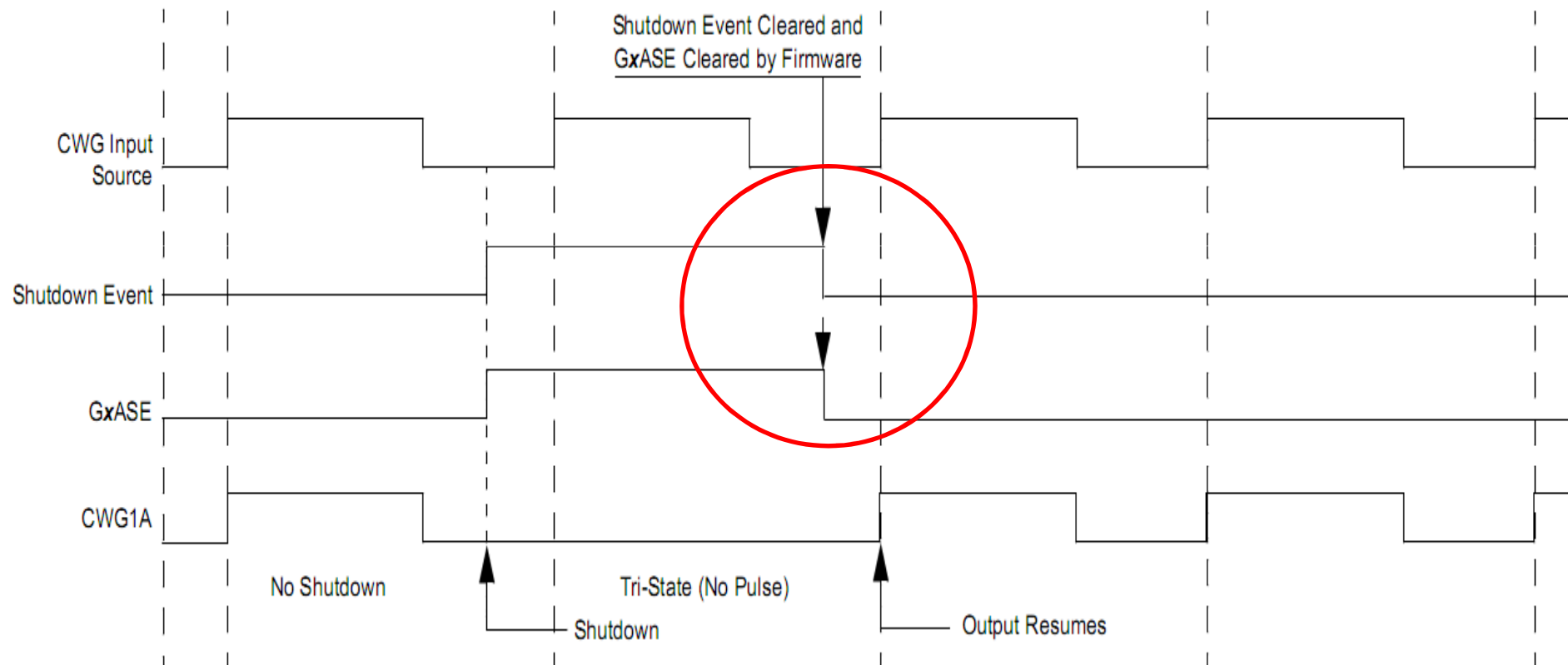

Complementary Waveform Generator


Auto-Shutdown without using Auto-Restart

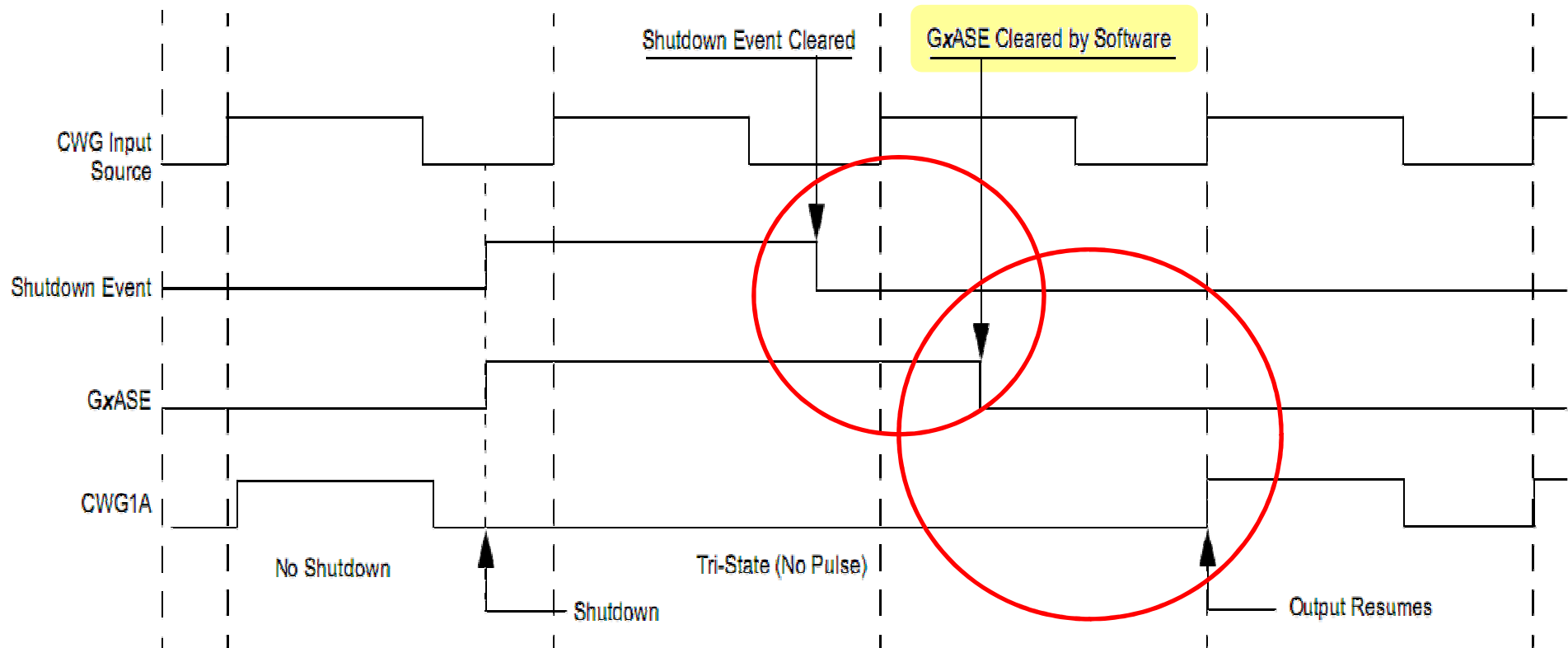

CWG Applications

 Example Applications

- Switch Mode Power Supplies
- LED / Fluorescent lighting
- Battery Charger
- Motor Drive
- Power Factor Correction
- Class D Audio Amplifiers



Ex: Half Bridge Circuit using CWG

Use CWG advanced features to provide dead-band control, auto shut down



Lab 3


Driving a Motor with the CWG

Lab 3 – CWG Motor Control


CWG Setup

Converts PWM signal into complementary form

P-type for efficiency

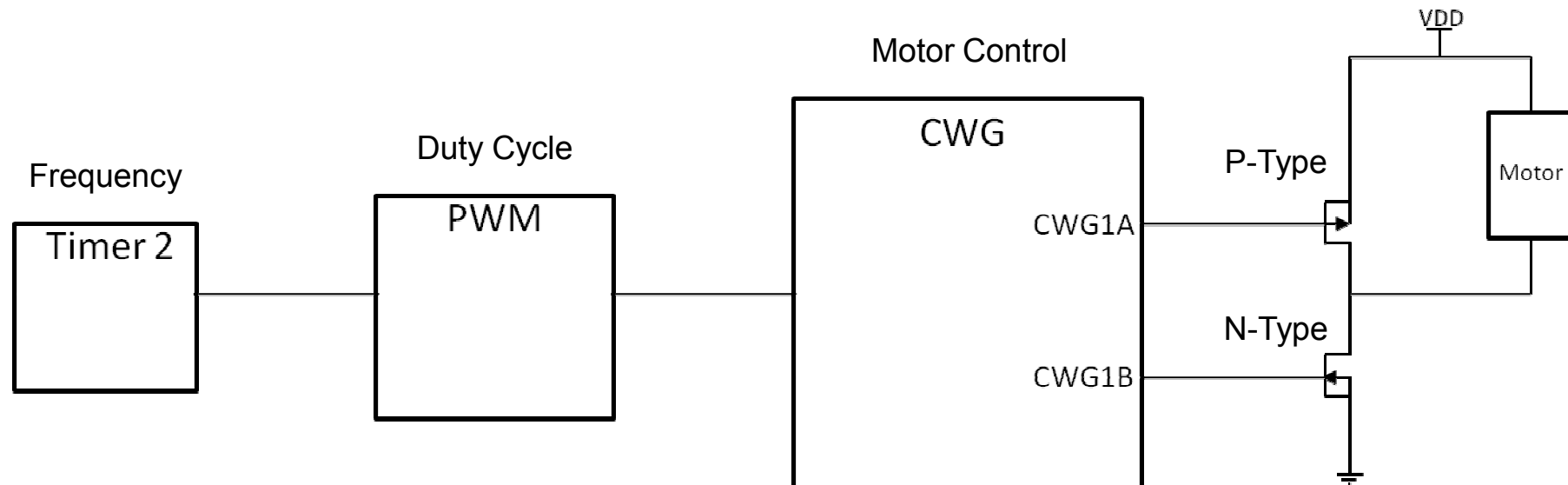

Lab 3 – CWG Motor Control

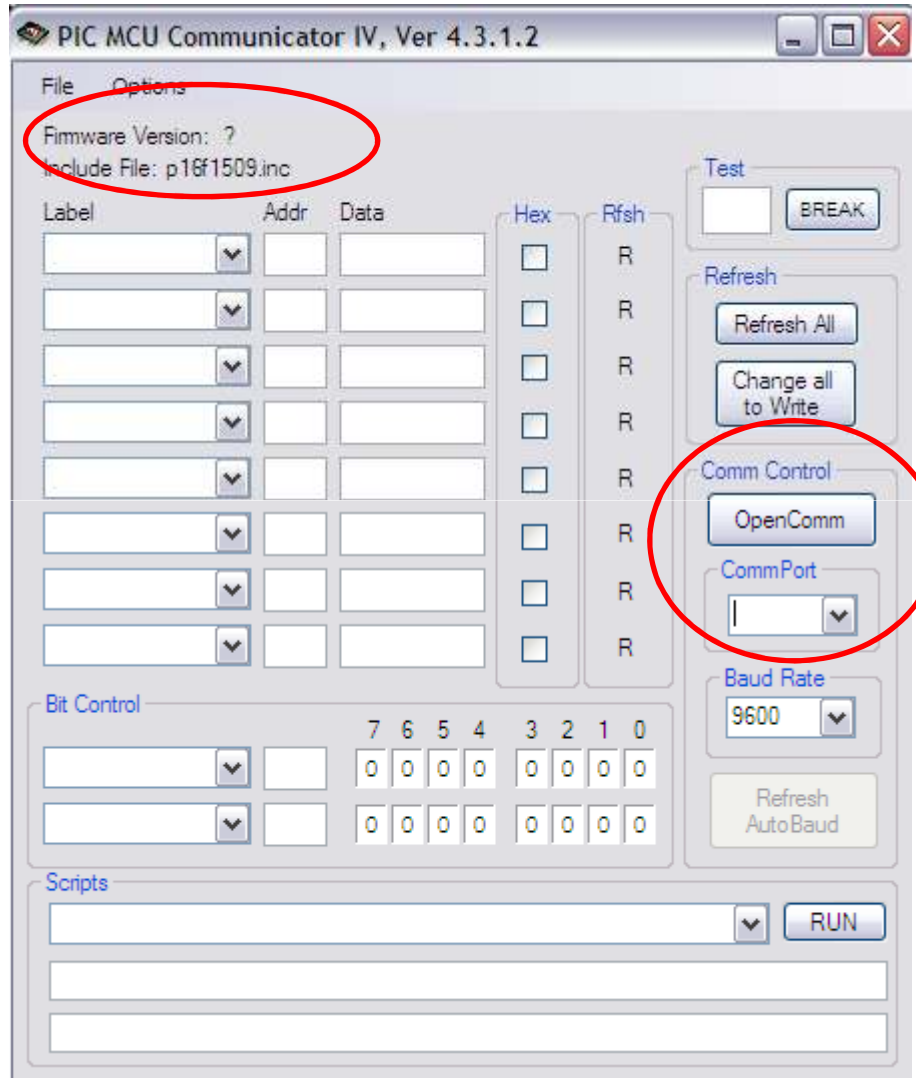

How to setup PIC communicator

1. Close jumpers J3 and bottom one on J4 on daughter board
2. Open CLC designer tool
3. In lower left hand corner, press "OPEN" button
4. Connect USB cord to board
5. Select the COM Port (most likely COM8) or whichever is the greatest number
6. Click "Open comm"
7. If successful, the firmware version will no longer be a question mark "?"

Lab 3 – CWG Motor Control


PIC Communicator

The registers needed are (in order):

T2CON
PWM1DCH
PWM1DCL
PWM1CON
CWG1CON1
CWG1DBR
CWG1DBF
CWG1CON0

Note:

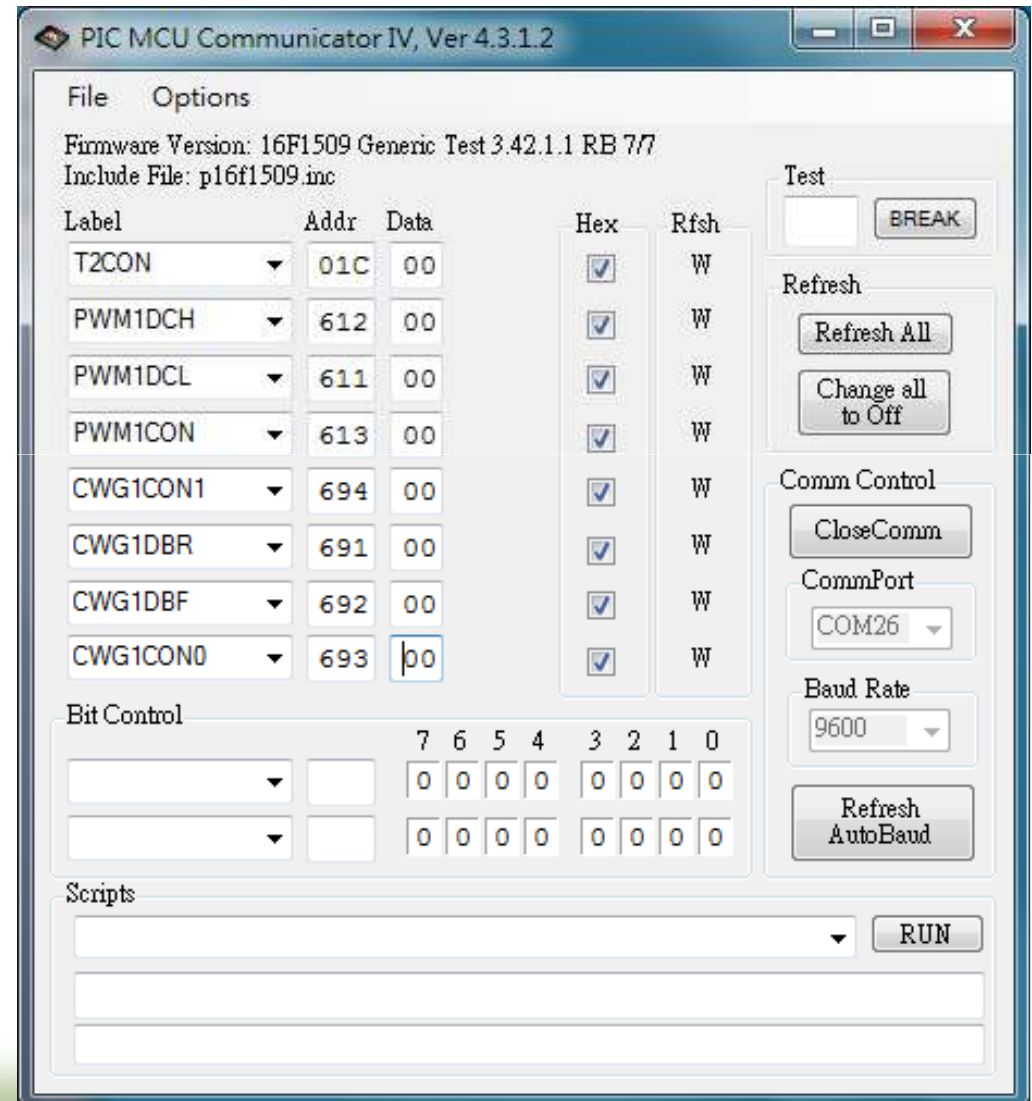
Remove all jumpers from J4 and J6 (daughter)
Close both horizontal jumpers on J5 (daughter)



NCO and CWG Applications

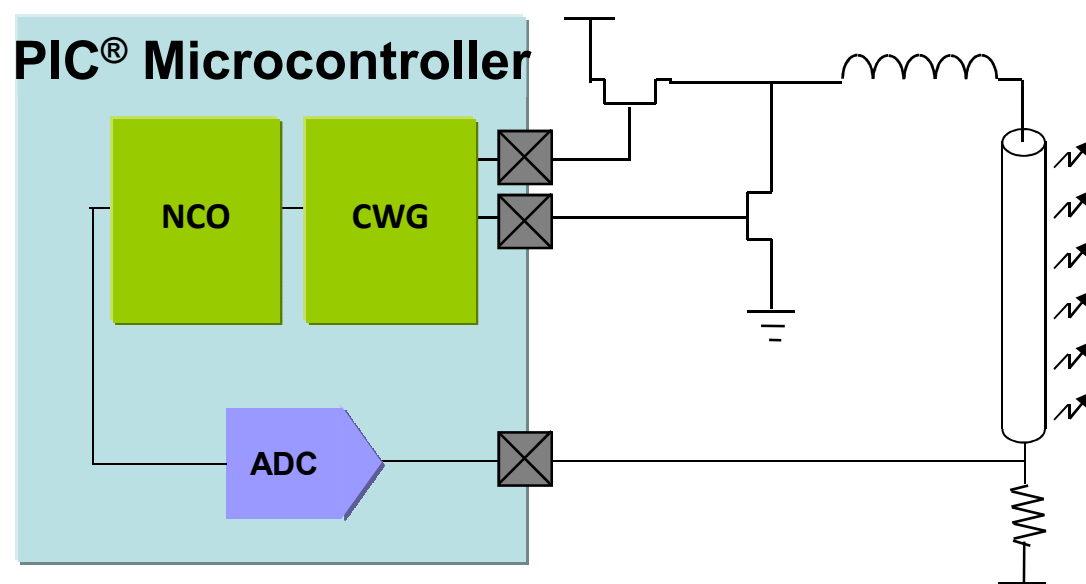
Example Applications

- Fluorescent & LED Lighting Control
- Neon Lighting Control
- Lighting Ballast
- Resonant Power Supplies
- Motor Drivers
- Radio Tuning Circuitry
- Class D Audio Amplifiers



Ex: **Fluorescent Lighting Control**

NCO used to create linear frequencies for start-up and dimming control for lower power and extended lifetime of the fluorescent bulb

 



Lab 4


Sending Motor Speed Through Manchester Encoder

Lab 4 – Motor Speed

Motor Speed Measurement

Gives a small pulse every half revolution


Design a method using two CLC blocks and the NCO to measure the period of the two pulses

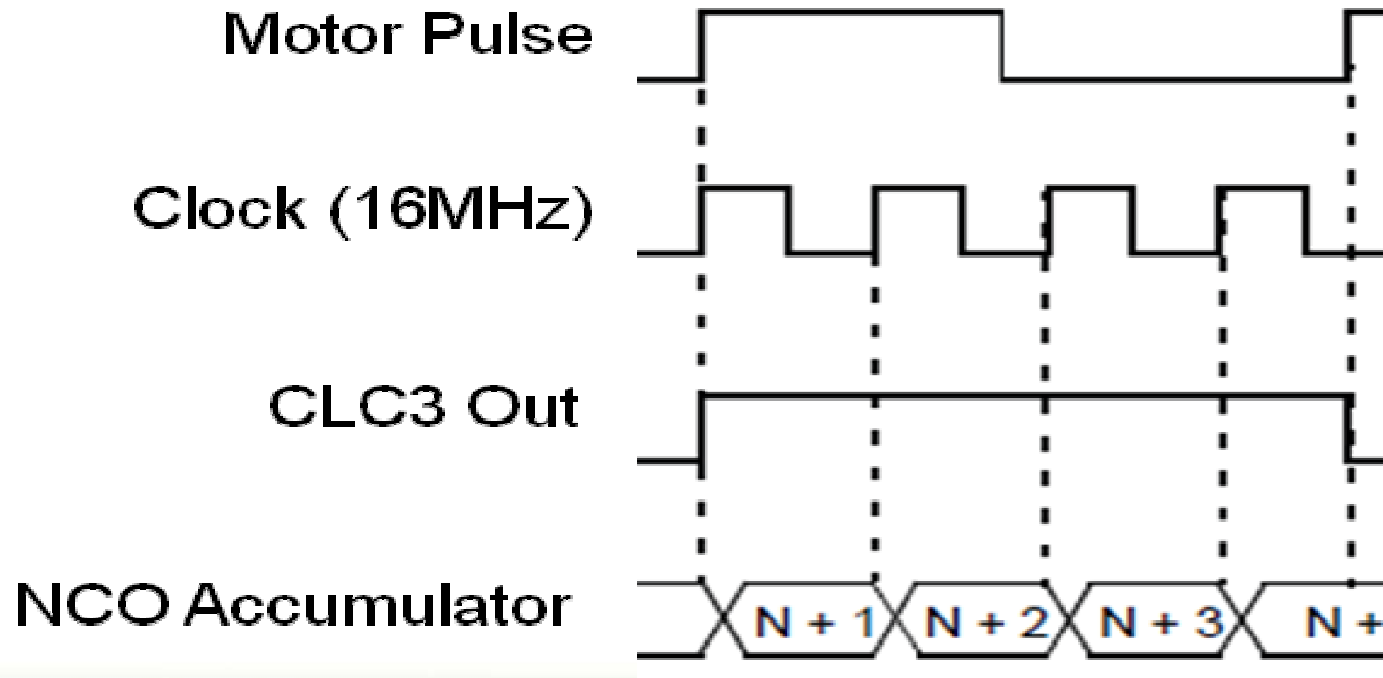


Lab 4 – Motor Speed

Period Measurement

Measures the time between two rising edges

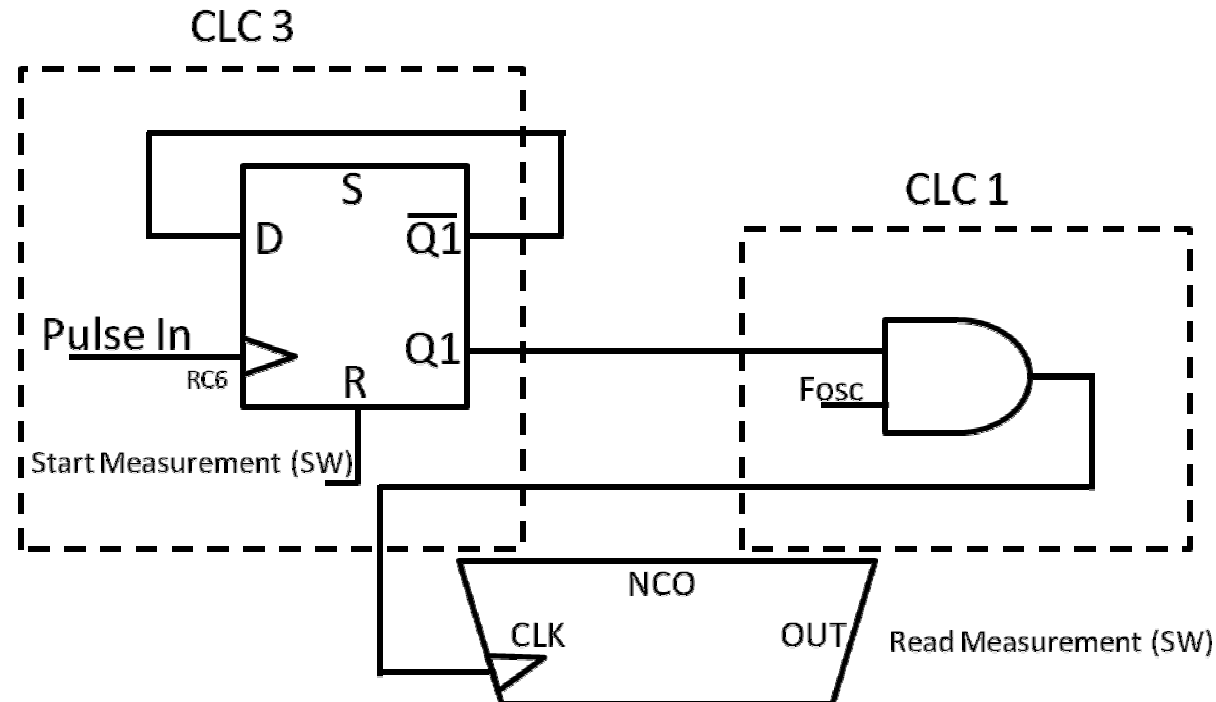

Lab 4 – Motor Speed

 


This stage toggles the output for every rising edge of the clock (clock divider)

The reset line is cleared in software when you want to measure the pulse, and then set when the pulse is captured.

The interrupt flag must be configured on the output falling edge in order to signal the end of the pulse. The flag can then be polled in software.

Lab 4 – Motor Speed

 

This stage passes the clock to the next stage when the input is high




This stage times the pulse. The value is read out in software.

Lab 4 – Motor Speed

Period Measurement

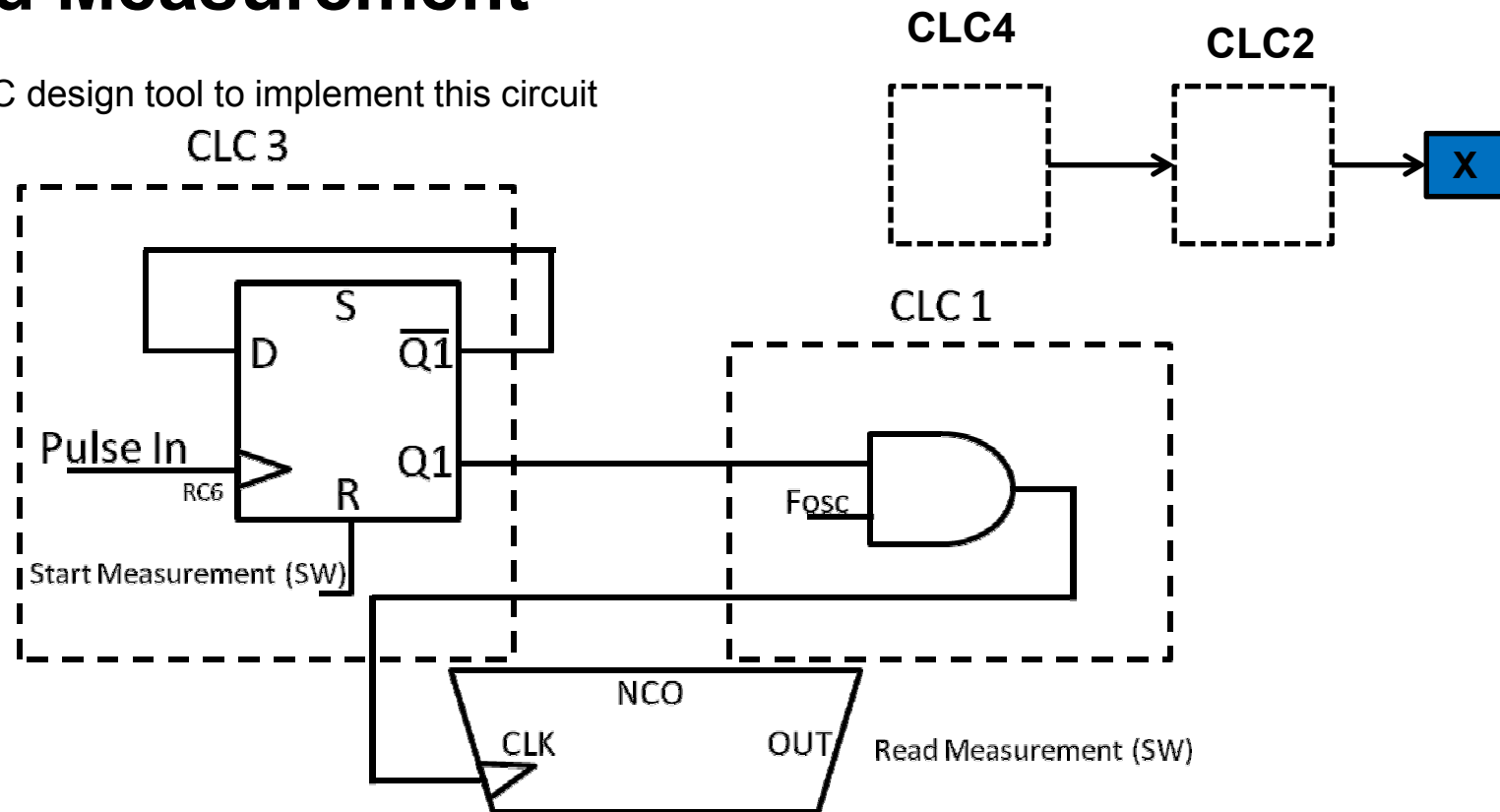Use the CLC design tool to implement this circuit



Note:

Connect POT2 to the PIC by placing a jumper on J5 on the base board.

Keep the same jumper connections from Lab 3.

Pin 2 of J6 is the top pin. Pin 2 of J7 is the right pin.

•Save as "lab4.inc" in:

C:\MASTERS\1610\Manchester Encoder.X\src



Summary

Summary

CLC Benefits

- Increases on chip interconnection of peripherals and I/O
- Integrates hardware functions & saves board area
- Save program code space & frees up resources

NCO Benefits

- Linear frequency control
- Increased frequency resolution

CWG Benefits

- Save Hardware space
- Improved switching efficiencies
- Save program code space & frees up resources

Current Parts

Device	FLASH (Bytes)	RAM (Bytes)	I/O Pins	ADC	Comp.	5-bit DAC	Comms.	CLC	CWG, NCO, Temp Ind	PWM	8-/16-bit Timers
--------	------------------	----------------	-------------	-----	-------	--------------	--------	-----	--------------------------	-----	---------------------

6-pin

PIC10(L)F320	448	64	4	3x 8-bit	-	-	-	1	<input checked="" type="checkbox"/>	2	2/0
PIC10(L)F322	896	64	4	3x 8-bit	-	-	-	1	<input checked="" type="checkbox"/>	2	2/0

8-pin

PIC12(L)F1501	1.75K	64	6	4x 10-bit	1	!!	-	2	<input checked="" type="checkbox"/>	4	2/1
---------------	-------	----	---	-----------	---	----	---	---	-------------------------------------	---	-----

14-pin

PIC16(L)F1503	3.5K	128	12	8x 10-bit	2	!!	MI ² C™, SPI	2	<input checked="" type="checkbox"/>	4	2/1
---------------	------	-----	----	-----------	---	----	-------------------------	---	-------------------------------------	---	-----

20-pin

PIC16(L)F1507	3.5K	128	18	12x 10-bit	-	-	-	2	<input checked="" type="checkbox"/>	4	2/1
PIC16(L)F1508	7K	256	18	12x 10-bit	2	!!	EUSART, MI ² C™, SPI	4	<input checked="" type="checkbox"/>	4	2/1
PIC16(L)F1509	14K	512	18	12x 10-bit	2	!!	EUSART, MI ² C™, SPI	4	<input checked="" type="checkbox"/>	4	2/1

Trademarks

The Microchip name and logo, the Microchip logo, dsPIC, KeeLoq, KeeLoq logo, MPLAB, PIC, PICmicro, PICSTART, PIC³² logo, rfPIC and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

FilterLab, Hampshire, HI-TECH C, Linear Active Thermistor, MXDEV, MXLAB, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, chipKIT, chipKIT logo, CodeGuard, dsPICDEM, dsPICDEM.net, dsPICworks, dsSPEAK, ECAN, ECONOMONITOR, FanSense, HI-TIDE, In-Circuit Serial Programming, ICSP, Mindi, MiWi, MPASM, MPLAB Certified logo, MPLIB, MPLINK, mTouch, Omniscient Code Generation, PICC, PICC-18, PICDEM, PICDEM.net, PICKit, PICtail, REAL ICE, rfLAB, Select Mode, Total Endurance, TSHARC, UniWinDriver, WiperLock and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.
All other trademarks mentioned herein are property of their respective companies.

© 2012, Microchip Technology Incorporated, All Rights Reserved.