



**MICROCHIP**  
*InControl*



# Mechatronics WIB


## Selecting Power MOSFET Drivers




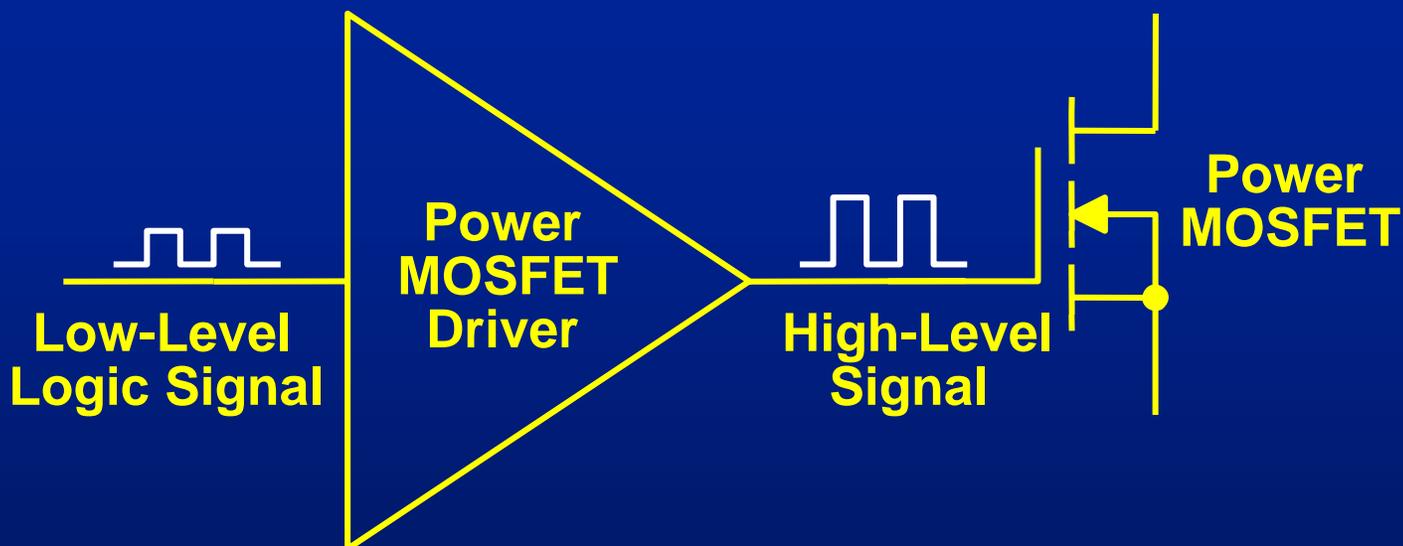
# What is a Power MOSFET Driver?


- **Power MOSFET Drivers Transform**
  - ❖ **Low-Level Logic Signal**
  - ❖ **High-Level Signal**
  - ❖ **Capable of Driving Power MOSFETs**




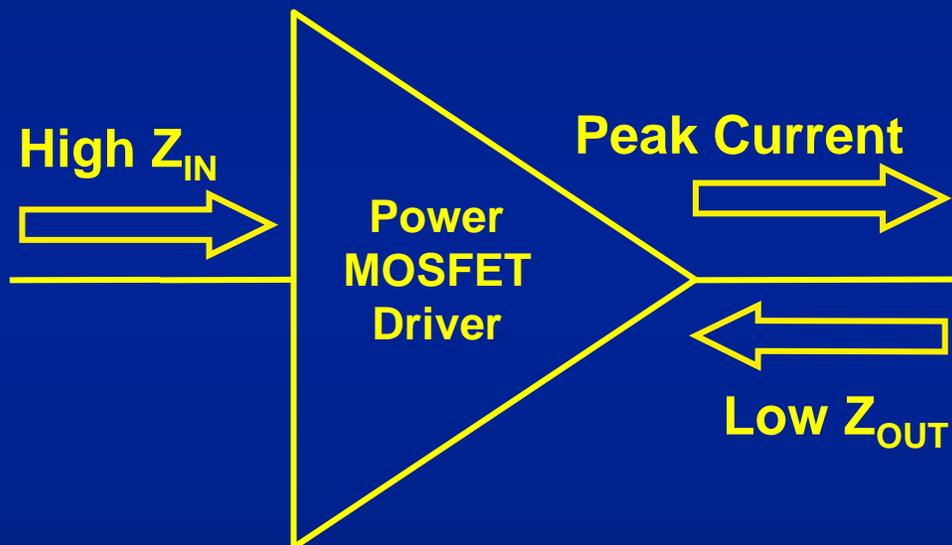
# Power MOSFET Driver Key Characteristics


- High Input Impedance
- Low Output Impedance
- Provide Large Peak Currents
- Low Internal Delays
- Fast Output Rise & Fall Times
- Minimize Shoot-Through Currents





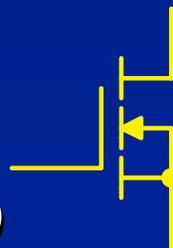
# What Do Power MOSFET Drivers Drive?

- **Power MOSFETs**
  - ❖ **Known Under Various Tradenames**
    - ❖ VMOS
    - ❖ TMOS
    - ❖ Vertical DMOS
    - ❖ HEXFET



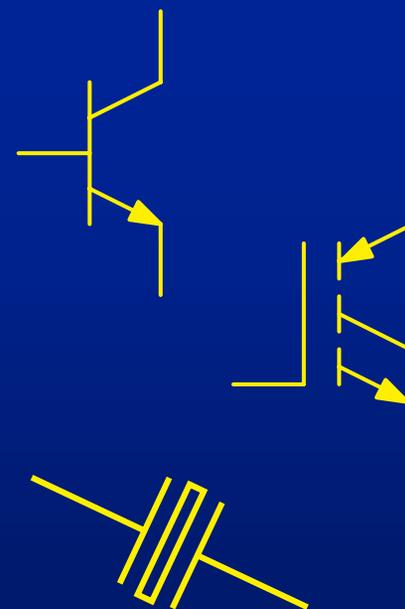- **BJTs (Bipolar Junction Transistor)**
- **IGBTs (Insulated Gate Bipolar Transistor)**
- **Piezo Electric Transducers**






# Power MOSFET Driver Applications

- Motors
- Relays and Solenoids
- Switch Mode Power Supply (SMPS)
- CCDs
- Inductive Loads
- Transducers
- Visual Indicators





# MOSFET Driver Offering

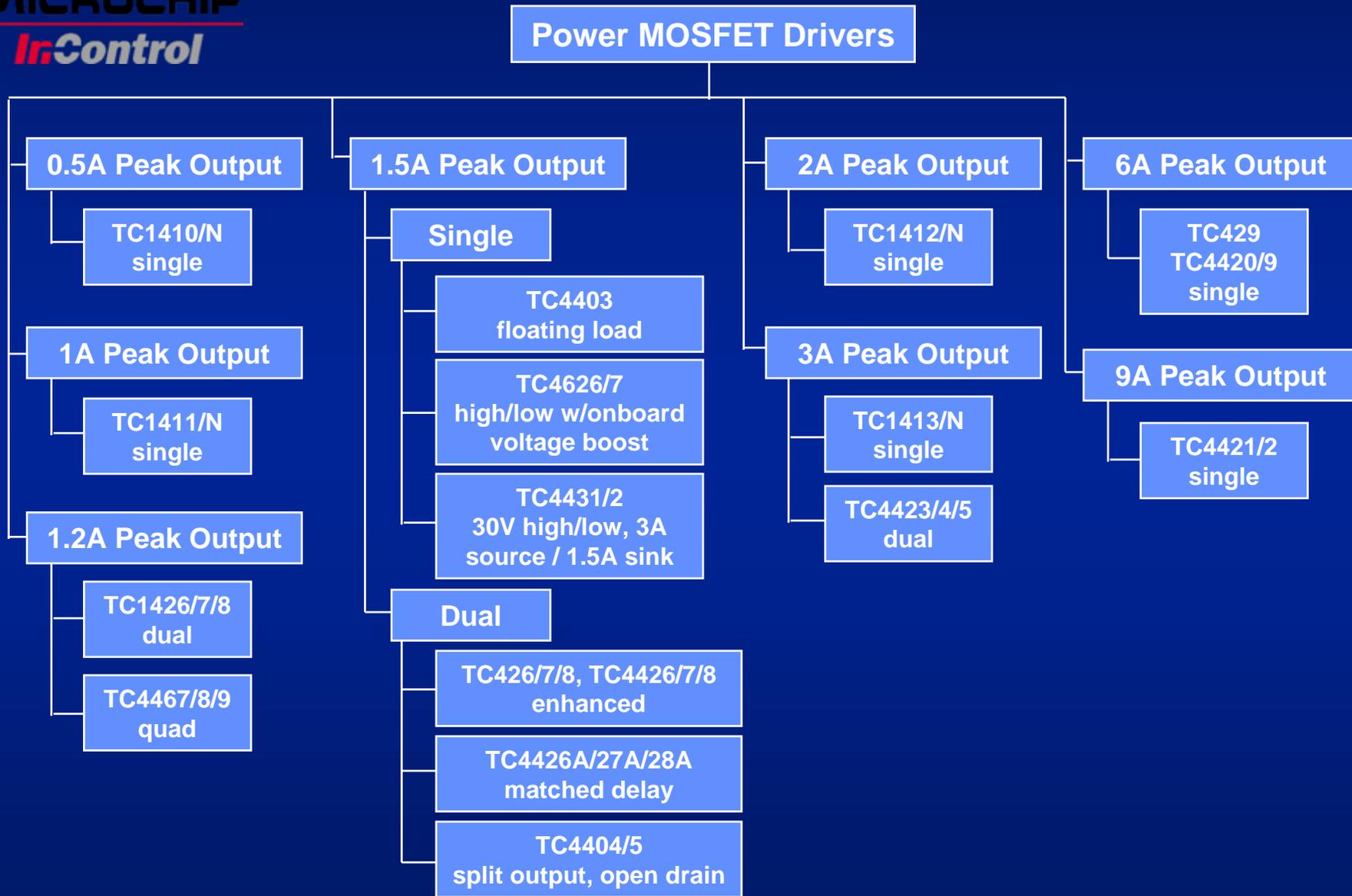

# Microchip MOSFET Driver Key Features

- Broad operating voltage range: 4.5V to 30V
- Broad peak current capability: 0.5A to 12A
- Input / output delay: 30 to 75 ns
- Low power dissipation
- Single, dual, quad packages
- Special features
  - ❖ Superior ESD & latch-up protection
  - ❖ TTL compatible
  - ❖ Operating junction temperature to 150°C



# Power MOSFET Driver Key Parameters By Application

## Low Speed Applications:


- ❖ Key Parameters:  $V_{OH}$ ,  $V_{OL}$ 
  - ❖ Level Shifters
  - ❖ H-Bridge Motor Controllers
  - ❖ Voltage Inverters.

## ● High Speed Applications:

- ❖ Key Parameters:  $V_{OH}$ ,  $V_{OL}$ ,  $I_{PK}$ ,  $t_R$ ,  $t_F$ ,  $t_{D1}$ ,  $t_{D2}$ 
  - ❖ Switch Mode Power Supplies



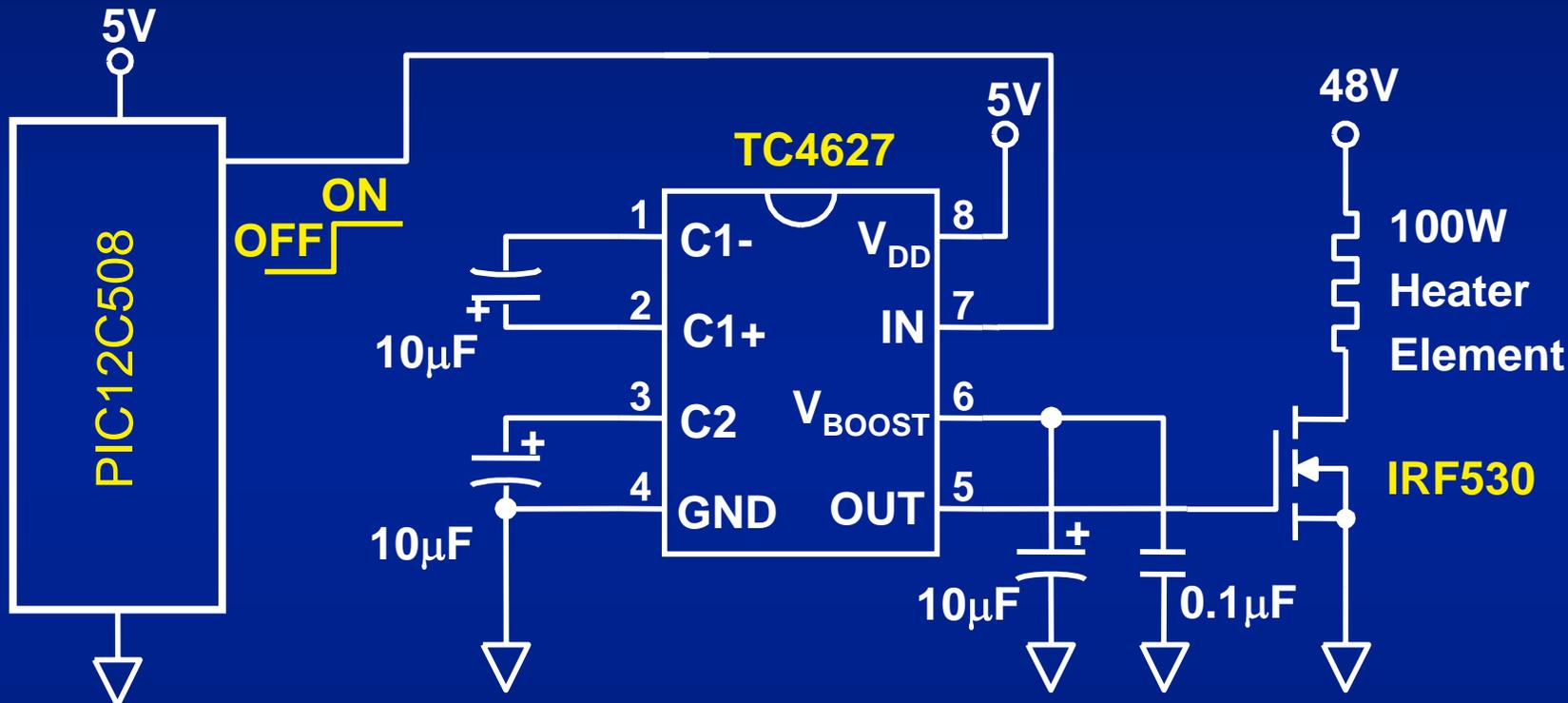
# Low Speed Power MOSFET Driver Application



- **IRF530**
  - ❖ Requires Gate-to-Source Drive Voltage of  $\geq 10V$
- **TC4627**
  - ❖ Provides Output Voltage of 15V




# Driver / MOSFET Requirements

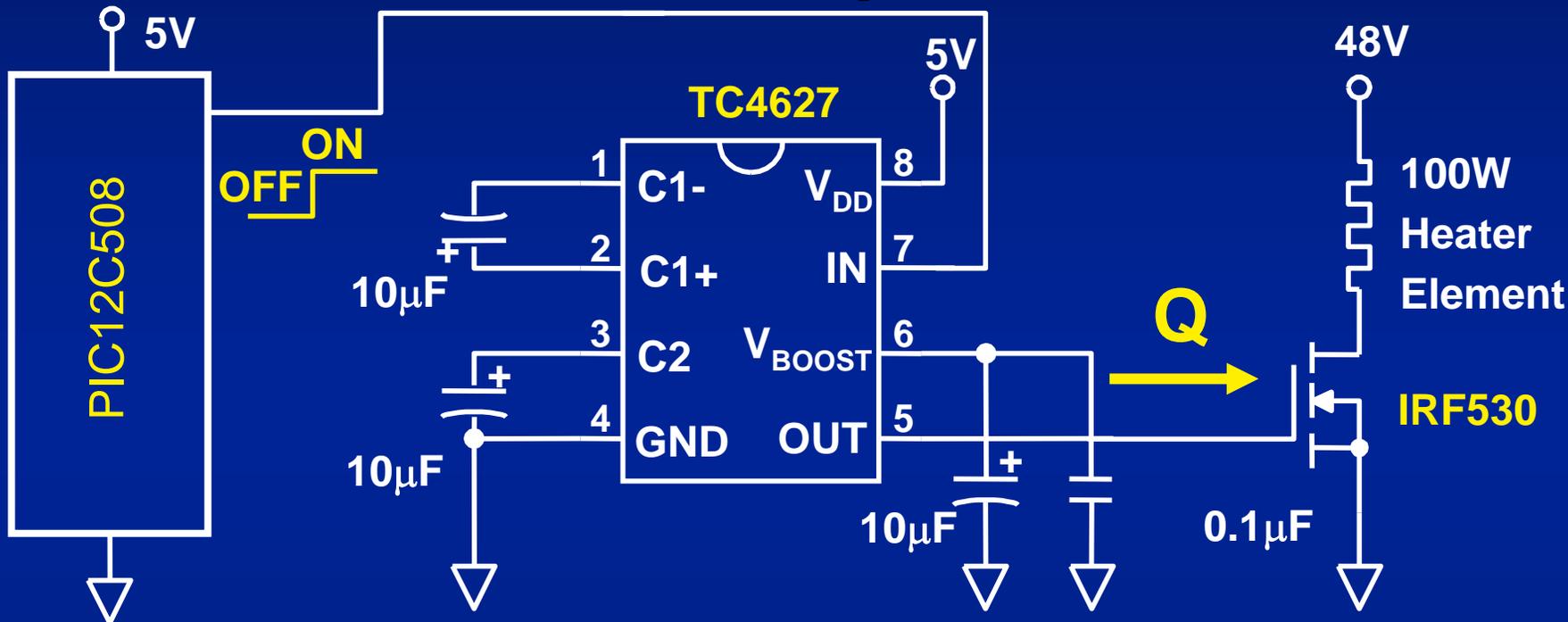


- Gate-to-Source Drive Voltage = 15V
- Specifications Not Important For This Application:
  - ❖ Total Gate Charge ( $Q_g$ ) from Driver  $\geq 37\text{nC}$
  - ❖ Switch Time  $\leq 0.1\mu\text{s} = \text{TC4627}_{\text{DELAY}} + \text{TC4627}_{\text{RISE TIME}} + \text{IRF530}_{\text{SWITCH TIME}}$
  - ❖  $I_{PK} = 1.5\text{A}$

# H-Bridge Driver Application

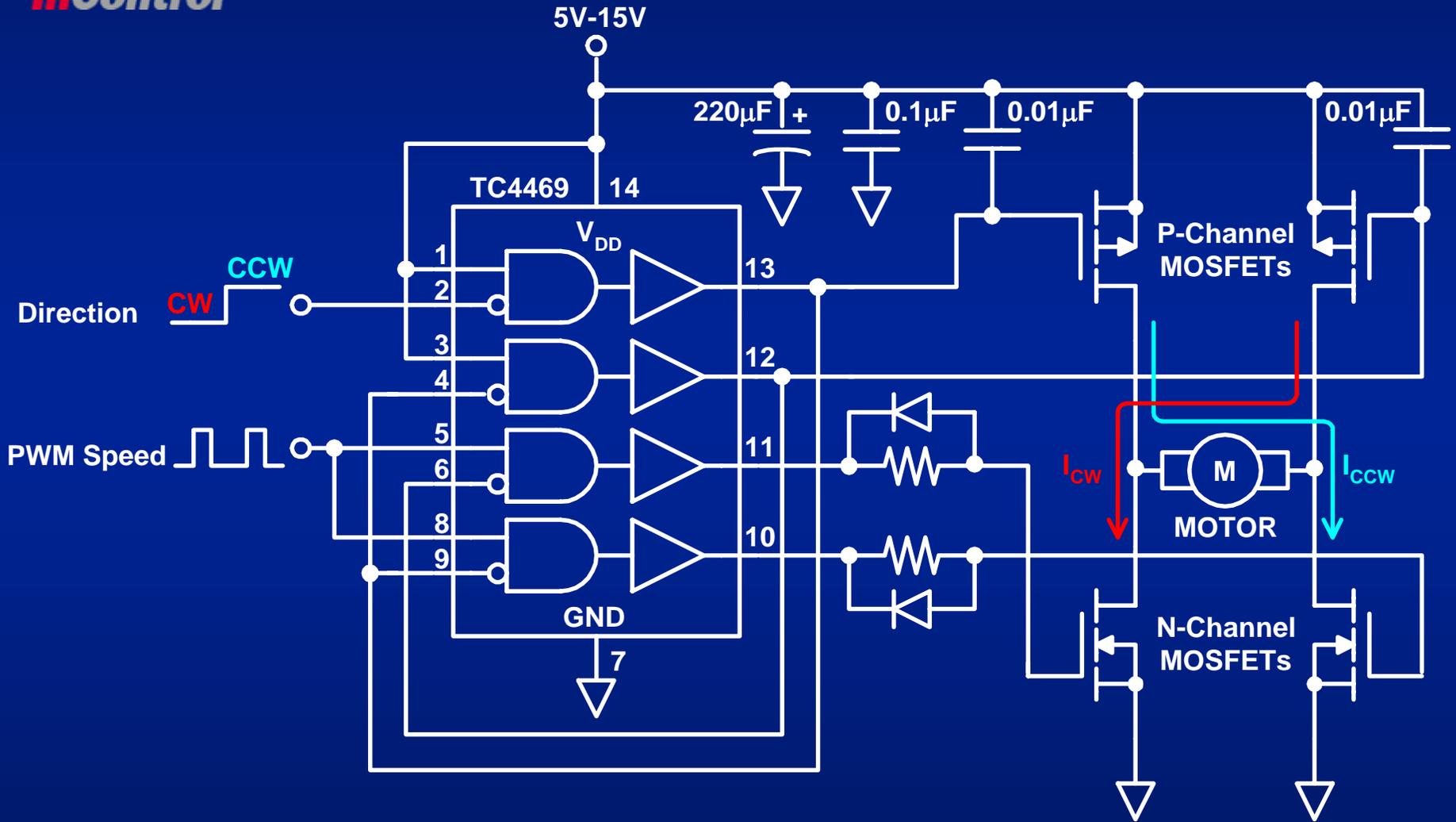


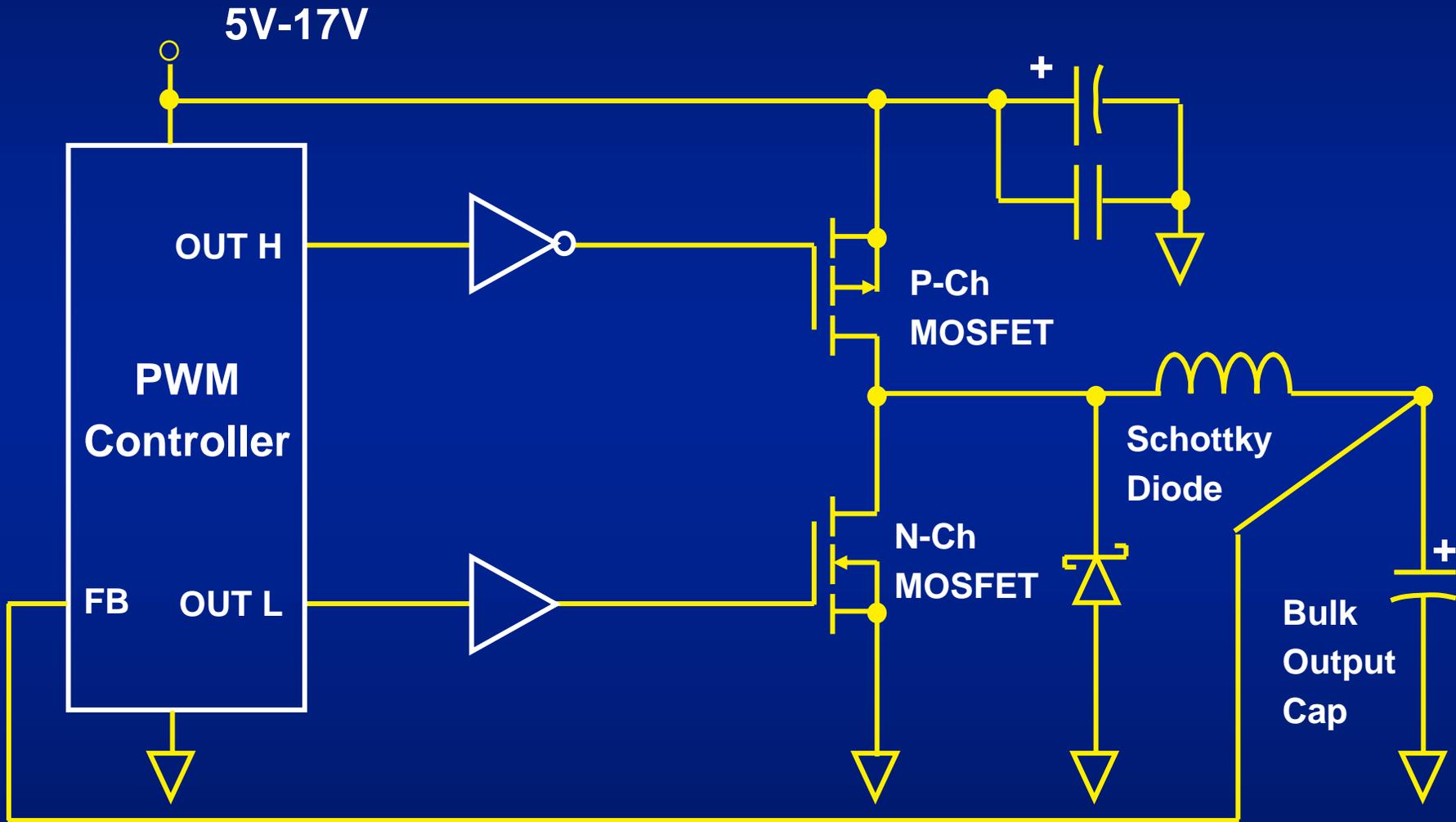
# High Speed Switch-Mode Power Supply (SMPS) Application





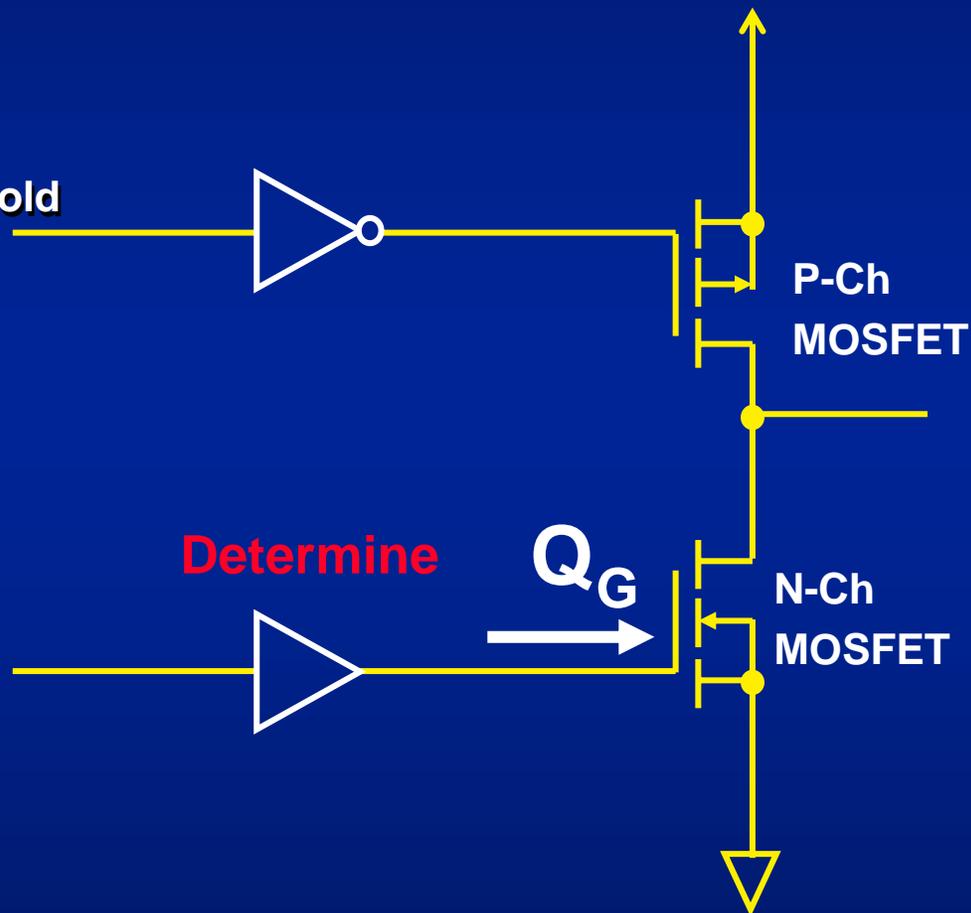
# MOSFET Interface Key Issues

- **MOSFET**
  - ❖ Total Required Gate Charge,  $Q_G$
  - ❖ Gate-to-Source Threshold Voltage,  $V_{GS(TH)}$


- **Driver**
  - ❖ Output Swing
    - ❖  $V_{OH}$  and  $V_{OL}$
  - ❖ Peak Output Current,  $I_{PK}$
  - ❖ Rise and Fall Times
    - ❖  $t_R$ ,  $t_F$
  - ❖ Delay Times
    - ❖  $t_{D1}$ ,  $t_{D2}$




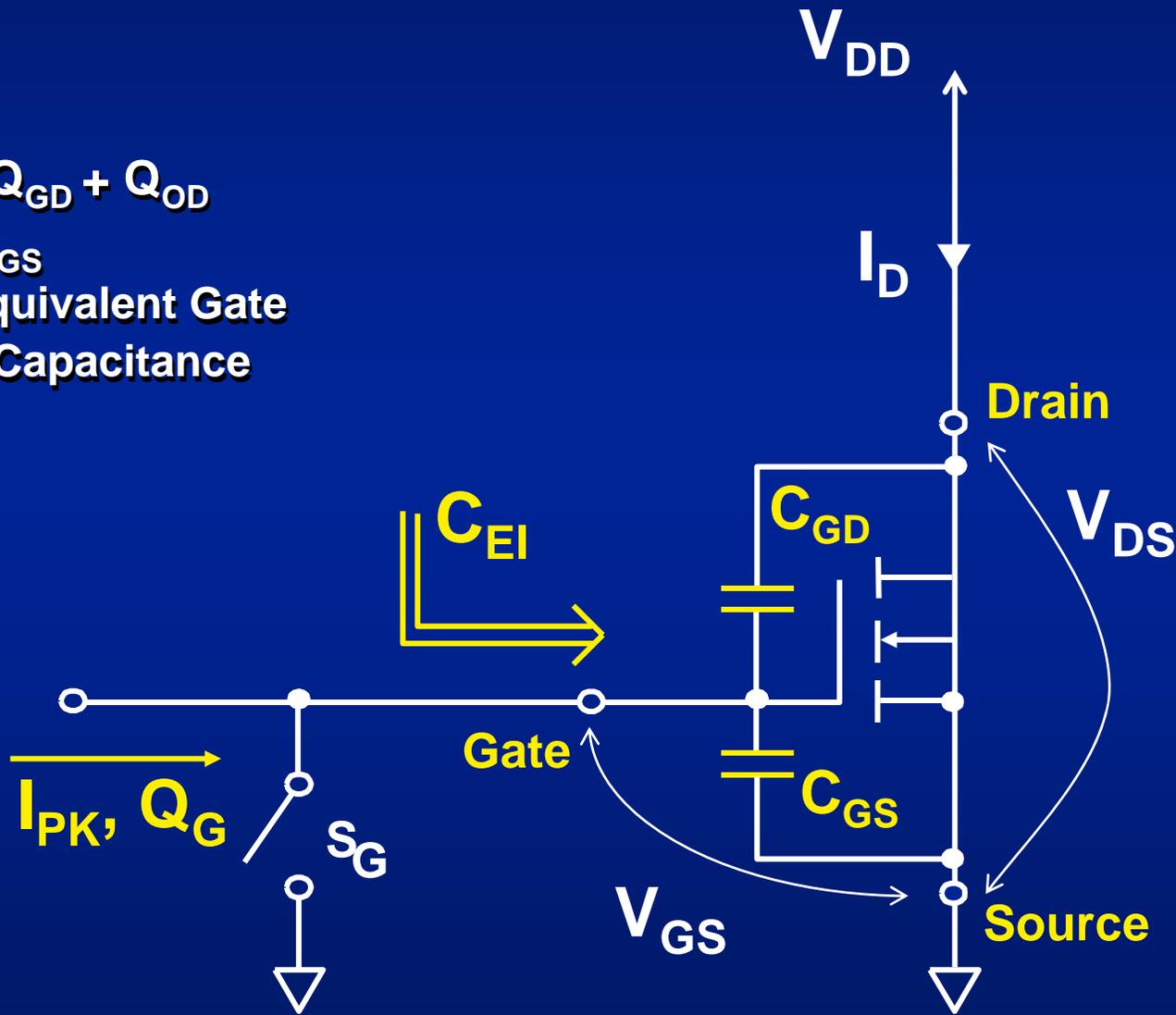
# MOSFET Driver Design Equations


- $Q_G = t \times I_{PK}$
- $Q_G = Q_{GS} + Q_{GD} + Q_{OD}$
- $Q_G = C_{EI} \times V_{GS}$ 
  - ❖  $C_{EI}$  = Equivalent Gate Capacitance





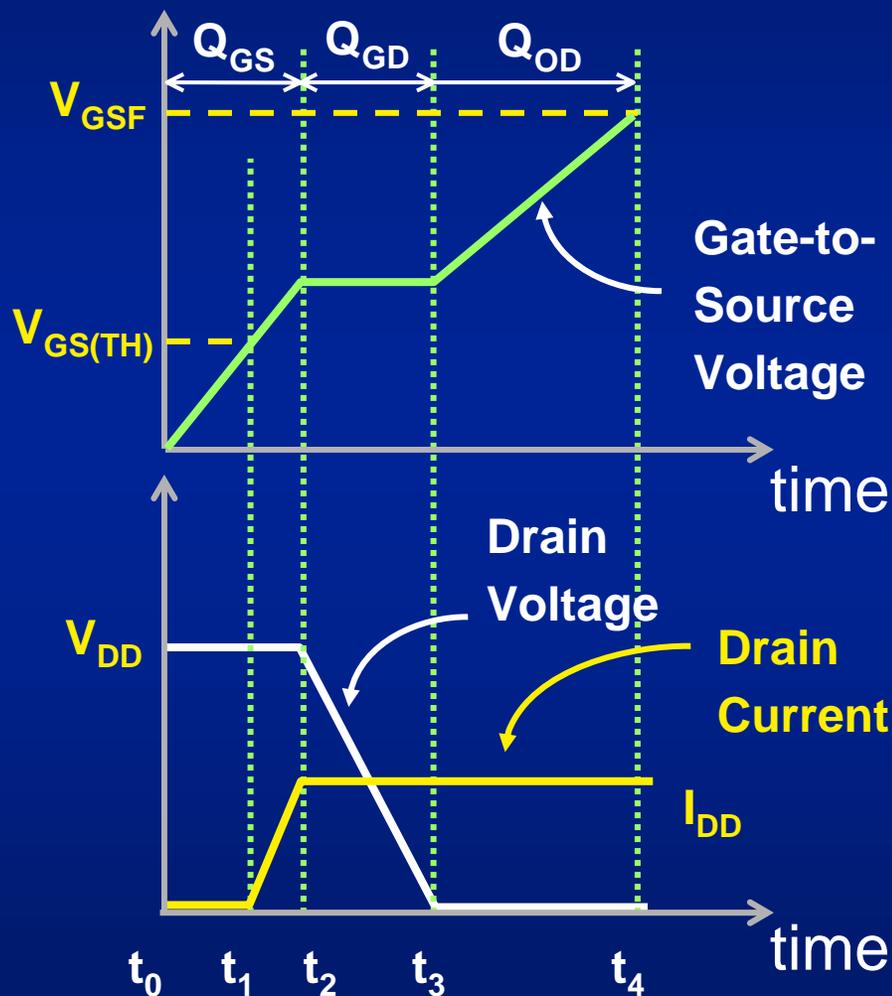
# MOSFET Gate / Drain Waveforms

- $Q_G = t \times I_{PK}$
- $Q_G = Q_{GS} + Q_{GD} + Q_{OD}$
- $Q_G = C_{EI} \times V_{GS}$ 
  - ❖  $C_{EI}$  = Equivalent Gate Capacitance




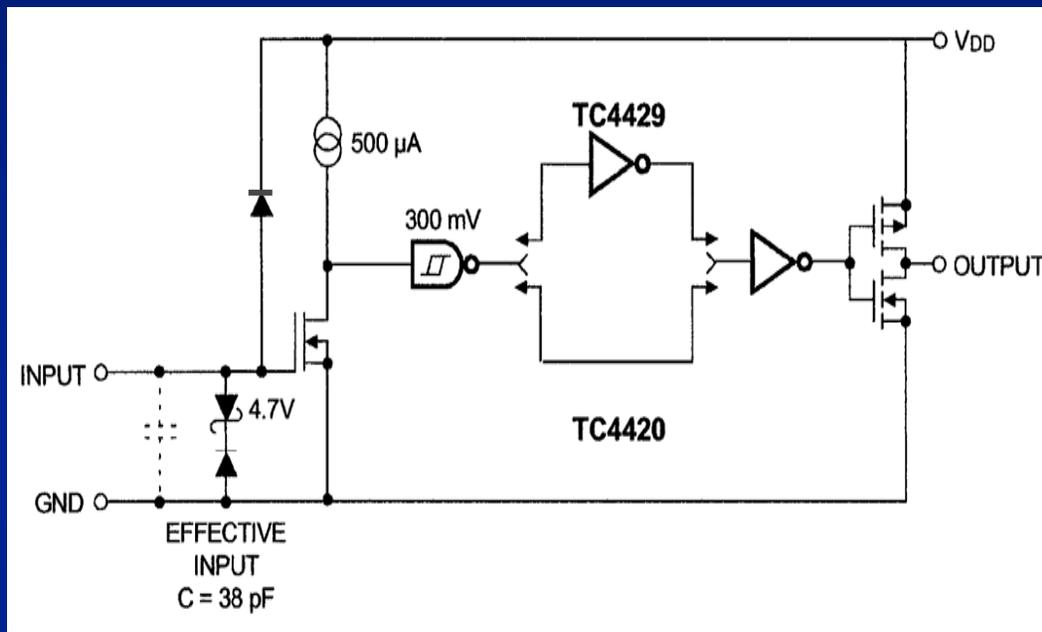
# Power MOSFET Driver Input Electrical Characteristics




Symbol	Parameter	Min	Max
$V_{IH}$	Logic High Input Voltage	2.4V	—
$V_{IL}$	Logic Low Input Voltage	—	0.8V
$V_{IN(MAX)}$	Input Voltage Range	-5V	$V_{DD} + 0.3V$
$I_{IN}$	Input Current	-10 $\mu$ A	10 $\mu$ A



# Power MOSFET Driver


## Output Electrical Characteristics

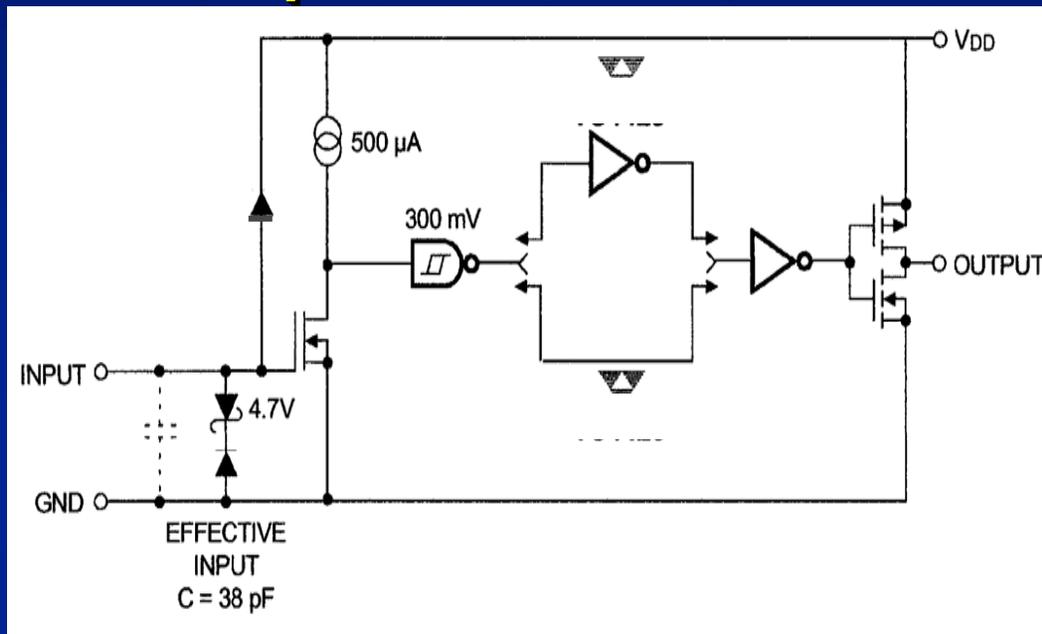

Symbol	Parameter	Min	Typ	Max
$V_{OH}$	High Output Voltage	$V_{DD} - 0.025V$	—	—
$V_{OL}$	Low Output Voltage	—	—	0.025V
$R_O$	Output Resistance	—	1.5 $\Omega$	2.8 $\Omega$
$I_{PK}$	Peak Output Current	—	6.0A	—
$I_{REV}$	Reverse Current	1.5A	—	—


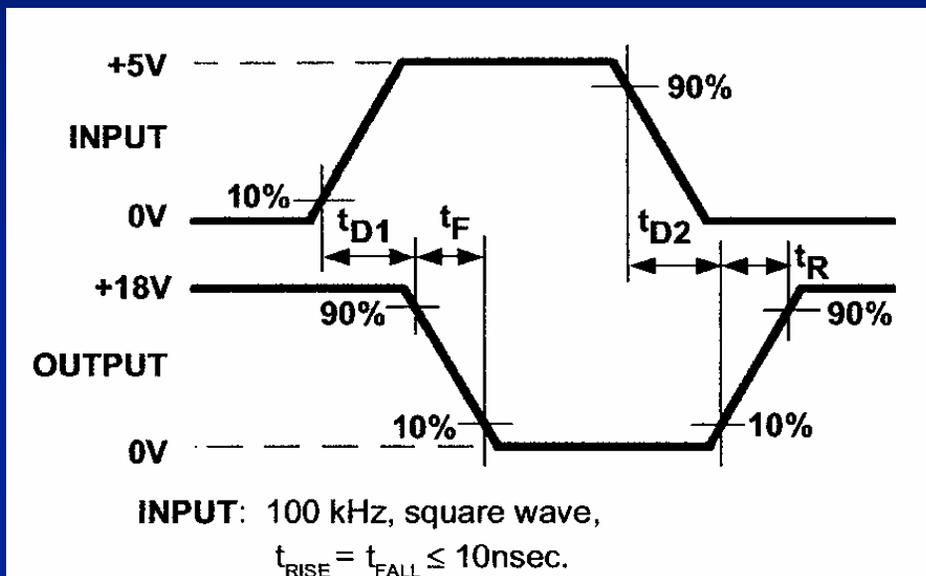
# Power MOSFET Driver Switching Time Characteristics



Symbol	Parameter	Min	Max
$t_R$	Rise Time	—	35nsec
$t_F$	Fall Time	—	35nsec
$t_{D1}$	Delay Time 1	—	75nsec
$t_{D2}$	Delay Time 2	—	75nsec



# Key Driver Output Voltage Considerations

- **Equivalent Input Gate Capacitance,  $C_{EI}$** 
  - ❖ **Must Be Charged Up Beyond Gate-to-Source Threshold Voltage,  $V_{GS(TH)}$** 
    - ❖  $V_{GSF} \gg V_{GS(TH)}$ 
      - ❖  $V_{GSF} = Q_G / C_{EI}$
      - ❖  $V_{GSF}$  Typically Equals  $V_{OH}$  of Driver



# Key Driver Timing Considerations

- **MOSFET Driver's Peak Output Current,  $I_{PK}$** 
  - ❖ Determines Time Required to Charge Up  $C_{EI}$  to  $V_{GSF}$ 
    - ❖  $t_R = Q_G / I_{PK}$
- **MOSFET Driver's Output Impedance,  $R_O$** 
  - ❖ Limits Peak Output Current,  $I_{PK}$



# Good Design Practices

- **$V_{GSF} \gg V_{GS(TH)}$  - Good Design Practice**
  - ❖ **Assures Channel of MOSFET is Fully Enhanced**
  - ❖  **$V_{GS(TH)} = 2V$  min. to  $4V$  max. For IRFR120N**
- **Have  $R_{DS(ON)}$  of MOSFET as Low as Possible**
  - ❖ **MOSFET Manufacturers Specify Static Drain-to-Source on Resistance,  $R_{DS(ON)}$**
  - ❖  **$R_{DS(ON)} = 0.21\Omega$  max. @  $V_{GS} = 10V$  For IRFR120N**



# Power MOSFET Driver Selection Example

- **Select MOSFET for Application**
- **Identify Important Design Parameters**
  - ❖ **Application**
  - ❖ **MOSFET**
  - ❖ **Driver**
- **Determine Total Required Gate Charge of MOSFET**
- **Calculate Required Driver Peak Output Current**
- **Select Driver**


# Power MOSFET Driver Selection Example

- **Step 1: Select MOSFET for Application**  
MOSFET = IRFR120N
- **Step 2: Identify Important Design Parameters**  
MOSFET Voltage :  $V_{DS} = 12V$   
MOSFET Gate Voltage:  $V_{GSF} = 12V$   
Required Rise Time in Application:  $t_R = 15ns$



# Power MOSFET Driver Determining Gate Charge

- **Step 3: Using MOSFET Curve  $V_{GS}$  vs  $Q_G$** 
  - ❖ Curve Closest to  $V_{DS} = 12V$ 
    - ❖ Use  $V_{DS} = 20V$  Curve
- **Step 4: Determine Total Gate Charge,  $Q_G$** 
  - ❖ Necessary to Charge Up  $C_{EI}$  to  $V_{GSF} = 12V$   
 **$Q_G \cong 16.25nC$**   
**(Typical Number)**

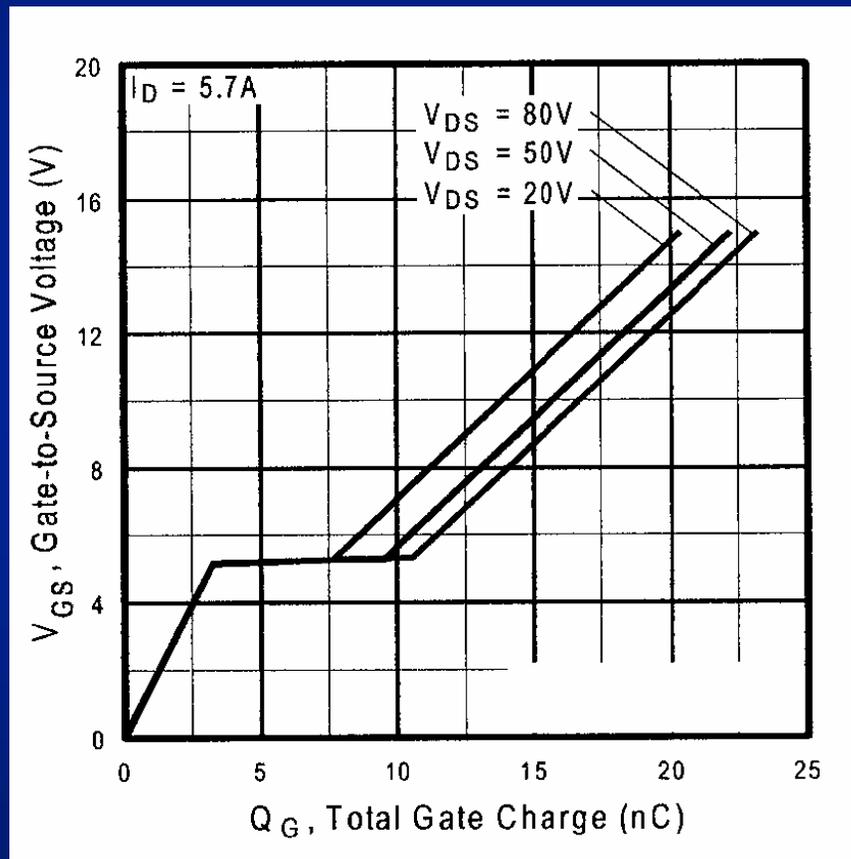

**IRFR120N**



# Power MOSFET Driver Selection Example (Continued)

- **Step 5: Calculate Power MOSFET Driver Required Peak Output Current**
  - ❖  $I_{PK} = Q_G/t_r$ 
    - ❖  $Q_G = \text{Total Gate Charge}$
    - ❖  $t_r = \text{Desired Rise Time}$
  
- **Using  $Q_G$  From IRFR120N  $V_{GS}$  vs.  $Q_G$  Curve**
  - ❖  $I_{PK} = Q_G/t_r = 16.25\text{nC}/15\text{ns} = 1.08\text{A}$

# Power MOSFET Driver Selection Example (Continued)

- **Step 6: Select a Power MOSFET Driver**
  - ❖ **Key Parameters:**
    - ❖ **Supply Voltage =  $V_{DD} \cong V_{OH} = 12V$**
    - ❖ **Peak Output Current =  $I_{PK} > 1.08A$**
  - ❖ **Use Power MOSFET Driver Selection Guide**
    - ❖ **Good Candidate Would Be TC1412**
      - ❖ **Supply Voltage Range = 4.5V - 16V**
      - ❖ **Peak Output Current = 2A**
      - ❖ **Delay Time = 35ns**



# Technical Information

## Microchip Application Notes ([www.microchip.com](http://www.microchip.com))

- **AN-22: Considerations For Driving Power MOSFETs in High-Current Switch Mode Regulators.**
- **AN-25: TC4426/27/28 System Design Practice.**
- **AN-28: TC4420/4429 Universal Power MOSFET Interface IC.**
- **AN-30: Matching MOSFET Drivers to MOSFETs.**
- **AN-40: Switched Attenuation to Improve Current Sensing.**
- **AN-42: Low-Cost DC Motor Speed Control With CMOS ICs.**



## **Technical Information (Continued)**

### International Rectifier Application Notes ([www.irf.com](http://www.irf.com))

- **AN-937 (v.Int): Gate Drive Characteristics and Requirements for HEXFET® s.**
- **AN-944 (v.Int): Use Gate Charge to Design the Gate Drive Circuit for Power MOSFETs and IGBTs.**
- **AN-957 (v.Int): Measuring HEXFET® Characteristics.**
- **AN-983 (v.Int): IGBT Characteristics.**

### International Rectifier Technical Papers ([www.irf.com](http://www.irf.com)):

- ***Power MOSFET Basics* by Vrej Barkhordarian.**
- ***IGBT or MOSFET: Choose Wisely* by Carl Blake and Chris Bull.**



# Conclusions

- **Identify Key Parameters For Application**
  - ❖ **Low Speed Application Key Parameters:**
    - ❖  $V_{OH}, V_{OL}$
  - ❖ **High Speed Application Key Parameters:**
    - ❖  $V_{OH}, V_{OL}, I_{PK}, t_R, t_F, t_{D1}, t_{D2}$
- **Proper Matching of Power MOSFET Driver to MOSFET & Application Yields:**
  - ❖ **Best Efficiency**
  - ❖ **Optimum Performance**
  - ❖ **Lowest Cost**

[BACK](#)