



# Introduction to Digital Controlled Totem-pole PFC Demo Board: Hardware Design

Transphorm Inc.






12/01/2021

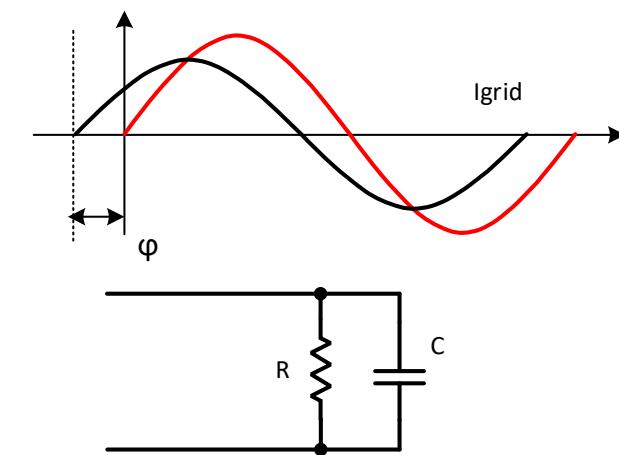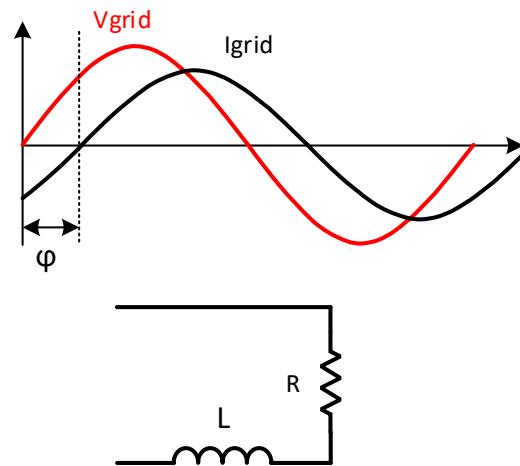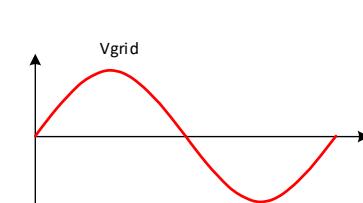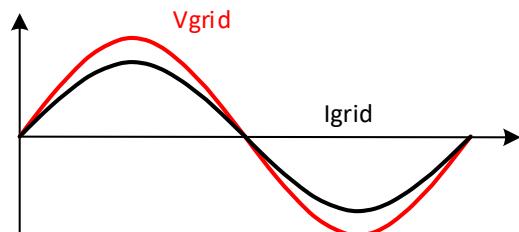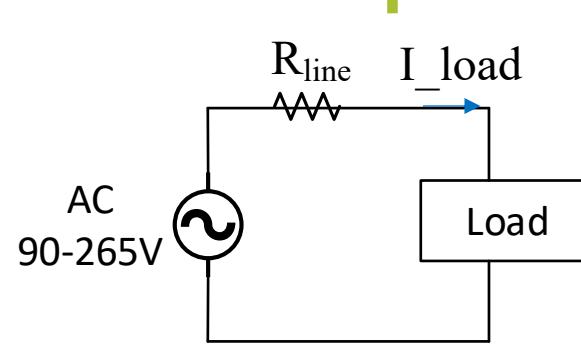**transphorm**

Highest Performance, Highest Reliability GaN



- Concept of PFC
- From Conventional PFC to Bridgeless Totem Pole PFC
- Digital Controlled Totem Pole Bridgeless PFC using Transphorm GaN and Microchip MCU



$$V_{grid} = \sqrt{2}V_s \sin(\omega t), \\ \text{where } V_s = 90 \sim 265V, \\ \omega = 2\pi f_o, f_o = 50 \sim 60Hz$$




$$i_{load} = \sqrt{2}I_s \sin(\omega t - \varphi)$$

$$\bar{P} = V_s I_s \cos \varphi = \text{Real Power}$$

$$S = V_s I_s, \text{ Apparent power}$$


The power factor:
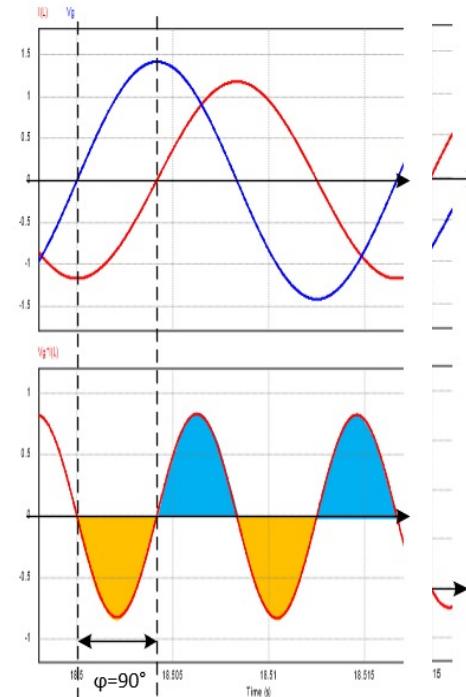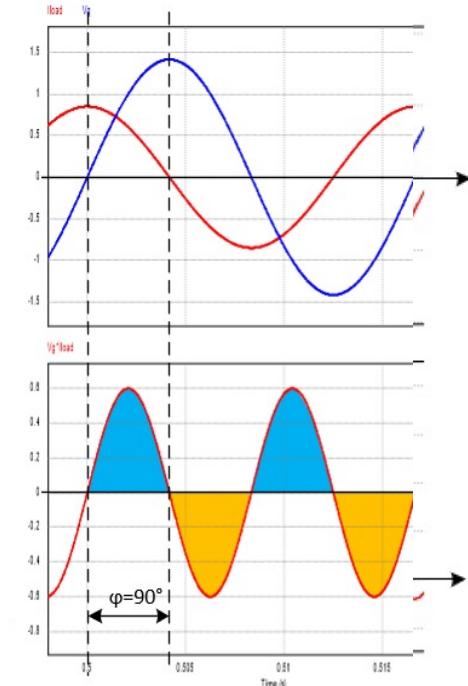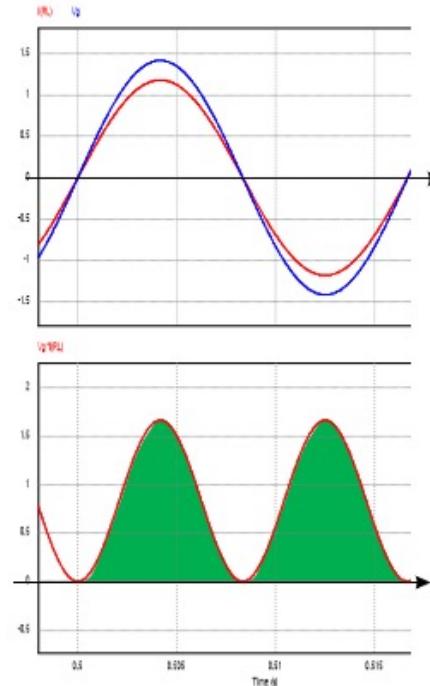
$$PF = \frac{\bar{P}}{S} = \cos \varphi$$







40W Light Bulb

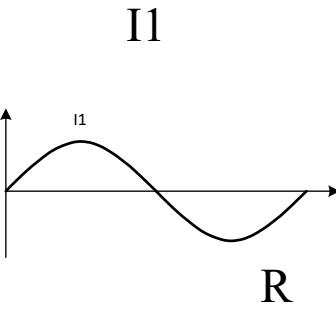

10W LED Bulb

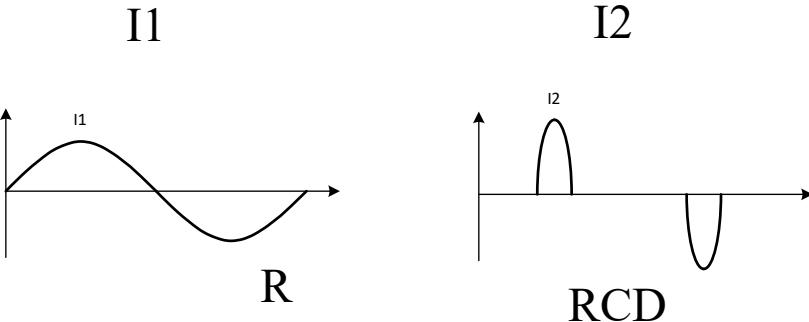

PF~1

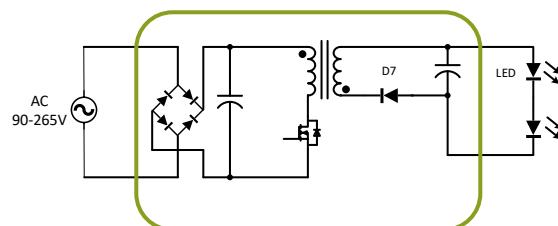

Flyback, PF~0.75





65W Laptop Power Supply





90W Laptop Power Supply



1/4 HP Motor

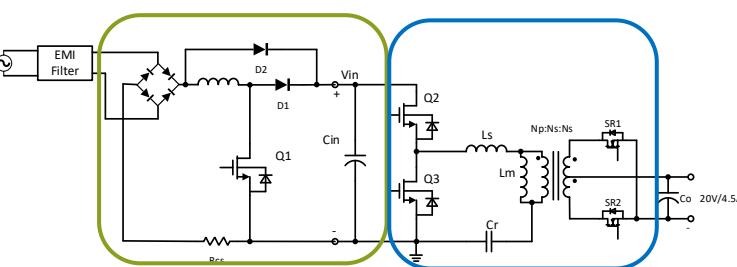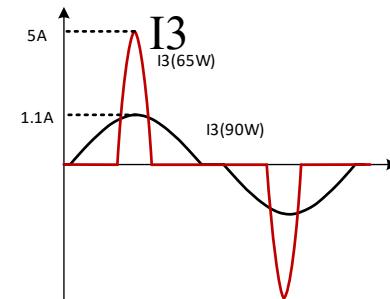

PFC + LLC, PF&gt;0.95

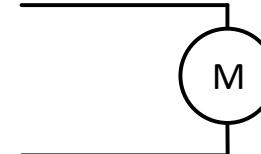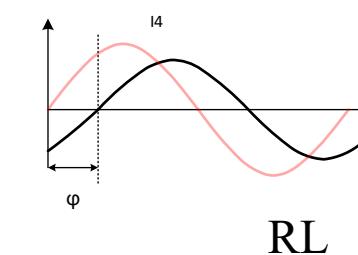

PF=0.6~0.8

1, Why do we need PFC?



To mitigate the impact of harmonics and reduce the power loss, power factor correction is needed.

2, What is the goal of PFC?



To improve the power factor and reduce the harmonics current, so as to improve the power quality.

3, What is the basic topology of PFC?

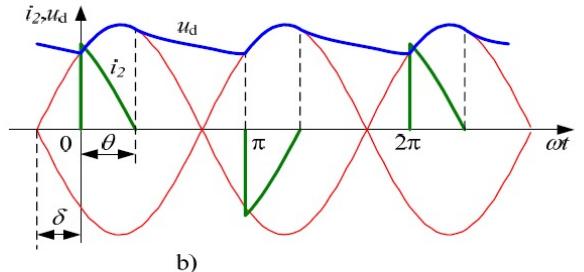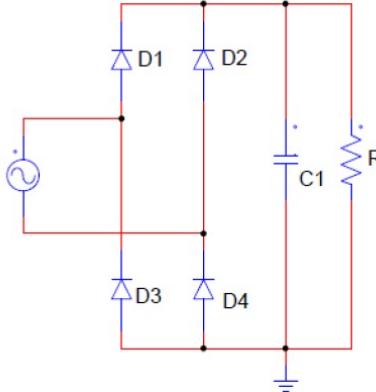The boost type converter is the basic circuit of PFC, as it has voltage boost function, and inductor connected to the grid is helping to improve the power quality.



PFC

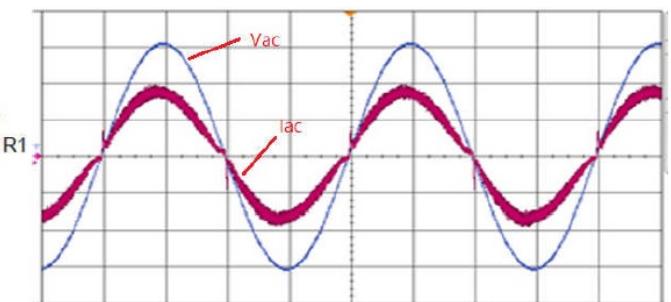
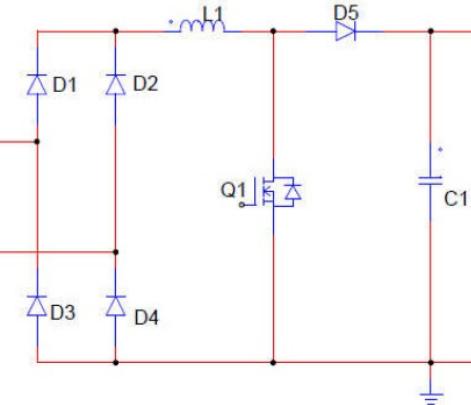


# The basic power factor circuit

Basic Requirement:

For high power factor converter:

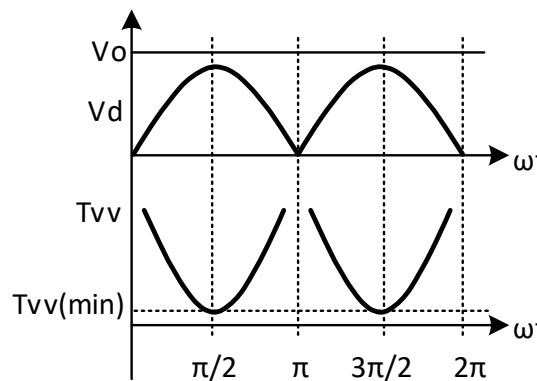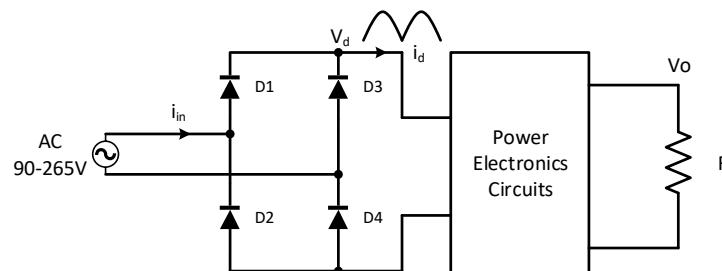1. Keep  $\phi=0$ , i.e.  $\cos\phi = 1$ ;
2. Reduce THDi, THDi < 5% (Meet IEC6100-3-2, IEEE-519)



1, The output is the DC voltage with small ripples.

The voltage transfer ratio:

$$T_{vv}(\omega t) = \frac{v_o}{v_{in}(t)} = \frac{v_o}{v_d(t)} = \frac{V_o}{\sqrt{2}V_s|\sin(\omega t)|}$$

When  $\omega t = k\pi + \pi/2$ ,  $T_{vv}(\omega t)$  is minimum;


When  $\omega t = k\pi$ ,  $T_{vv}(\omega t) \rightarrow \infty$ , need boost function

Converter to reduce the distortion at near zero-crossing:  
Boost, Buck-boost, cuk, flyback, etc.


2, The input current  $i_{in}(t)$  is in phase with  $v_{grid}(t)$ :

$$i_{in}(t) = A \cdot V_s |\sin(\omega t)|$$

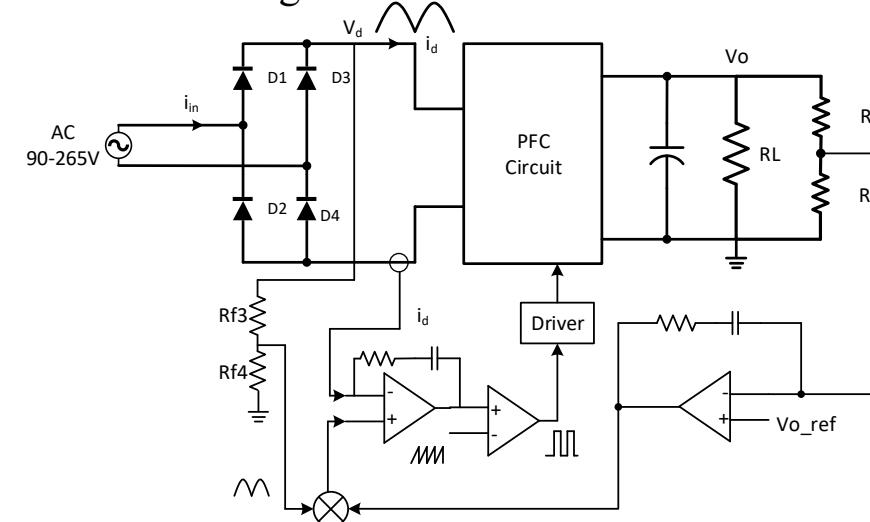
3, Output voltage is controllable by adjusting the input current magnitude.





Basic Control Diagram

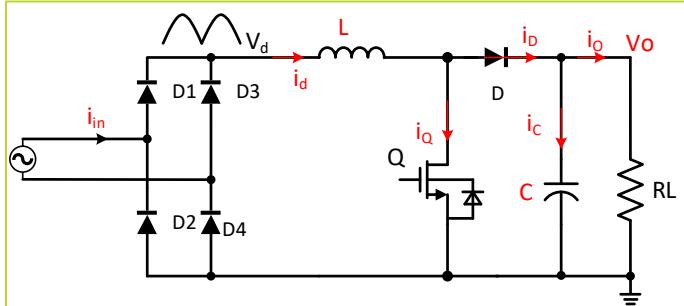

Stage I: switch Q is on.  
Inductor is charging

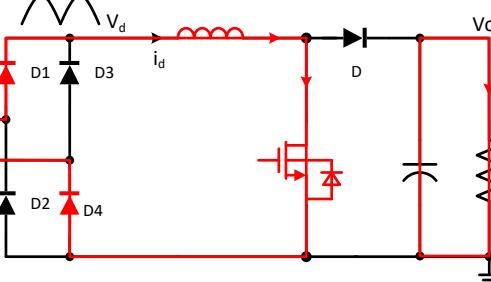

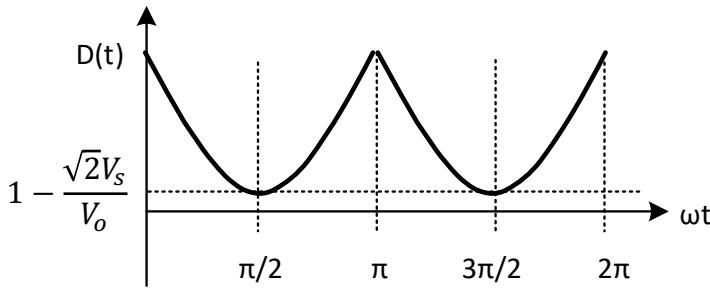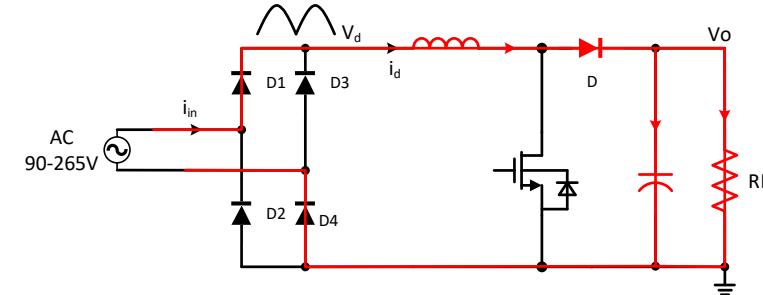Stage II: switch Q is off.  
Inductor is discharging




- 1, The output is the DC voltage with small ripples. Boost function to reduce the distortion at near zero-crossing.
- 2, The input current  $i_{in}(t)$  is in phase with  $v_{grid}(t)$ :  $i_{in}(t) = A \cdot V_s |\sin(\omega t)|$
- 3, Output voltage is controllable by adjusting the input current magnitude.



Duty cycle of a boost PFC converter: in one switching cycle, the average voltage on inductor is zero:

$$D(t) = 1 - \frac{\sqrt{2}V_s |\sin(\omega t)|}{V_o}$$

Positive Half Cycle

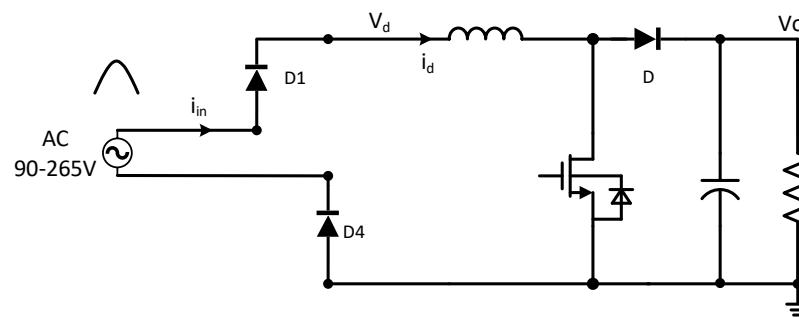

Negative Half Cycle

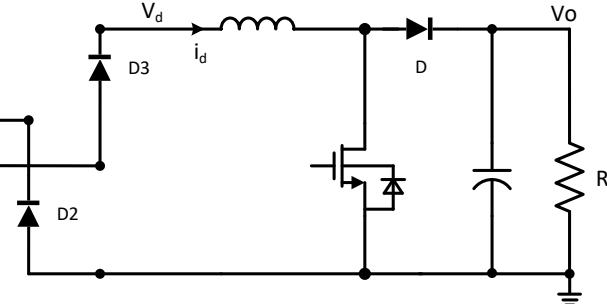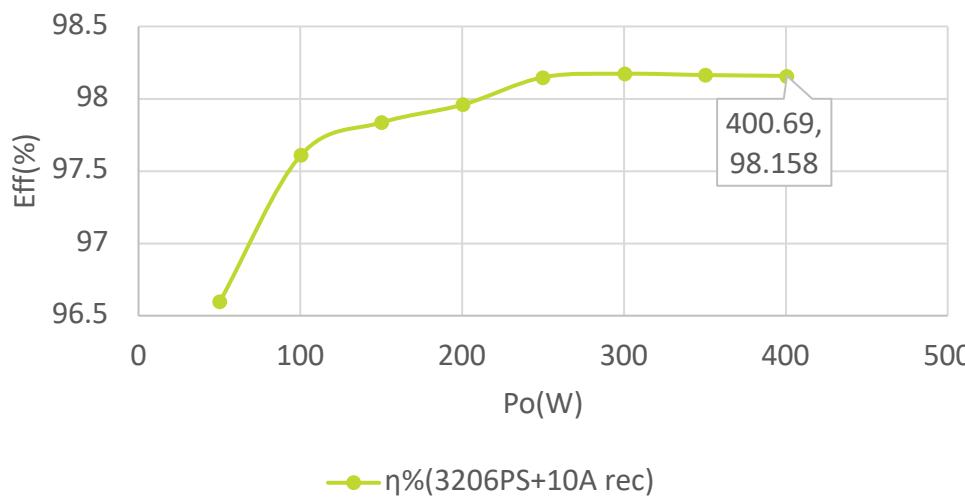
Measured Efficiency for 400W conventional PFC  
@ 230Vin

Two rectified diodes are always connected in series in the circuit,  
For a 230V/400W power supply as an example:

$$P_{con\_D1,2} = 2 \frac{2\sqrt{2}}{\pi} I_s V_f = \frac{2\sqrt{2}}{\pi} \times 1.77A \times 1V \\ = 3.19W$$


$\frac{3.19W}{400W} \times 100\% = 0.8\%$  efficiency loss in the rectified diode bridge.

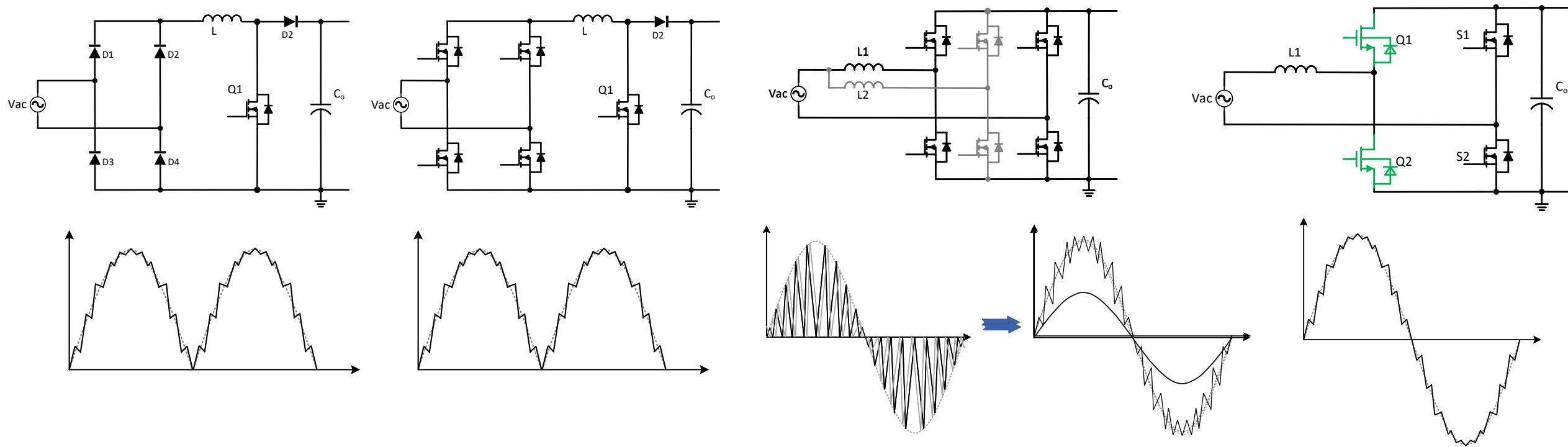At low line condition, the loss will be doubled.  
If the conduction loss is saved, the efficiency could be 99% at high line.





Topology	Diode Bridge Boost PFC	MOSFET Bridge Boost PFC	CRM Bridgeless Totem Pole PFC		CCM Bridgeless Totem Pole PFC
			Single Leg	Interleaved	
Efficiency (high line)	98.2%	98.8%	99 %	> 99%	> 99%
Power level	Mid	Mid to High	Low	Mid	High
Issue	High Power Loss	Low Surge Tolerance	High EMI	Complex Ctrl	
Components Count	Mid	Very High	Low	High	Low

# Bridgeless PFC Topology I

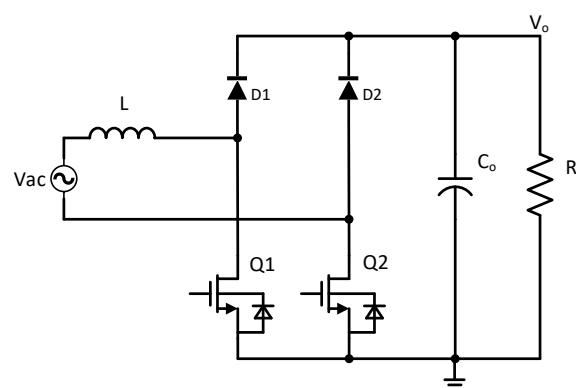



*Adding diodes on DC side*

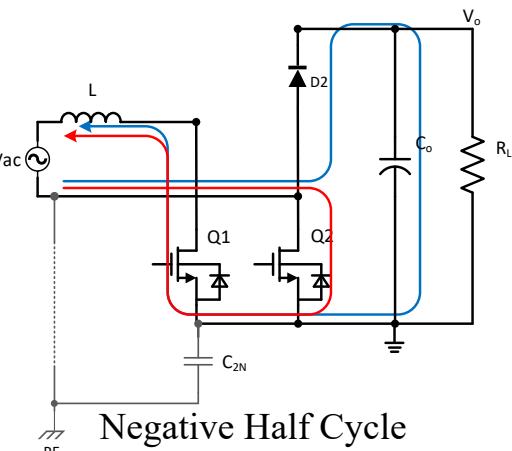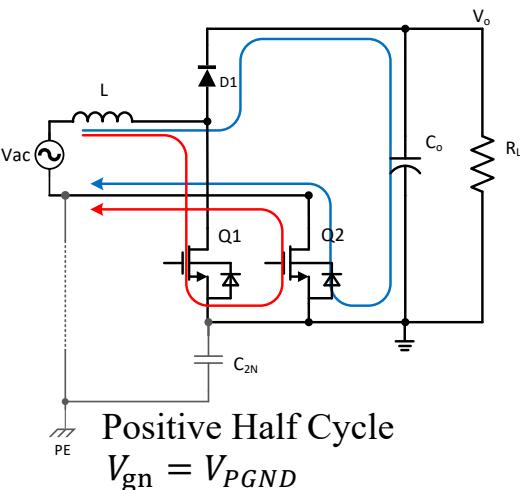

$$V_{gn} = V_{PGND} \text{ (Q2 is on)}$$


$$V_{gn} = V_o \text{ (D2 is conducting)}$$

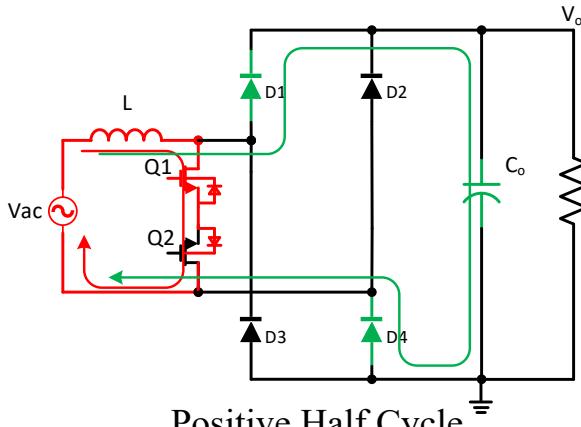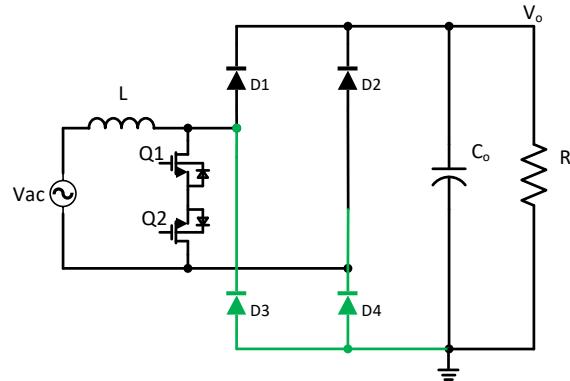At positive half cycle,  $V_{gn}$  is constant and there is no common mode noise;  
 At negative half cycle,  $V_{gn}$  is switching between  $V_{PGND}$  and  $V_o$ , common mode noise will be seen.



$$V_{gn} = \frac{V_o}{2} \text{ (Q1 on)}$$
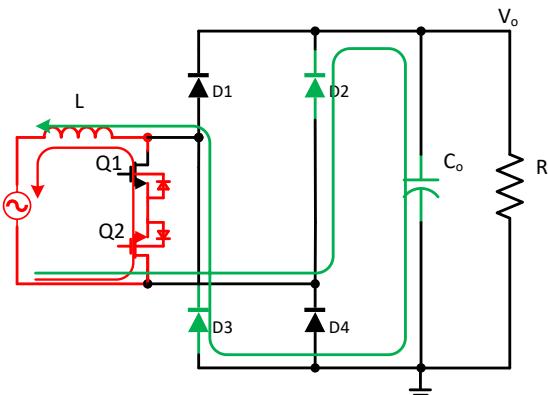
$$V_{gn} = V_{PGND} \text{ (D1, D4 conducting)}$$




$$V_{gn} = \frac{V_o}{2} \text{ (Q2 on)}$$


$$V_{gn} = V_o \text{ (D2, D3 conducting)}$$

When active switching Q is on,  $V_{gn}$  is  $V_o/2$ , when diodes are conducting,  $V_{gn}$  is tie to GND or  $V_o$ . The voltage change reduces from  $V_o$  to  $V_o/2$

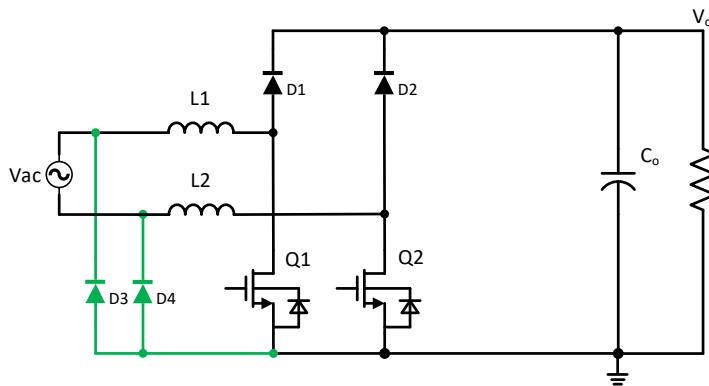Add two diodes D3, D4 on AC side and one more inductor.




Q1 is on

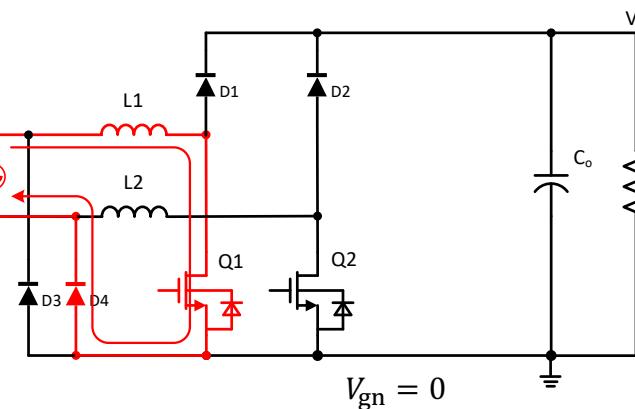


In Positive half cycle

Q1 is off

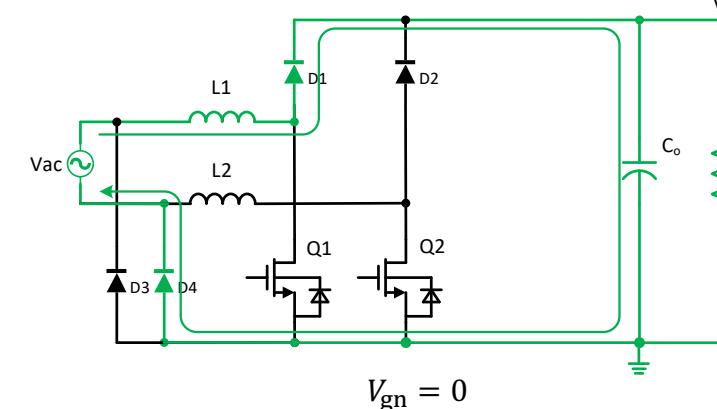


No common mode noise issue.

Q2 is on


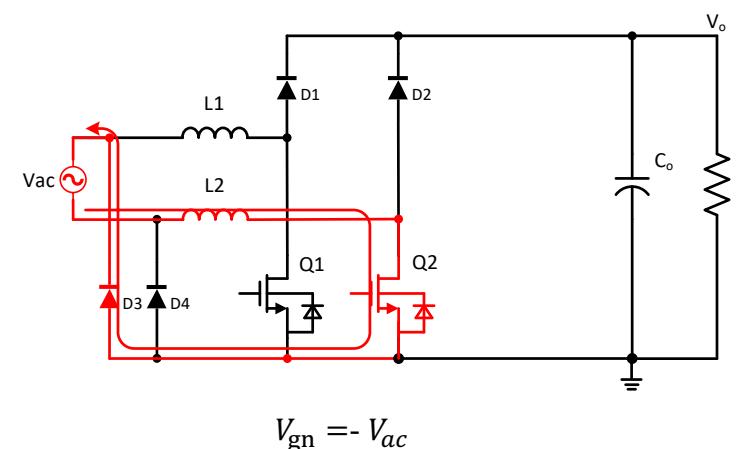


In Negative half cycle

Q2 is off

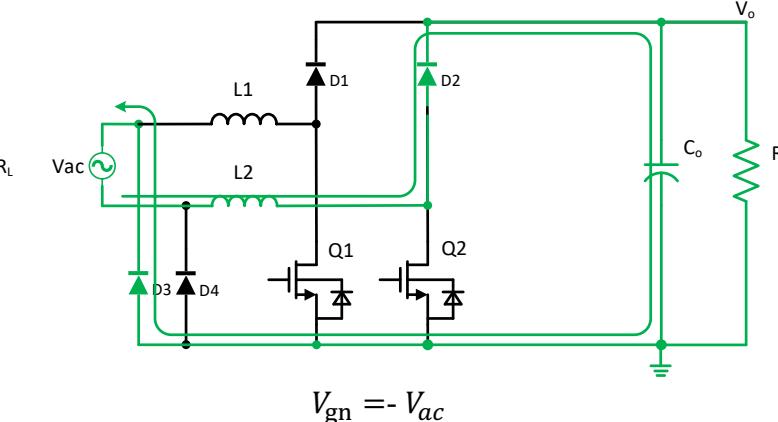
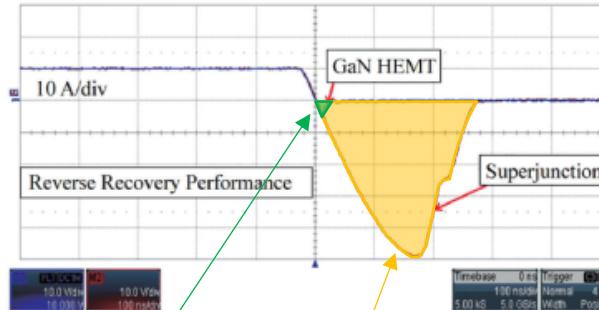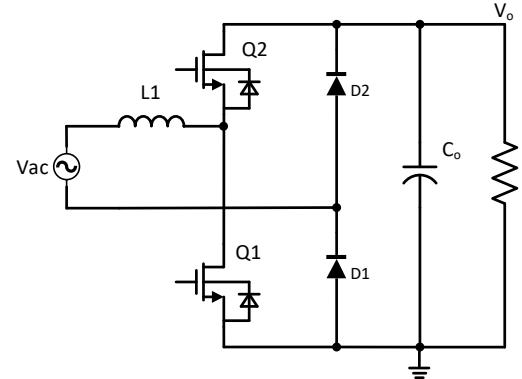
# Bridgeless PFC Topology IV-Totem Pole PFC




Parameter	TP65H035G4WS	IPB60R040CFD7
ID	46.5 A (Continuous)	50 A (for D=0.75)
Ron	41 mΩ	40 mΩ
Qg	22 nC	108 nC
Eoss(400V)	17 uJ	12.5 uJ
Qrr	150 nC (1A/ns)	1.76 uC (0.1A/ns)

Table 1: Comparison of GaN HEMT with equivalent CoolMOS IPB60R040CFD7


In Positive half cycle

Q1 is on

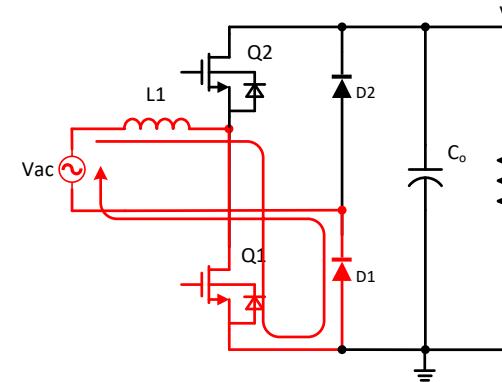

$$V_{gn} = V_{PGND}$$


Q1 is off

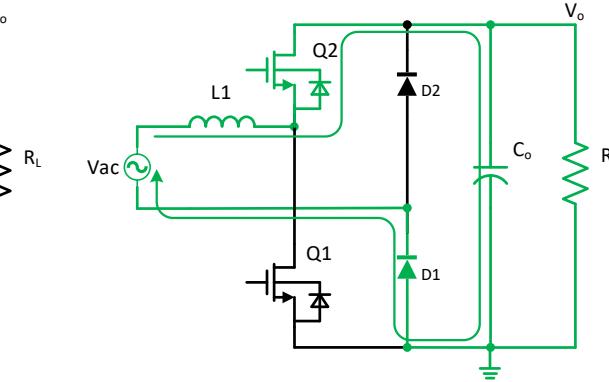

$$V_{gn} = V_{PGND}$$


In Negative half cycle

Q2 is on

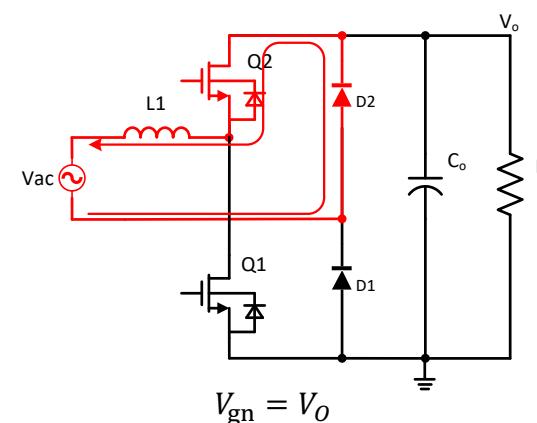


$$V_{gn} = V_O$$

Q2 is off


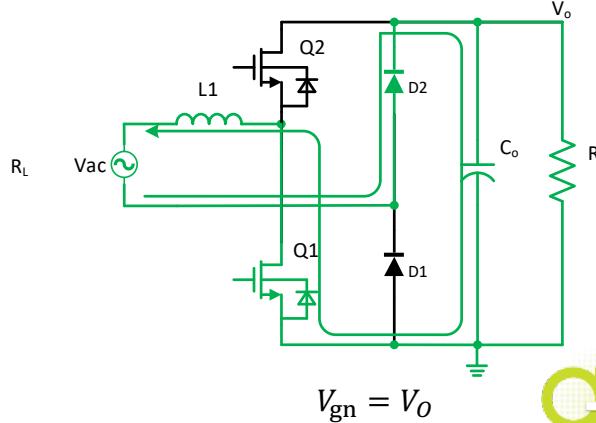


$$V_{gn} = V_O$$

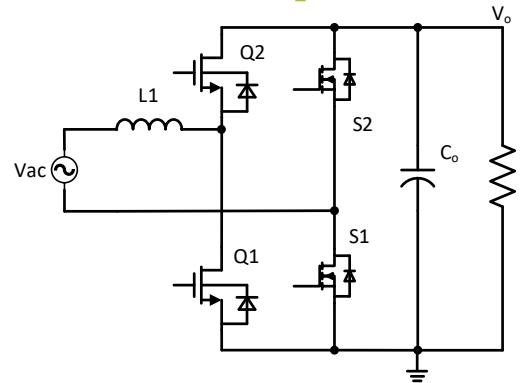


D1, D2 are replaced by MOSFETs S1 and S2,  
The conduction loss is reduced.

**Vf\_Diode=1V, Rds(on)\_MOSFET=20mΩ**

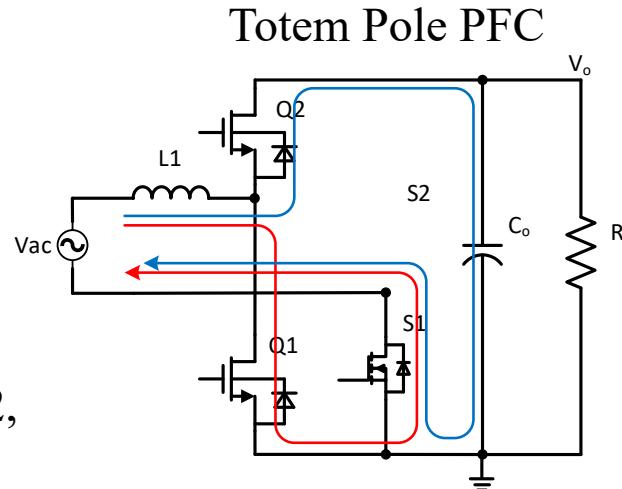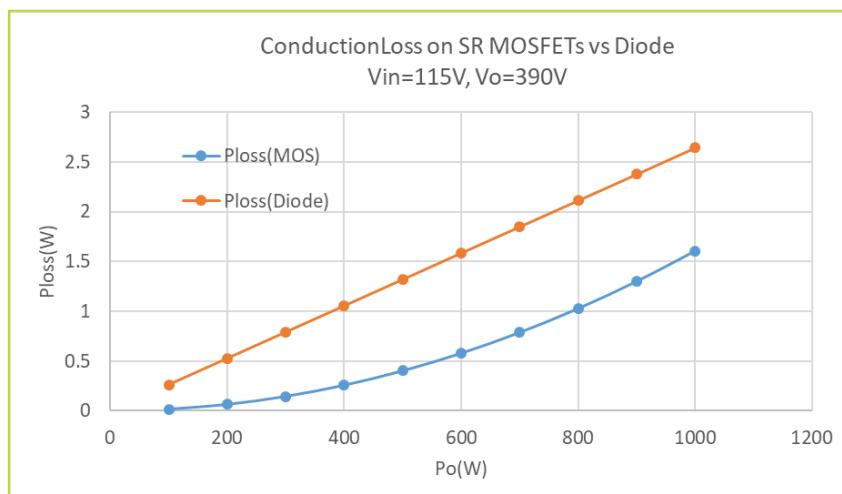

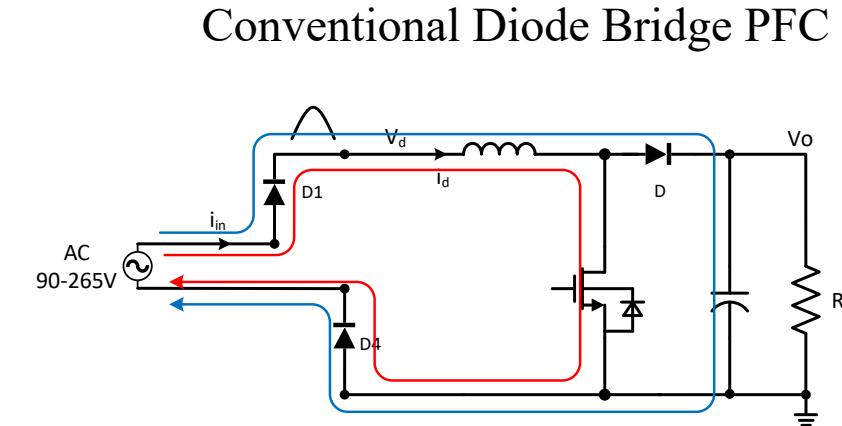
Q1 is on: Q1, S1 conducting  
Q1 is off: Q2, S1 conduction  
No Diode Vf drop.




Q1 is on: D1, Q1, D4 conducting  
Q1 is off: D1, D4, D conducting

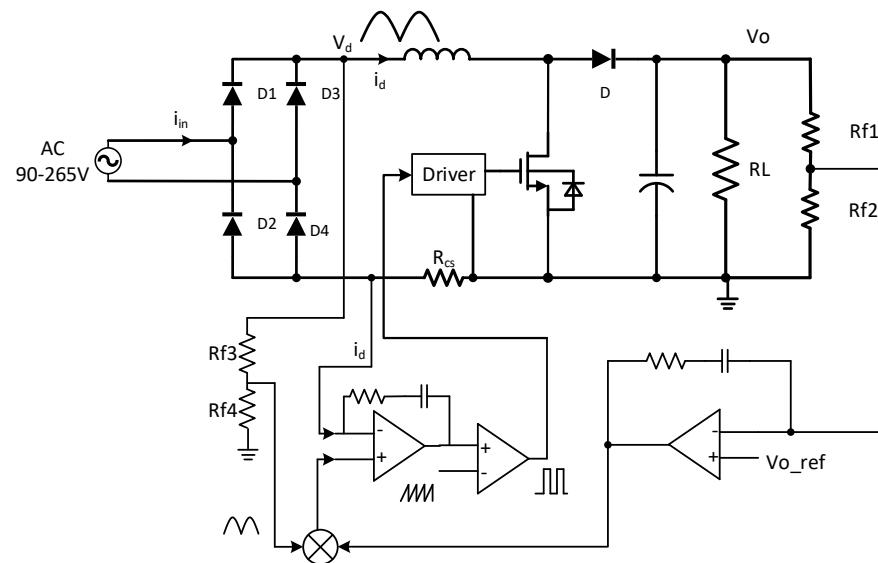- 1. Input voltage sensing, AC polarity detection
- 2. Input current and DC bus voltage sensing
- 3. GaN HEMT and SR MOSFET power stage
- 4. Inrush thermistor at Start-up
- 5. DSP control card interface


Control and driving circuit for traditional PFC



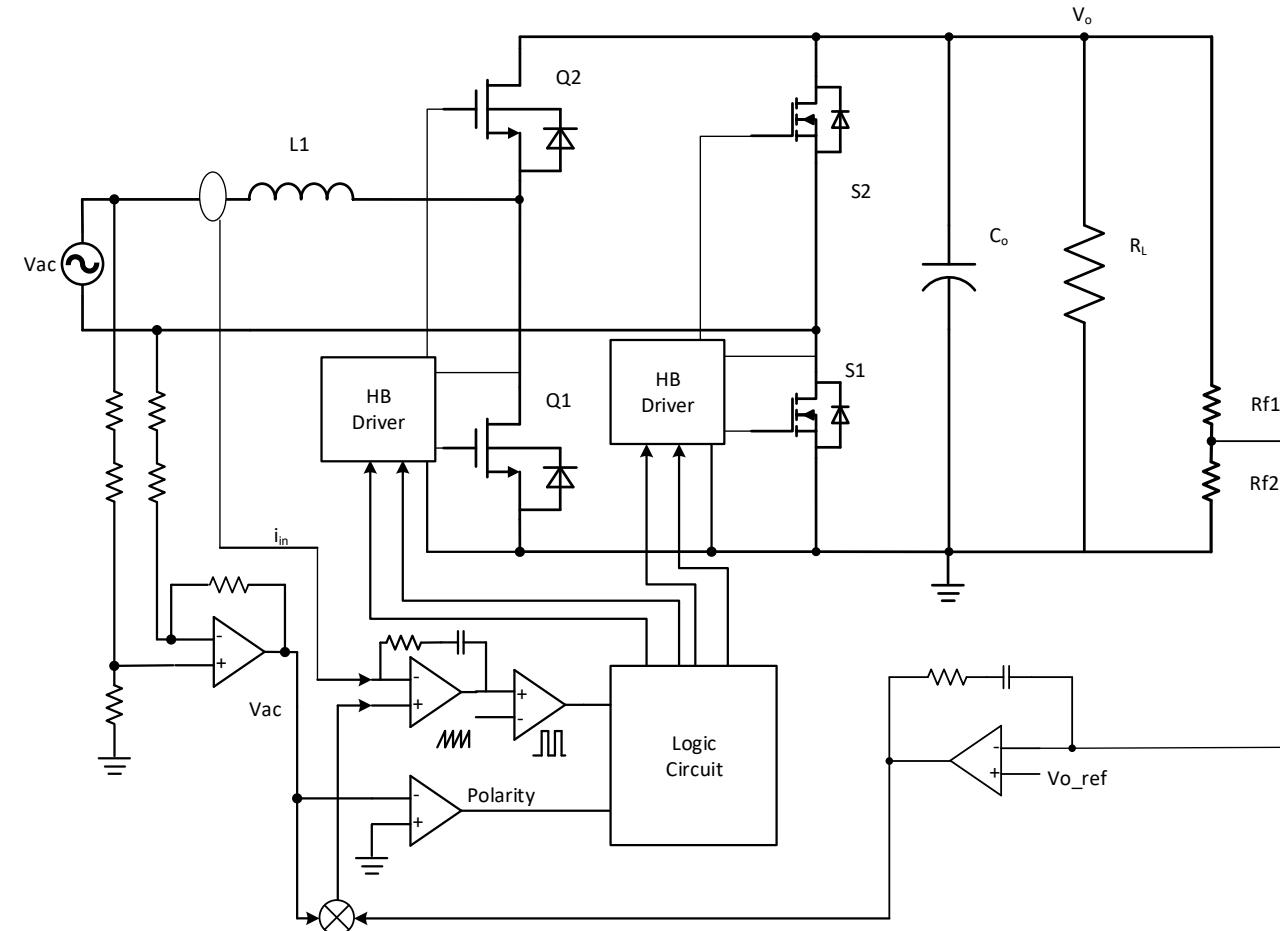
Control and driving circuit for Totem Pole PFC





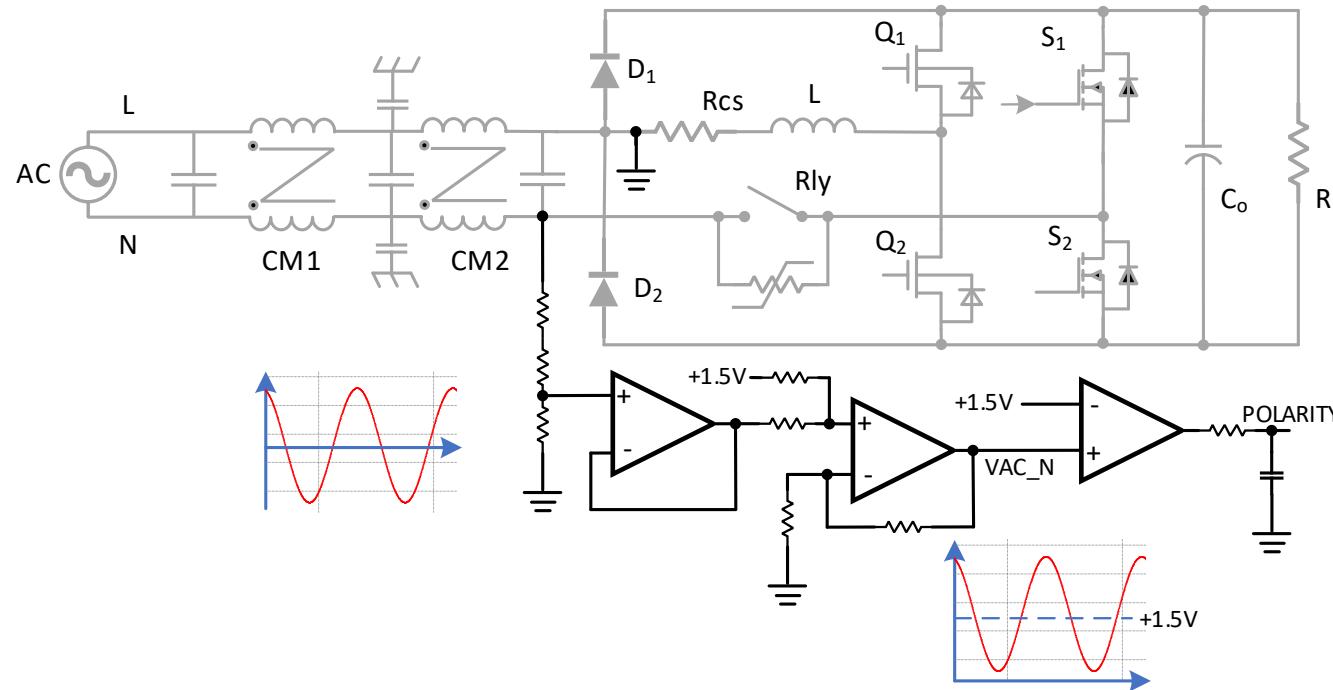
# 1. Input voltage sensing, AC polarity detection



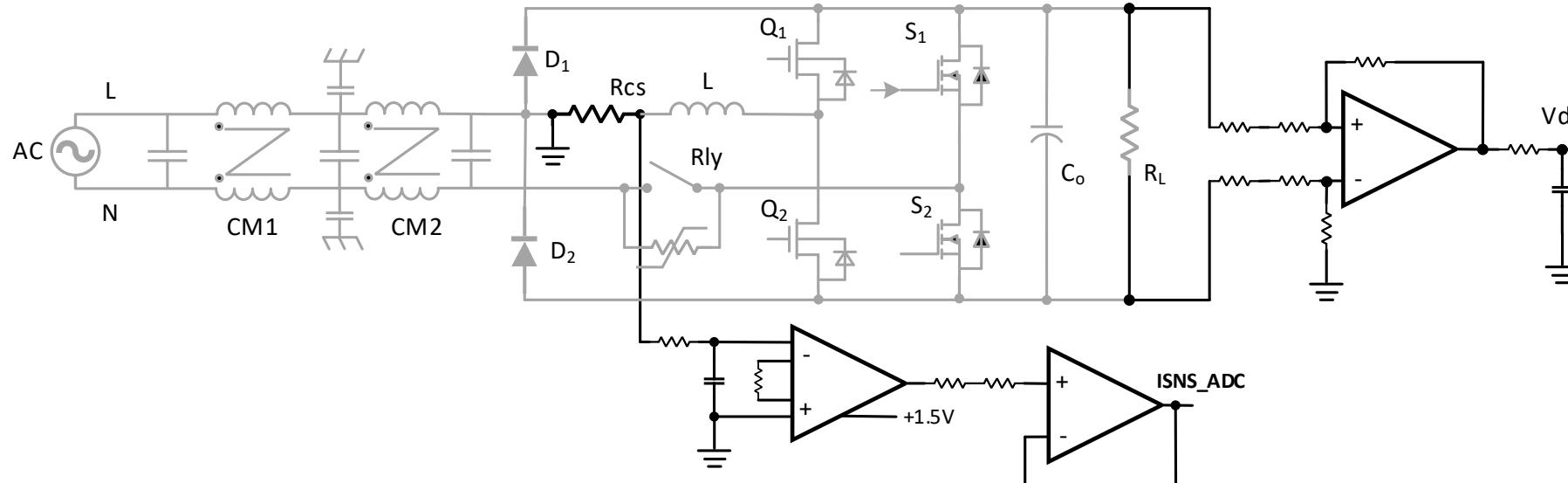
## 2. Input current and DC bus voltage sensing




# 3. GaN HEMT and SR MOSFET power stage

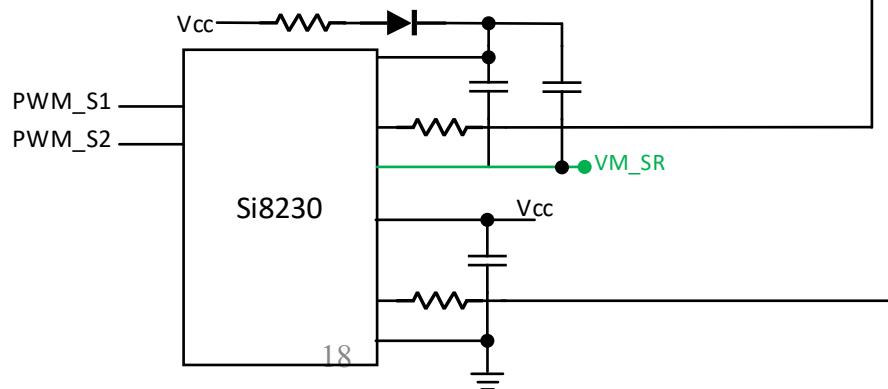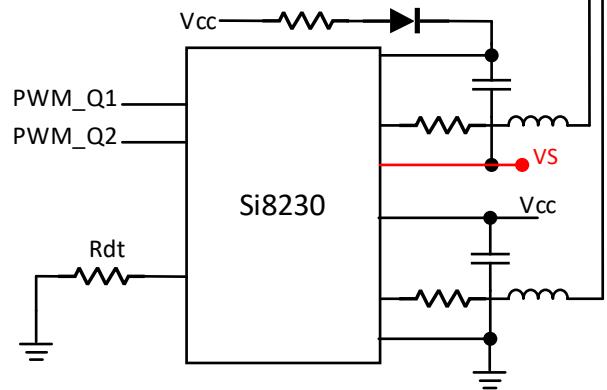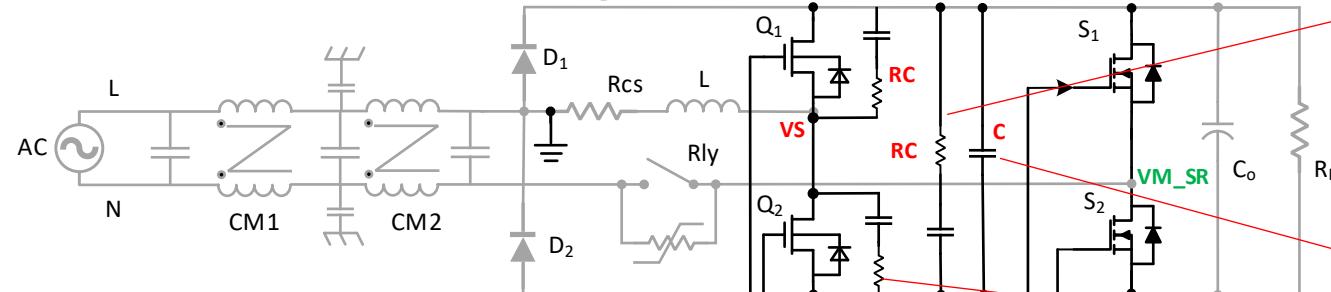

Top Layer

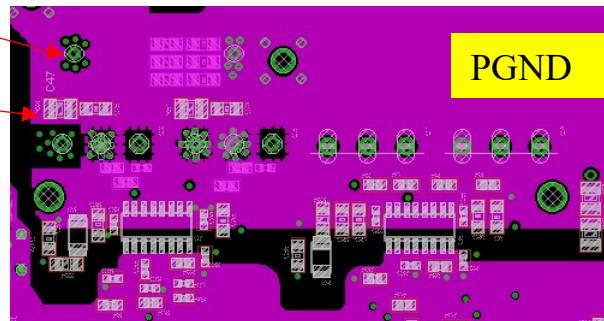

Mid Layer 1

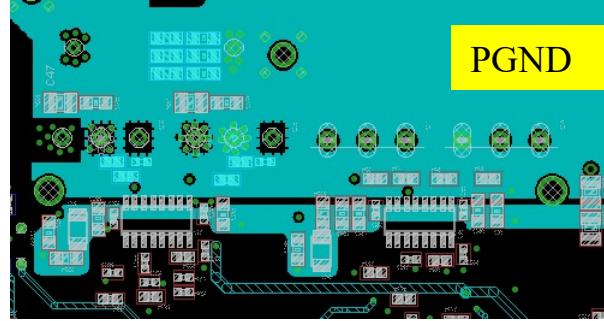


Mid Layer 2




Bottom Layer
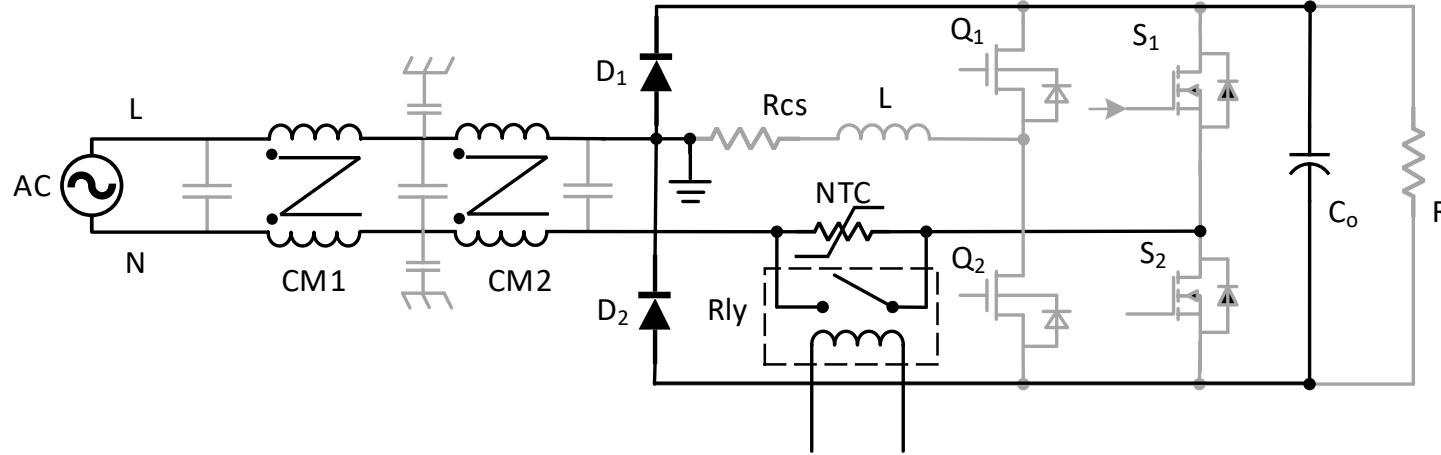
# 4. Inrush thermistor and bypass Diode at Start-up



- 1, When AC grid voltage is connected, DC bus capacitor will be pre-charged through NTC and D1, D2;
- 2, Relay is closed to bypass the NTC, and DC bus voltage increases to peak of the grid voltage;
- 3, PFC controller start to work. Q1 and Q2 will operate in PWM mode at positive half cycle.

# 5. DSP control card interface

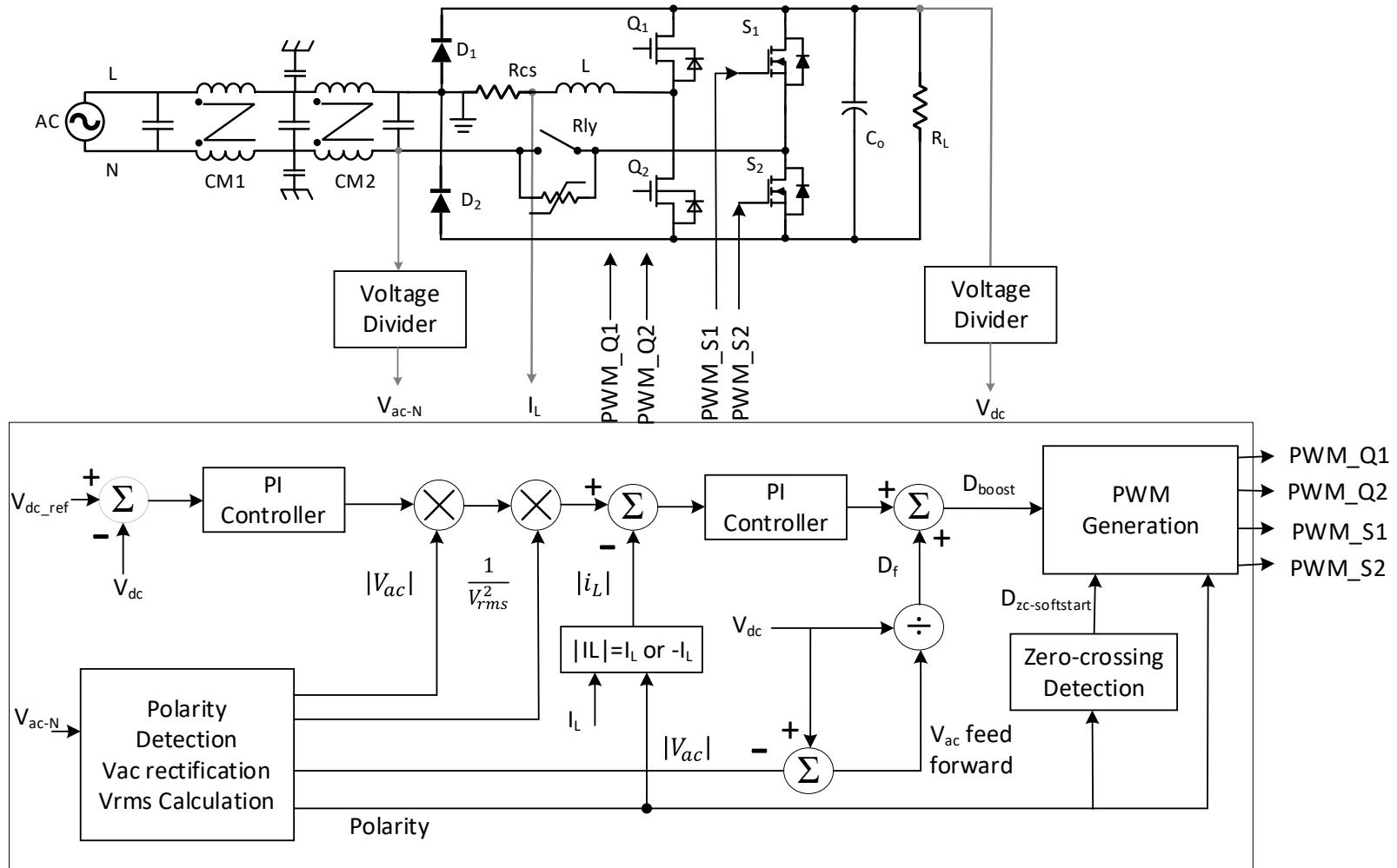


## 4 kW Bridgeless Totem-Pole: TDTPP4000W066C

Transphorm SuperGaN™ and Microchip dsPIC33CK


Test Setup and Conditions	
Evaluation Kit	TDTPP4000W066C-KIT
Operating frequency	66 kHz
Input voltage	85 V <sub>ac</sub> to 265 V <sub>ac</sub>
Output voltage	387 V <sub>dc</sub> ±5 V <sub>dc</sub> (programmable)
Digital power PIM	dsPIC33CK256MP506
GaN device	TP65H035G4WS
Gate resistor	30 Ω
Gate ferrite bead	200 Ω @ 100MHz
Snubber circuit	Not required
Deadtime	Programmable

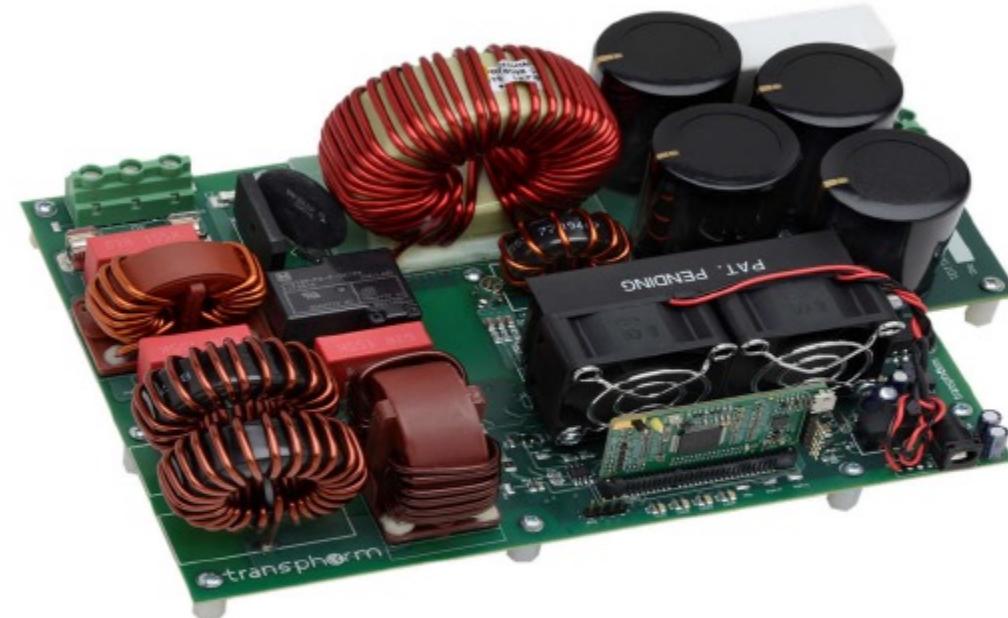Digital Controller: Microchip  
dsPIC33CK





Available at:




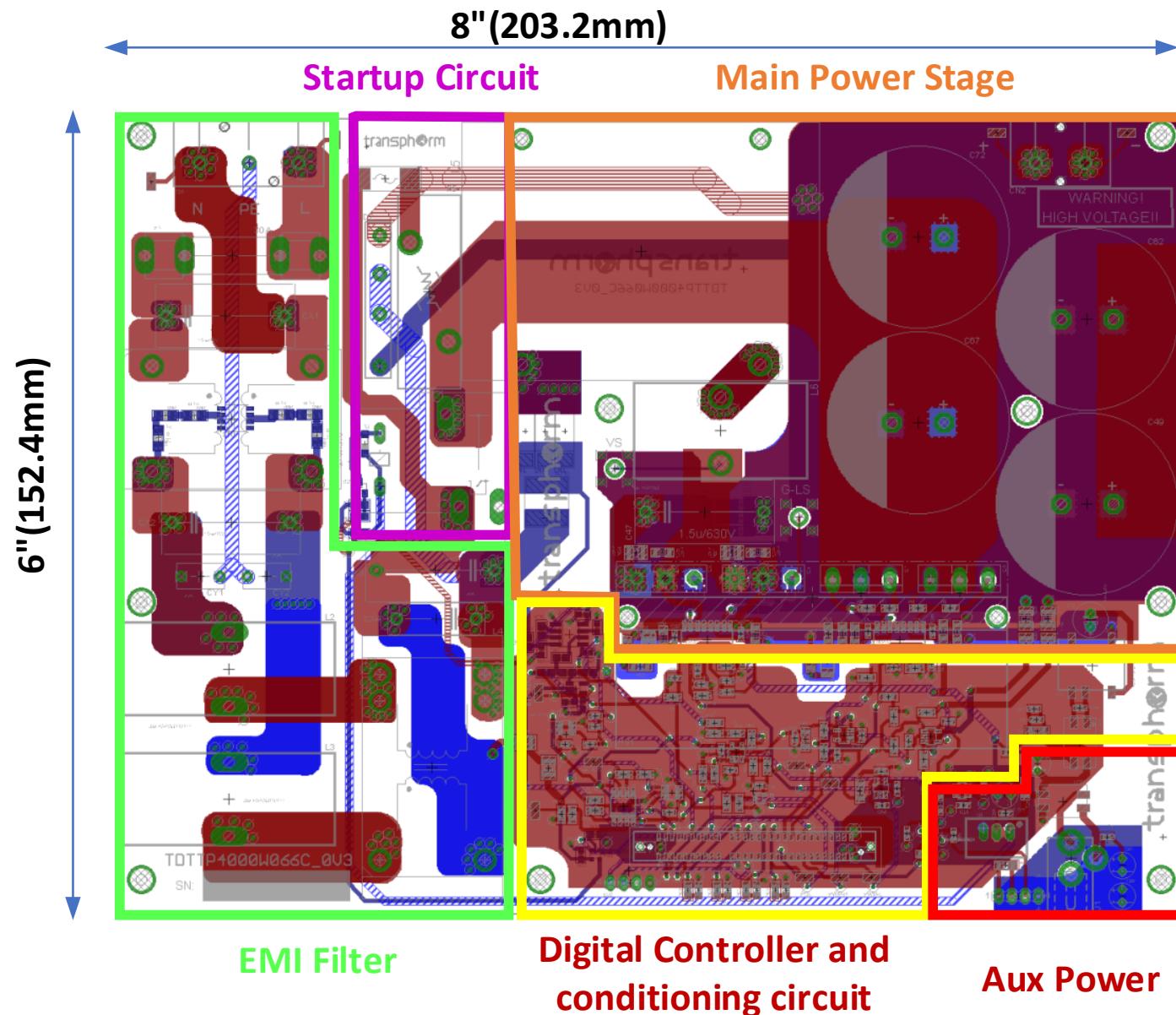

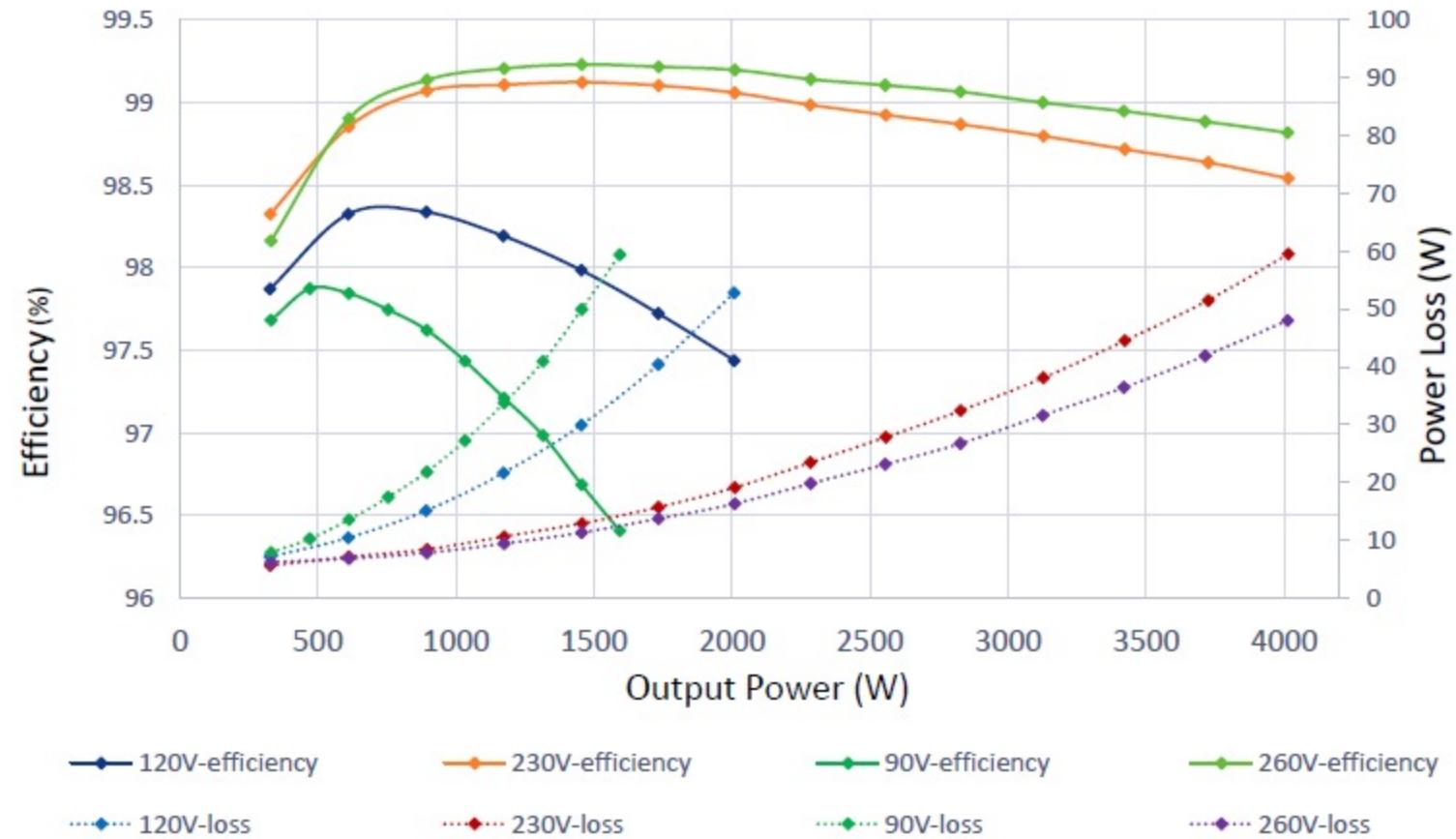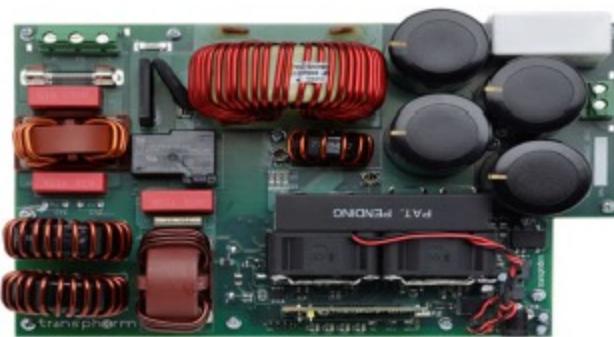
## 4 kW Totem-Pole Efficiency Sweep Results

Transphorm SuperGaN™ and Microchip dsPIC33CK



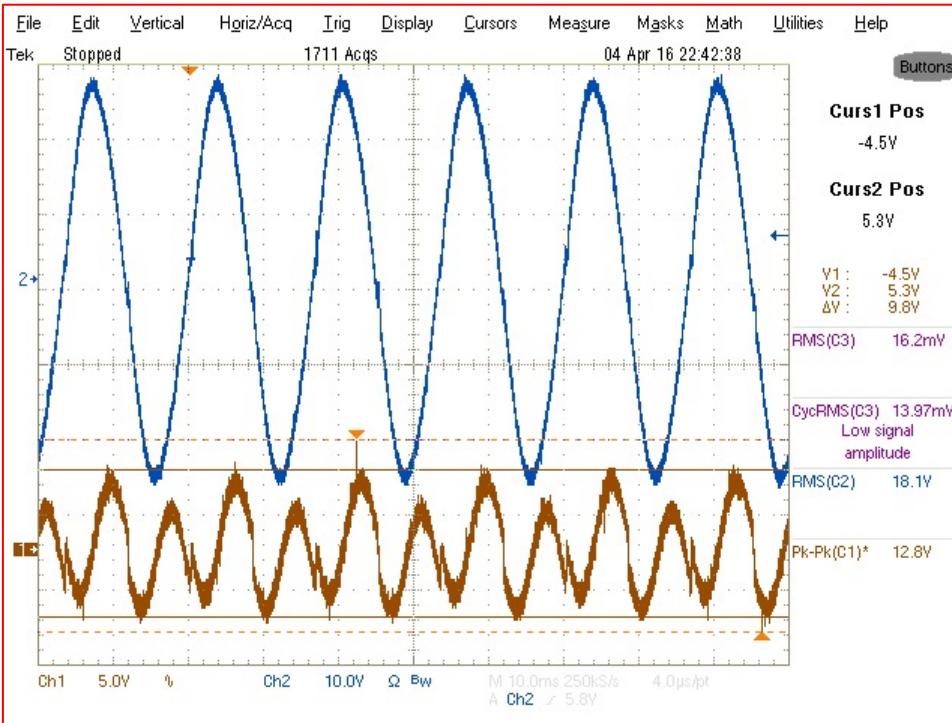


Low line 115V, 2kW full load

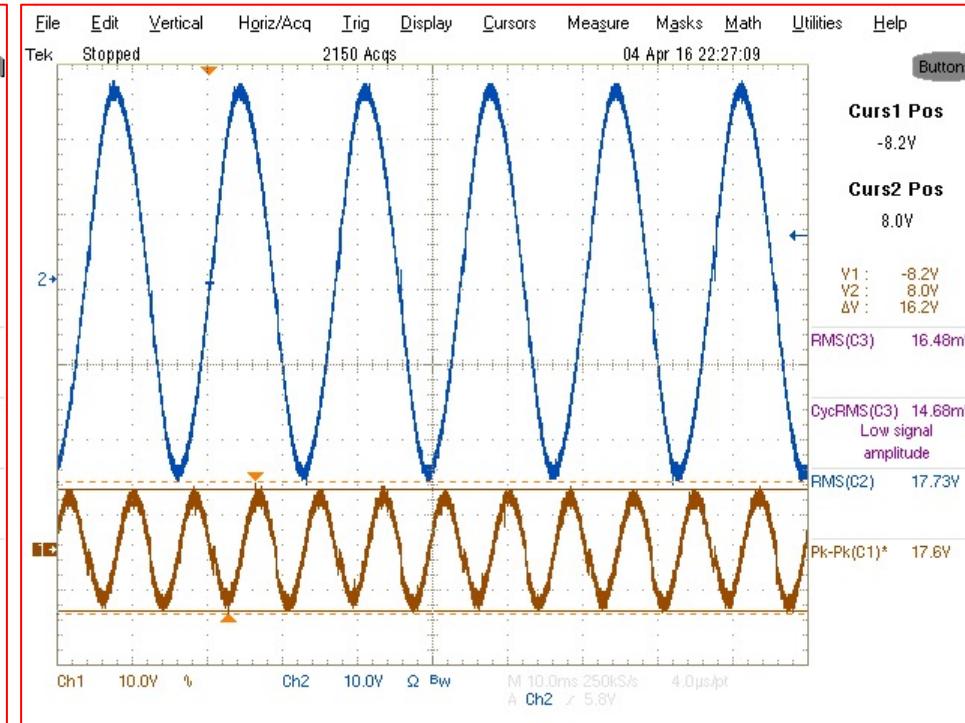


$Co=2250\mu F$ ;  
 $T_{holdup}=15ms$ ;  
 $\Delta V < 5\% Vo = 19.3V$

$$i_{corms} = 10.434A \text{ (4kW)}$$

4x 470uF, 2.82A Capacitors.

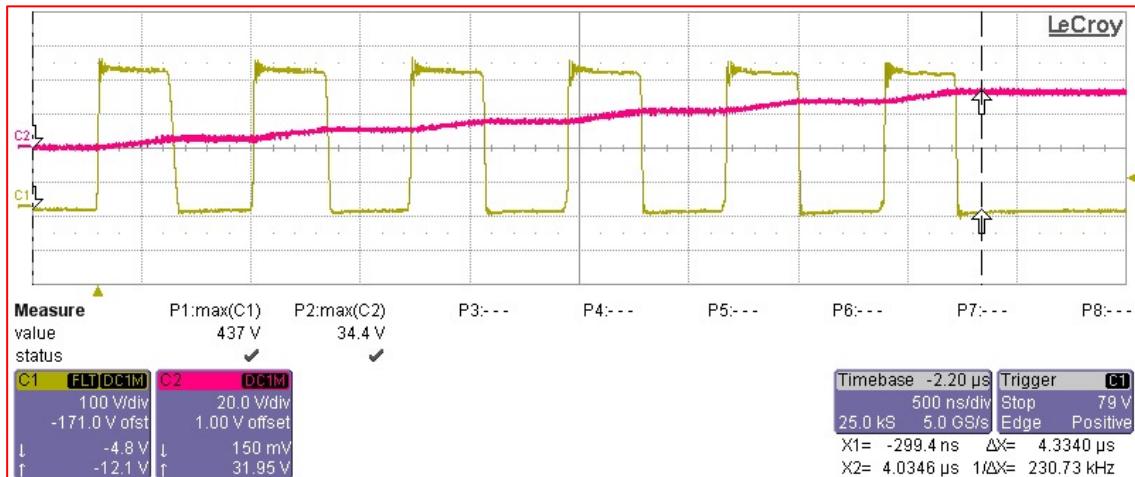


High Side switch to 34.4A

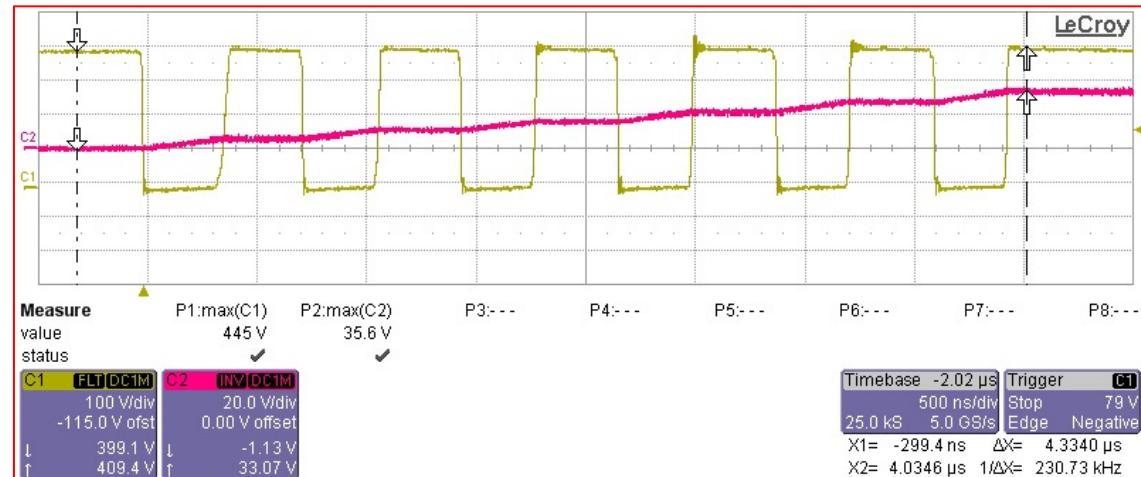


Low Side switch to 35.6A
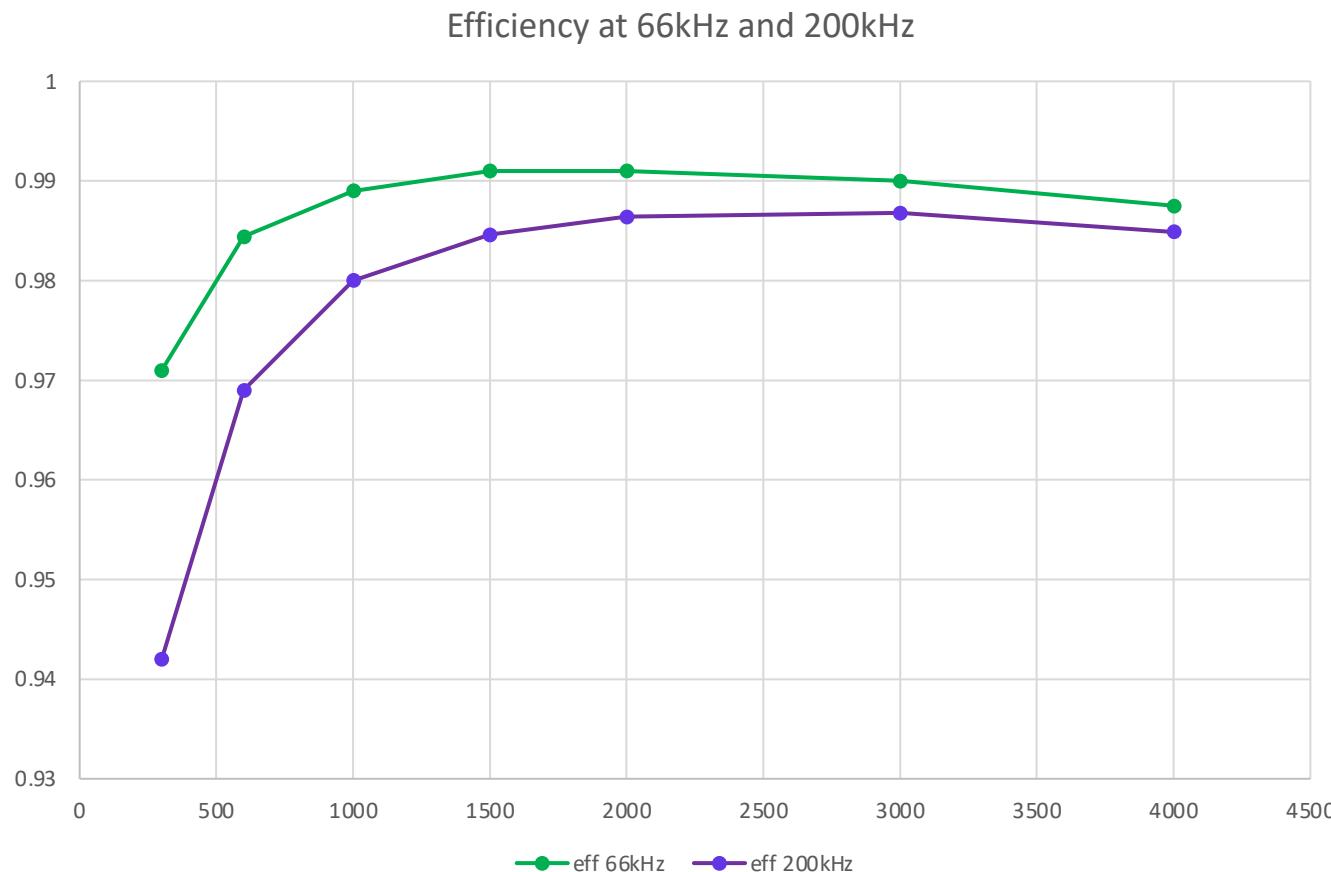
# Estimated Efficiency with 200kHz Switching



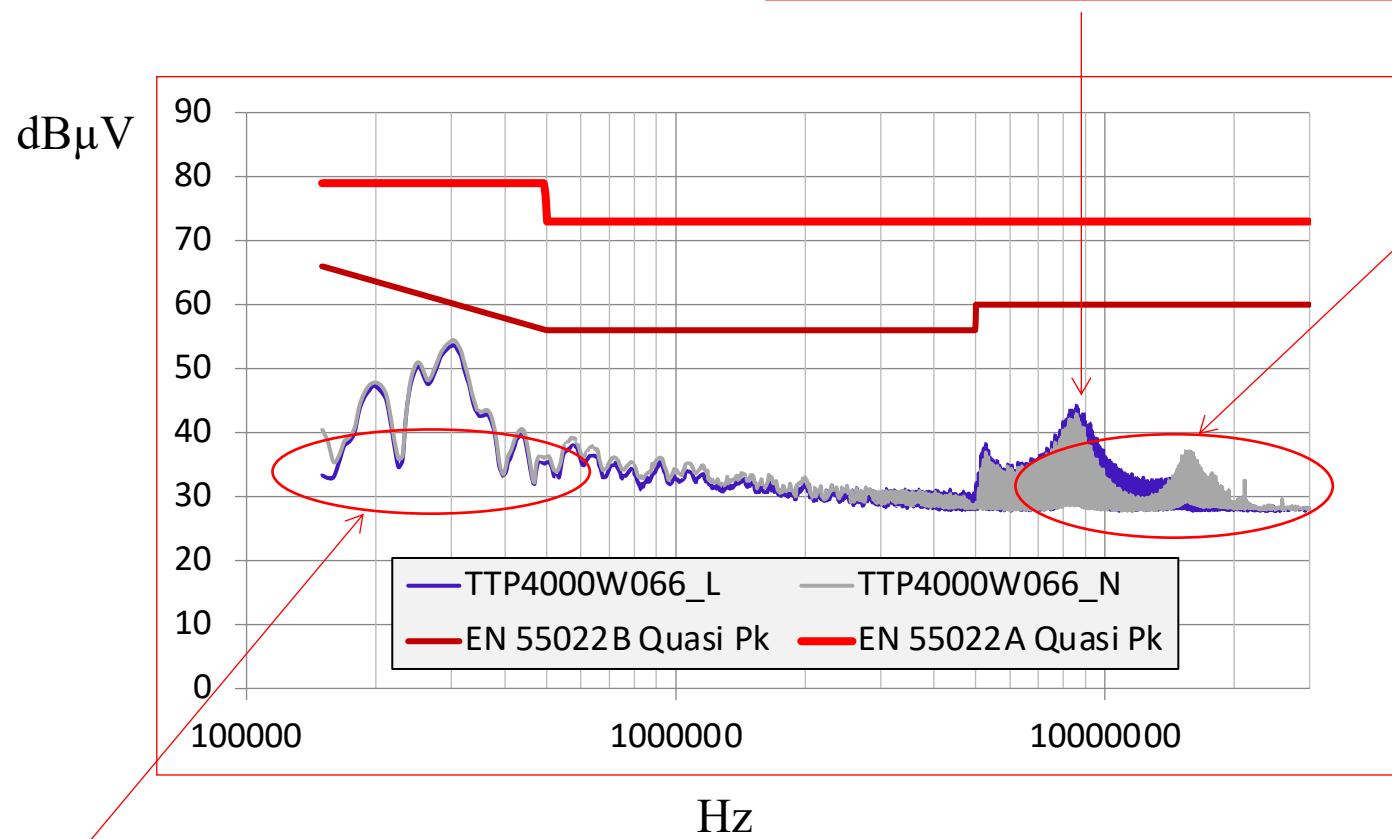Add small loose inductor L6 to reduce the PFC inductor self-resonance noise peak.




Use high permeability nano crystalline core to replace ferrite CM choke for lower copper loss and higher Lcm.


### Meet EN 55022 Class A

Test conditions: Vin= 115V, Vo=385V, Po= 1050W

# THDi and Power Factor

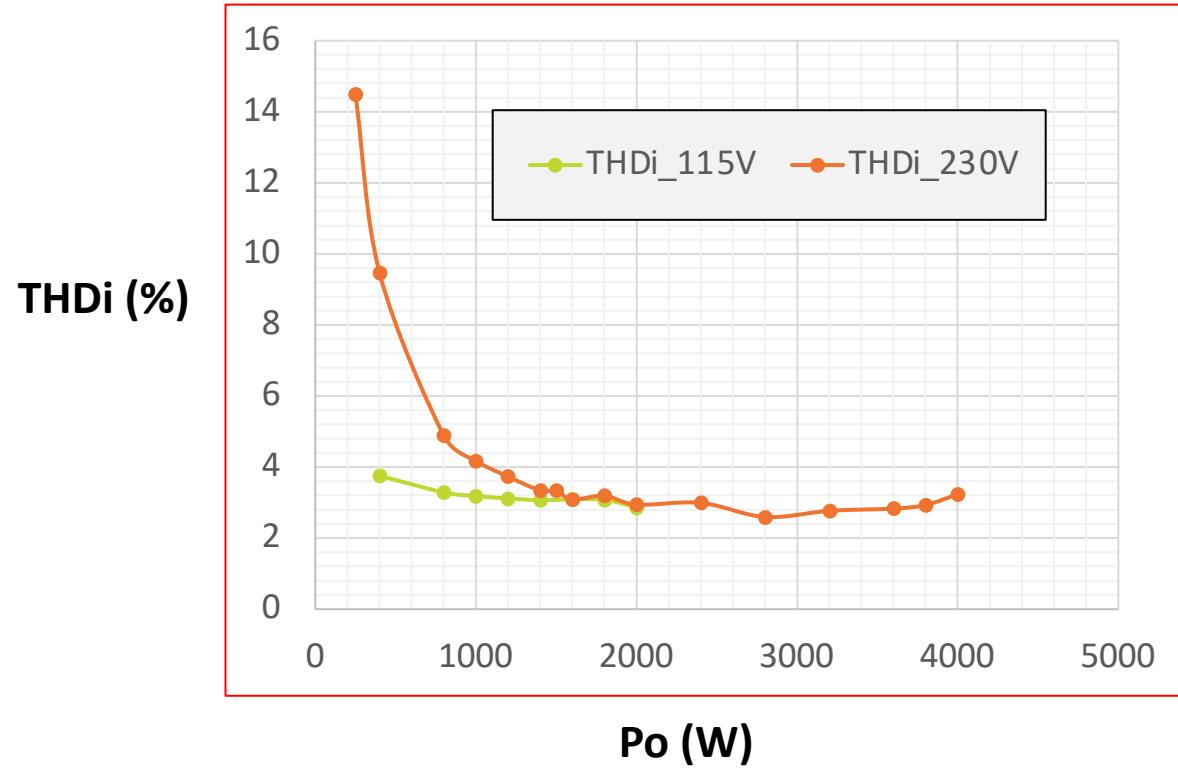

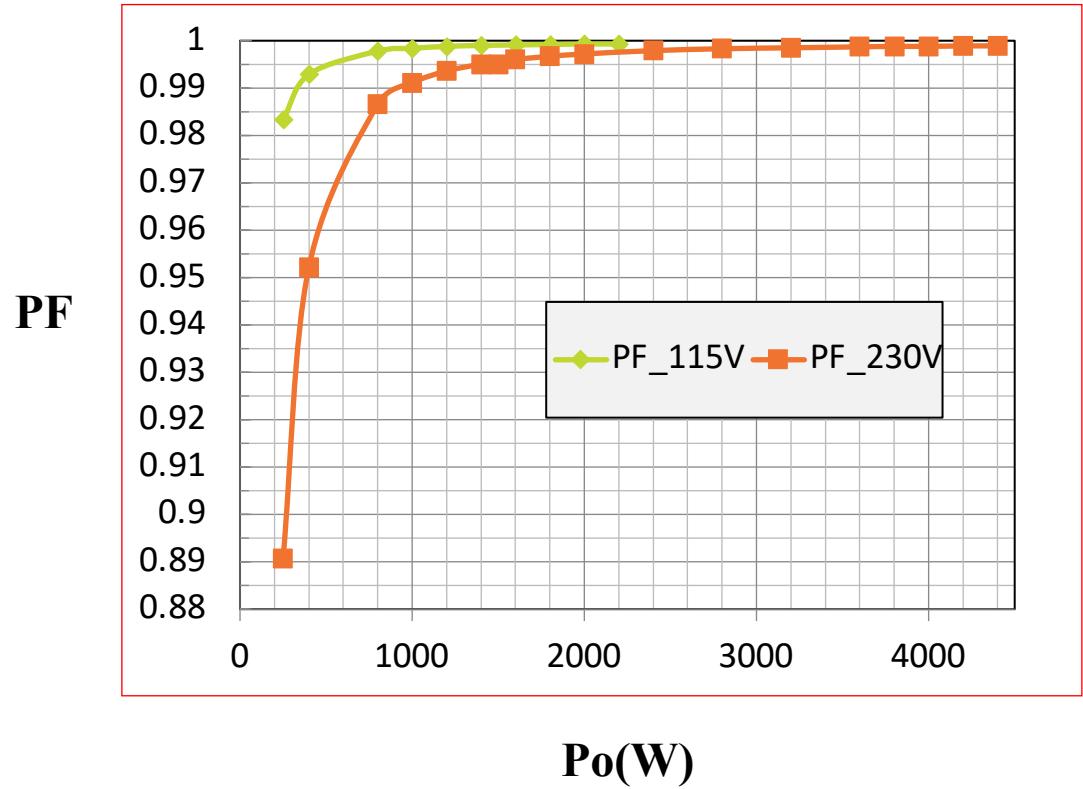THDi\_115V < 5%;  
THDi\_230V < 5% (@>25% Load)





Thank you!

**transphorm**

Highest Performance, Highest Reliability GaN

